

# SATHYABAMA UNIVERSITY

(Established under section 3 of UGC Act, 1956)

Course & Branch: B.E /B.Tech – CSE/IT/ECE/EEE/E&C/EIE/ETCE

Title of the paper: Circuit Theory

Semester: II

Max. Marks: 80

Sub.Code: 6C0026

Time: 3 Hours

Date: 26-05-2008

Session: FN

---

## PART – A

(10 x 2 = 20)


Answer All the Questions

1. State and explain superposition theorem.
2. What are the limitations of Thevinin's theorem.
3. What is the significance of initial conditions? Write a note on initial conditions in basic circuit elements.
4. Define the term rise time and time delay.
5. What do you mean by resonance and anti-resonance?
6. What is the Q-factor? Find the value of Q-factor for an inductor and capacitor.
7. Differentiate between planar and non-planar graph.
8. What is graph of a network? Give different types of graph.
9. What are the advantages of Pspice software.
10. List the steps involved to run a program written in Pspice.

**PART – B**  
**Answer All the Questions**


**(5 x 12 = 60)**

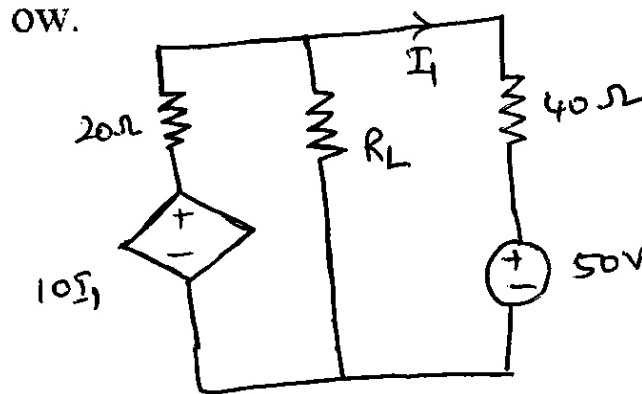11. Determine the value of  $R_L$  so as to have maximum power transfer to  $R_L$  in the circuit shown below.



(or)

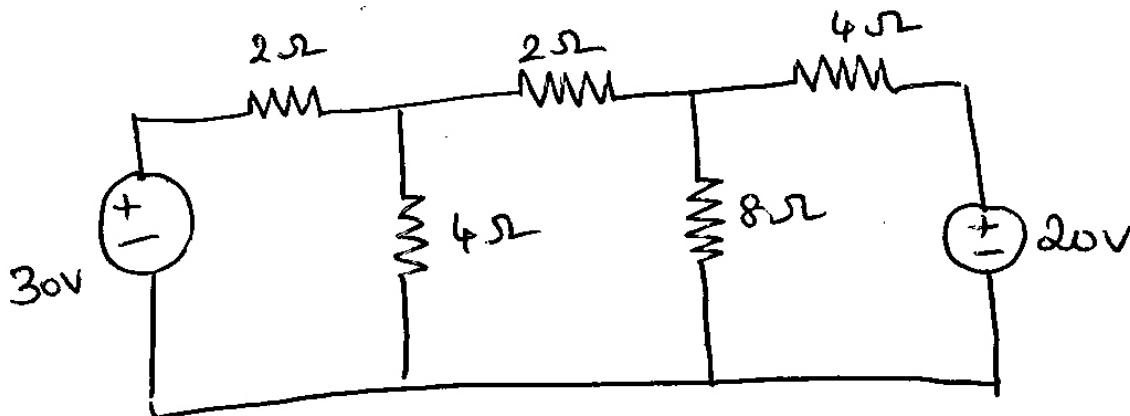
12. Verify Tellegen's theorem for the network shown.



3. Obtain the expression of current it is connected to a dc voltage through switch K instantaneously and having a resistor and capacitor in its series. Assume initial voltage across capacitor is zero.

(or)

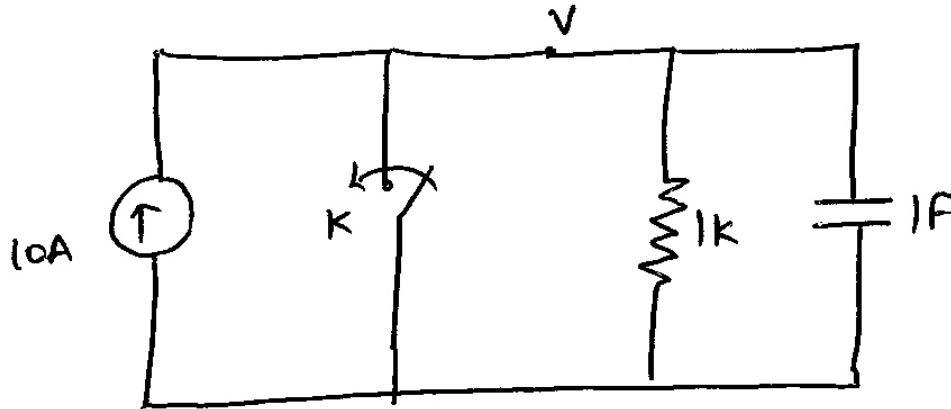14. In the network shown in figure switch K is opened at  $t = 0$ . Solve for  $V$ ,  $dv/dt$  and  $d^2v/dt$  at  $t=0^+$ .




15. A parallel resonant circuit has a coil of  $150\mu\text{H}$  with  $Q$  factor of 100 and is resonated at 1 Mhz
- Specify the required value of capacitance
  - What is resistance of the coil
  - What is the resistance of the circuit at parallel resonance.
  - What is absolute bandwidth of resonant circuit.

(or)


16. Explain briefly the following terms
- Self inductance
  - Mutual inductance
  - Coefficient of coupling

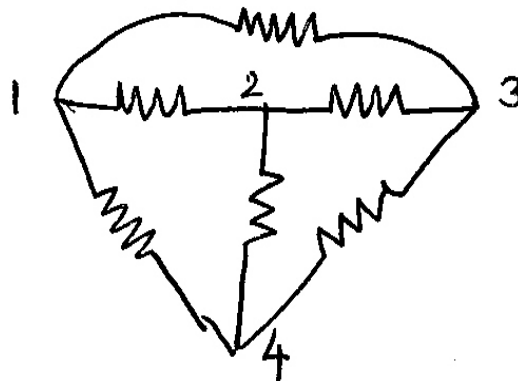17. In the following network the numerical values of resistance also indicate the branch numbers. Write the oriented graph of the network. Select a tree with 1,2,3 as tree branches, write tie-set and cut-set schedule.




(or)

18. Find dual of the network shown below

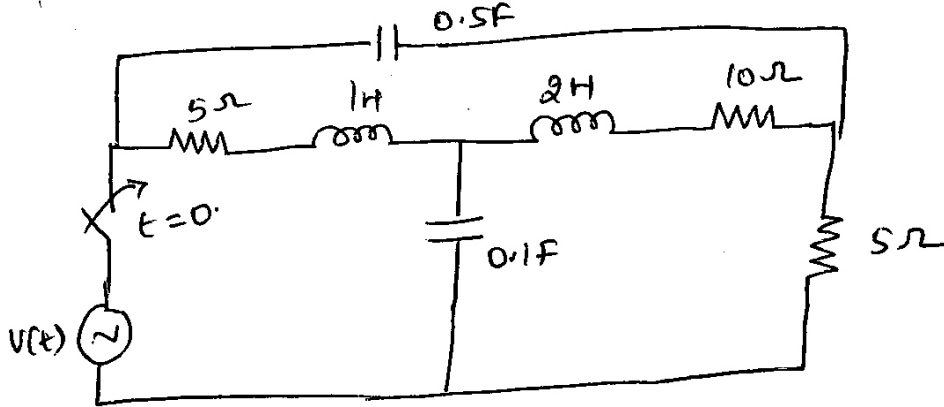

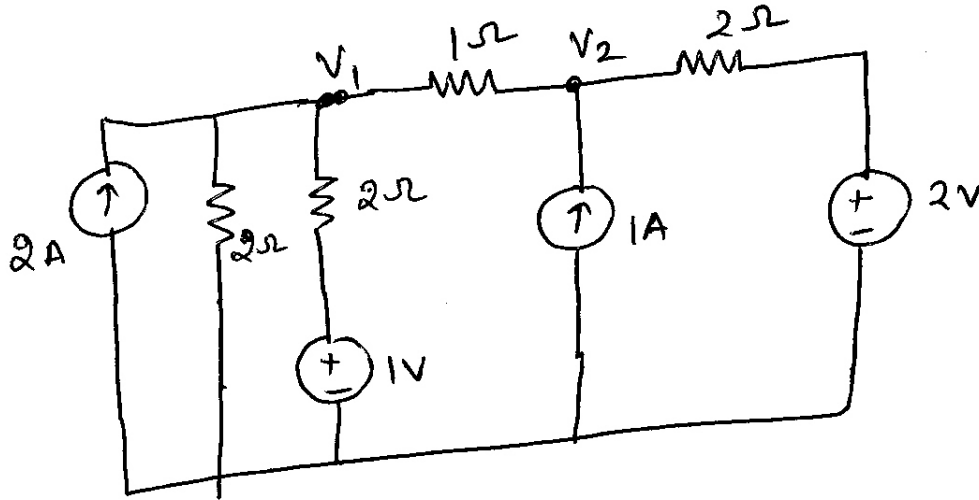19. Write a Pspice program to find  $V_1$  and  $V_2$  shown in the circuit.



(or)

20. Write a Pspice program for the network shown in figure reaches a steady state with switch K closed. At  $t=0$ , the switch is opened find  $i(t)$  for  $t>0$ .

