

- (C) 1 ns. (D) 3.2 ns.
- f. The number of states in its counting sequence that a ring counter consisting of 'n' flip-flops can have is
- (A) $2^n - 1$ (B) 2^{n-1}
 (C) n (D) 2^{n+1}
- g. The number of select input lines required by a 1-to-8 demultiplexer are
- (A) Two. (B) One.
 (C) Four. (D) Three.
- h. The Maximum binary number counted by a ripple counter that uses form FFs is
- (A) $(0000)_2$ (B) $(1011)_2$
 (C) $(1111)_2$ (D) $(0101)_2$
- i. The cut-in voltage of the aluminium n-type Schottky diode is about
- (A) 0.5 V. (B) $0.5 \mu\text{V}$.
 (C) 0.35 V. (D) 0.35 mV.
- j. In applications where measurement of a physical quantity is involved, the OPAMP circuit recommended is
- (A) Basic non-inverting amplifier. (B) A comparator.
 (C) An active filter. (D) An instrumentation amplifier.

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. What is it that an OPAMP contains to achieve a very high voltage gain? What do you mean by common-mode rejection as applied to an OPAMP? (4)
- b. With a circuit for illustration, explain the effect of the input offset voltage for the OPAMP, V_{io} (which is normally specified in the manufacturer's data sheet) on the output. (7)
- c. Write a note on frequency response of OPAMPS. (5)

Q.3 a. What is the role of an OPAMP in an active filter? Define an ideal low-pass filter. Write the equation for the squared magnitude response of a low-pass Butterworth filter. Mention the variables involved in the above equation. (7)

b. Design a first order high-pass active filter for a cut-off frequency of 10 KHz providing a pass-band gain of 1.5. Illustrate the circuit of the filter designed and find the magnitude of the response for the following frequencies:

- (i) 10 Hz
 - (ii) 100 Hz
 - (iii) 500 Hz
 - (iv) 1000 Hz
- (9)


Q.4 a. Starting from fundamentals, explain the meaning of the term “SWITCHING TIME” as applied to a semiconductor diode. What is the use of the above quantity? (8)

b. What is the advantage of Schottky diode over an ordinary PN-junction diode in terms of speed of operation? Support your answer with relevant comments. (4)

c. What are the advantages of switched capacitor filters? (4)

Q.5 a. What is an ADC? Compare the performance of a flash ADC with successive approximation ADC. (6)

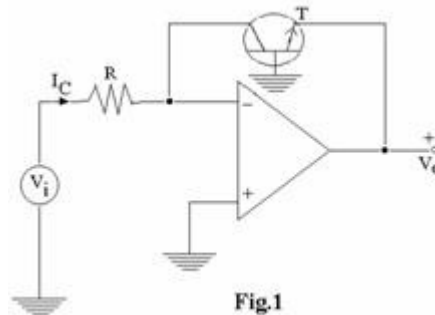b. For the OPAMP circuit shown in the Fig.1, show that the output will be proportional to the logarithm of the input voltage. (10)



Comment on the disadvantage of the circuit, if any.

Q.6 a. What are NMOS and PMOS logic circuits? Write the circuit of an NMOS nor-gate and briefly explain. (7)

b. Write a note on a ROM with an illustration. (9)

- Q.7** a. What are the important elements of a bipolar IC? How are bipolar logic circuits broadly classified? Give examples for each classification. (8)
- b. What is the other name given to the ECL family? Comment on your answer. What are the characteristics of ECL family? (8)
- Q.8** a. What is a digital magnitude comparator? With a circuit diagram that uses exclusive-NOR gate, AND gates and inverters, explain the operation of a single-bit magnitude comparator. (7)
- b. Write the general structure of a PLA. Write the logic diagram of a general $n \times p \times m$ PLA. How are PLAs characterised? (6)
- c. Write the logic diagram, Truth table, and the logic symbol of a positive-edge-triggered T flip-flop. (3)
- Q.9** a. Design a combinational circuit that accepts a 3-bit number as input and generates an output binary number equal to the square of the input number using ROM. (9)
- b. What is a counter? How are counters broadly classified? Write at least two lines on each such classification. (7)