

Roll No.

Total No. of Questions : 09]

May 2007

[Total No. of Pages : 02

J-6018[S-507/18]

[2957]

B.Tech. (Semester - 3rd)

ELECTRONIC DEVICES AND CIRCUITS (EC - 201)



Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 × 2 = 20)

- a) What is the relation between the transition capacitance and reverse bias voltage in a p-n diode?
- b) A BJT with $\beta = 49$ and $I_{CO} = I_{CBO} = 1\mu A$ and $I_B = 10\mu A$. Calculate I_C ?
- c) Why CE configuration is preferred for cascaded amplifiers?
- d) What is thermal runaway?
- e) What are the requirements of a good biasing circuit?
- f) What are the advantages of voltage series feedback topology?
- g) Compare the performance of FET with MOSFET.
- h) State the working principle of a photodiode.
- i) Explain harmonic distortion in amplifiers.
- j) Why it is advisable to express amplifier gain in dB.

Section - B

(4 × 5 = 20)

Q2) Draw the practical circuit of complementary symmetry push-pull amplifier and explain its working.

Q3) In the fixed-bias circuit of a transistor, $V_{CC} = 15V$, $R_B = 300 k\Omega$, $R_E = 2 k\Omega$. If $\beta = 100$, $I_{CO} = 20 nA$ and $V_{BE} = 0.7V$. Find the stability factor of Q-point with respect to I_{CO} .

Q4) Explain how an FET is used as a VVR.

P.T.O.


Q5) Draw two stages of RC-coupled, direct-coupled and transformer-coupled amplifiers and make a chart showing the comparison of three coupling schemes.

Q6) The open-loop gain of an amplifier is -200. A voltage series negative feedback is used with a feedback ratio of -0.02. The input and output impedances of the amplifier are $2\text{k}\Omega$ and $40\text{k}\Omega$ respectively in the absence of feedback. Determine the closed-loop gain, input and output impedances when the feedback circuit is completed.

Section - C

(2 × 10 = 20)

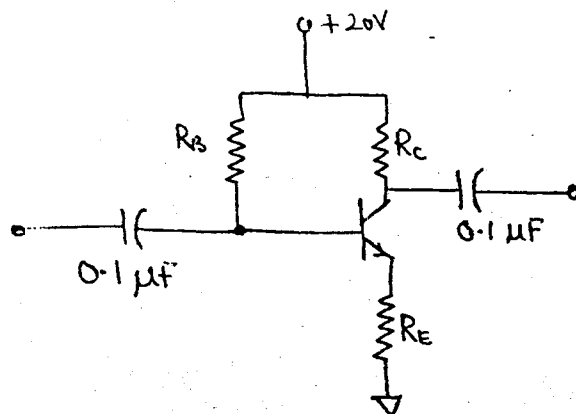Q7) In a small-signal amplifier shown below, $h_{fe} = 100$, $h_{ie} = 560\ \Omega$, $R_C = 2\text{ k}\Omega$, $R_E = 1\text{ k}\Omega$, $R_B = 600\text{ k}\Omega$, h_{re} and h_{oe} are negligible.



- Draw the h-parameter equivalent circuit for the amplifier. Calculate the input and output impedances and the voltage gain.
- Give the DC load line of the circuit and find Q-point.

Q8) (a) Draw the circuit of Wein bridge oscillator using op-amps. Explain its working principle. What is its frequency of oscillations and β requirement?
 (b) A certain Colpitt oscillator uses a tank circuit with $L = 20\text{ mH}$, $C_1 = 200\text{ pF}$ and $C_2 = 300\text{ pF}$. Calculate the frequency of oscillations.

Q9) (a) Draw the block diagram of regulated power supply and explain the role of each block.
 (b) Draw the circuit of a Class-A direct-coupled power amplifier. Show that the dissipation in the transistor is maximum under quiescent conditions. Obtain the expression for maximum efficiency of the circuit.

