


(3 Hours)

[Total Marks : 100

- N.B.** (1) Question No. 1 is compulsory.
 (2) Answer any four out of remaining six questions.
 (3) Assume any suitable data wherever required.


1. (a) Determine the Currents I_1, I_2 and I_{D2} for the following network :—

5

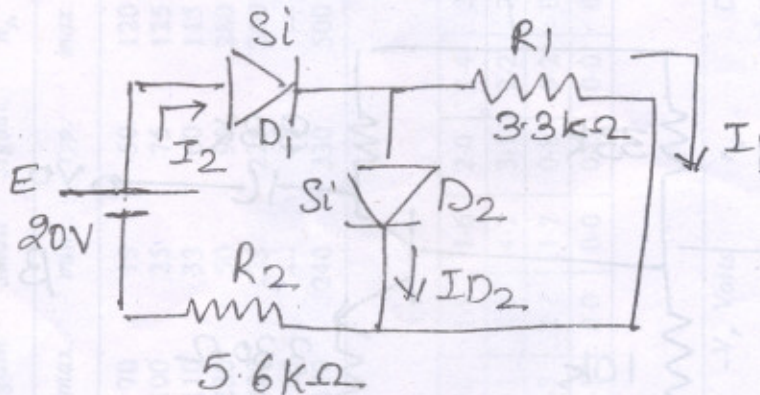

(b) Determine the dc bias Voltage V_{CE} and the current I_C for the following configuration :—

5

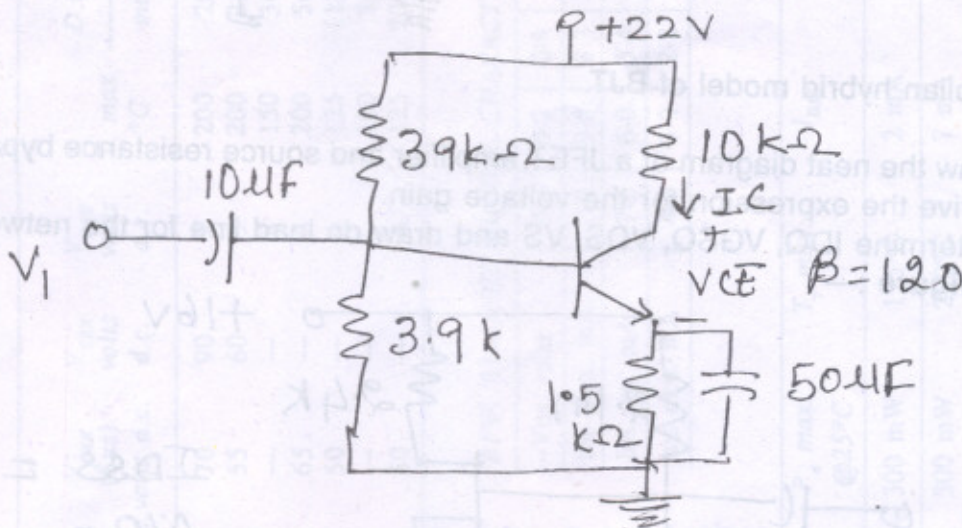

- (c) Derive the condition for zero temperature drift biasing of FET. 5
 (d) What is the maximum reverse voltage (PIV) across a diode in :— 5
 (i) HWR
 (ii) FWR with center tapped transformer
 (iii) Bridge type rectifier.

2. (a) Design a Single stage BJT CE Amplifier for the following requirements :—

15

$A_v \geq 100$, $Z_i > 3K \Omega$, $V_{cc} = 18 V$.

(b) Determine A_v , Z_i and Z_o for designed circuit.


5

2. (a) Design a Single stage BJT CE Amplifier for the following requirements :— 15
 $A_v \geq 100$, $Z_i > 3K \Omega$, $V_{cc} = 18 V$.
- (b) Determine A_v , Z_i and Z_o for designed circuit. 5
3. (a) Explain the operation of fullwave rectifier and draw the o/p waveform for $V_L dc$ 10
and $I_L dc$.
- (b) Derive an Expression for ripple factor for capacitor filter with center tapped Full 10
wave rectifier.
- If a circuit of fullwave center tapped rectifier with capacitor filter employs a load $R_L = 100 \Omega$ and $C = 1050 \mu F$. Calculate the ripple factor.

[TURN OVER

4. (a) For the circuit shown in figure determine :—

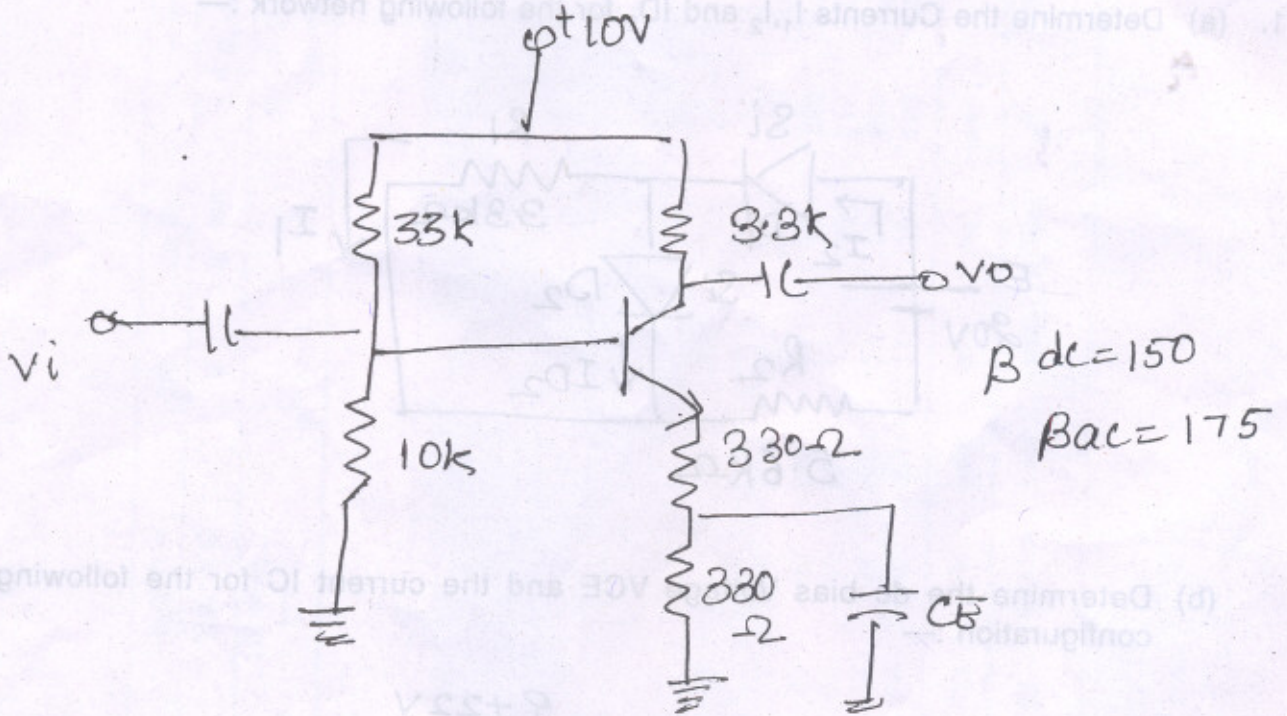- (i) Operating point
- (ii) Voltage gain
- (iii) Input impedance
- (iv) What will be Voltage without CE ?
- (v) What will be i/p impedance without CE ?



(b) Explain hybrid model of BJT.


5

5. (a) Draw the neat diagram of a JFET amplifier and source resistance bypassed and derive the expression for the voltage gain.

10

(b) Determine I_{DQ} , V_{GSQ} , V_{DS} , V_S and draw dc load line for the network shown in figure :—

10

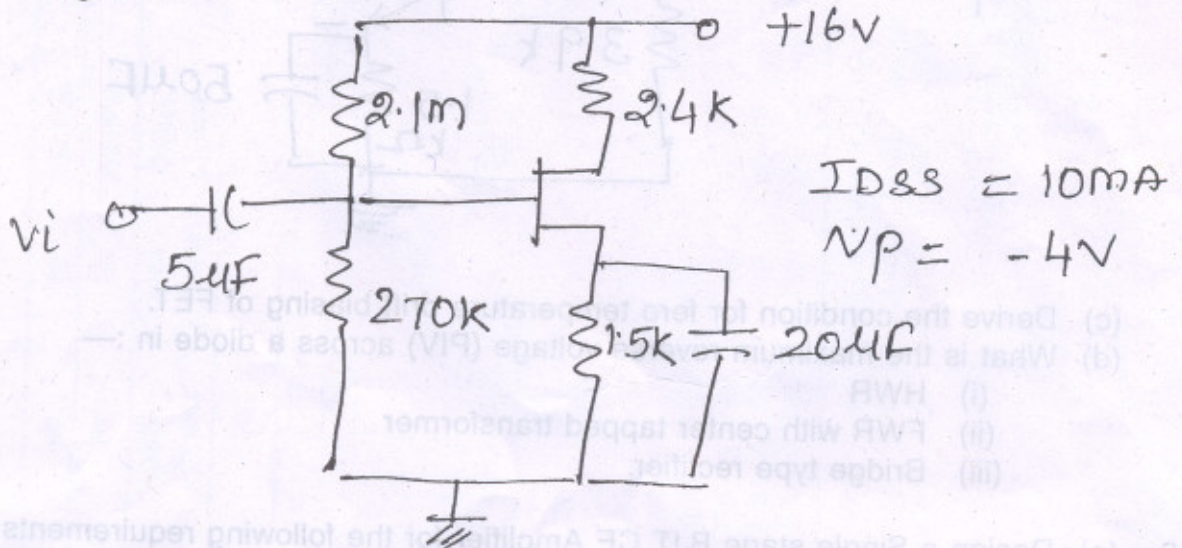

6. (a) Explain Construction, Working principle and characteristic of D Mosfet. **10**
- (b) Explain different biasing techniques for E MOSFET. **5**
- (c) Compare MOSFET and FET. **5**
7. Write short notes any **three** of the following :— **20**
- (a) Voltage multiplier

DBEC DATA SHEET

Transistor type	P_{dmax}	I_{cmax}	$V_{CE}^{(sat)}$	V_{CBO}	V_{CEO}	V_{CER}	V_{CEX}	V_{BEO}	T_j max	D.C. current	gain	Small Signal	h_{fe}	V_{BE}	θ_{jc}		
	@ 25°C	@ 25°C	volts	volts	(SUS)	(SUS)	volts	volts								°C	min
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—

Transistor type	h_{ie}	h_{oe}	h_{re}	θ_{ja}
BC 147A	2.7 K Ω	18 μ $\bar{\Omega}$	1.5×10^{-4}	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ $\bar{\Omega}$	3.2×10^{-4}	—
BC 147B	4.5 K Ω	30 μ $\bar{\Omega}$	2×10^{-4}	0.4°C/mw
ECN 100	500 Ω	—	—	—
ECN 149	250 Ω	—	—	—
ECN 055	100 Ω	—	—	—
2N 3055	25 Ω	—	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I _{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I _{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I _{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V_{DS} max.	V_{DG} max.	V_{GS} max.	P_d max.	T_j max.	I_{DSS}	g_{mo}	$-V_p$ Volts	r_d	Derate	θ_{jc}
	Volts	Volts	Volts	@25°C			(typical)			above 25°C	
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ $\bar{\Omega}$	6	50 K Ω	2 mW/°C	0.59°C
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ $\bar{\Omega}$	2.5	50 K Ω	—	0.59°C