 


- N. B. : (1) Question No. 1 is compulsory.
 (2) Answer any four out of remaining six questions.
 (3) Assume any suitable data, wherever required.
 (4) Answer to questions should be grouped and written together.


1. Solve any four :—

20

(a) Sketch the o/p waveform for shown figure.



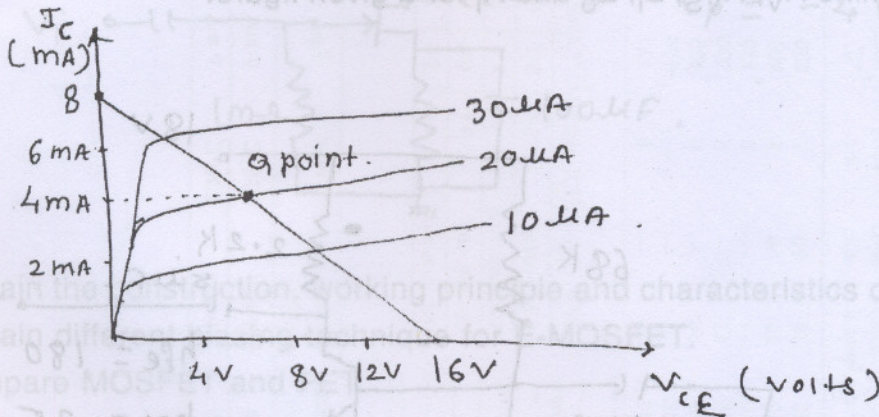(b) The d.c. load line of fixed bias is shown in figure. Determine the required values of V_{CC} , R_C and R_B for a fixed-bias circuit.



- (c) What is maximum reverse voltage (PIV) across a diode in
 (i) HWR (ii) a FWR with center tapped transformer (iii) Bridge type rectifier ?
 (d) Derive the condition for zero temp. drift biasing of FET.
 (e) Which biasing method can not be used for D-MOSFET and Why ?

2. (a) Design single stage BJT CE Amplifier for the following requirements.

15


$A_v \geq 100$, $Z_i > 3K\Omega$, $V_{CC} = 18V$

(b) Determine A_v , Z_i and Z_o for designed circuit.


5

3. (a) Explain the operation of fullwave rectifier and draw the output waveforms for V_{Ldc} and I_{Ldc} . 10
 (b) Design for a full wave rectifier, an L type LC filter which gives a dc output voltage of 10V at a load current of 100 mA. The allowable ripple factor is 0.02. 10

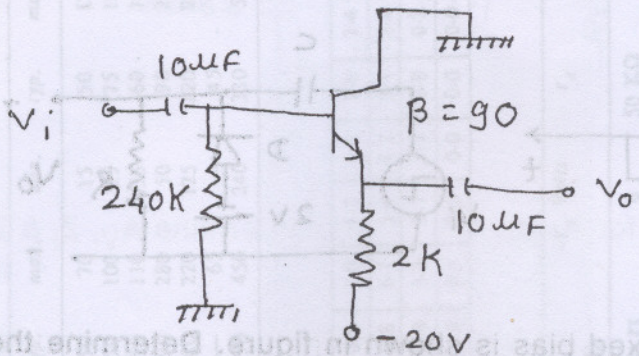
4. (a) Determine I_B , I_C , V_{CEQ} , V_E and V_B for a given network. 10



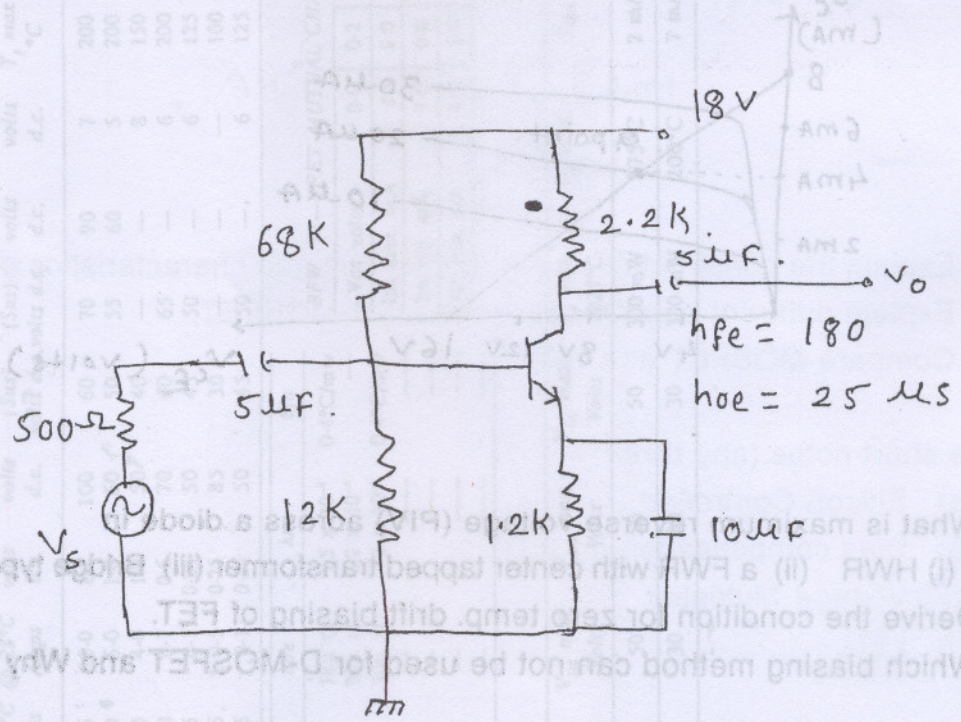
- (b) Determine A_V , A_{VS} , Z_i , Z_o and A_I for a given figure. 10



 5. (a) Determine I_{DQ} , V_{GSQ} , V_{DS} , V_S and draw dc load line for the network shown in figure. 10



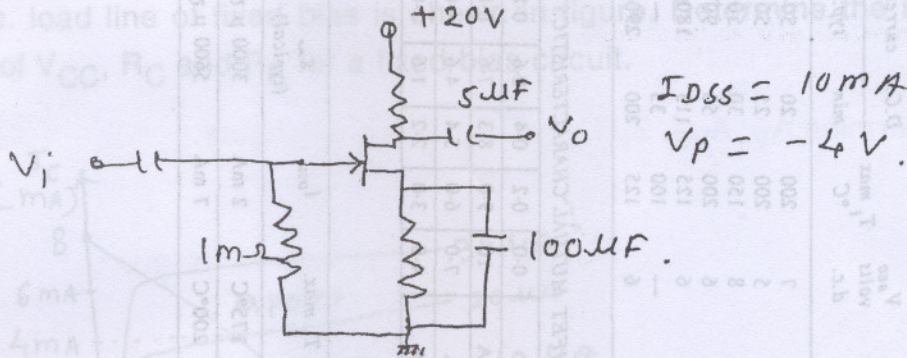- (b) Derive the equations for A_V , Z_i and Z_o and determine A_V , Z_i & Z_o for a given network. 10



6. (a) Explain the construction, working principle and characteristics of D-MOSFET. 10
 (b) Explain different biasing technique for E-MOSFET. 5
 (c) Compare MOSFET and FET. 5
7. Write short notes (any three) :— 20
 (a) Silicon Controlled Rectifier
 (b) Bias compensation for BJT
 (c) Voltage Multiplier
 (d) LED.

DBEC DATA SHEET

Transistor type	P_{dmax}	I_{cmax}	$V_{CE}^{(sat)}$	V_{CE0}	V_{CE0}	V_{CER}	V_{CEX}	V_{BE0}	T_j max	D.C. current gain			Small Signal	h_{fe}	V_{BE} max.	θ_{jc}	Derate above 25°C	
	@ 25°C Watts	@ 25°C Amps	volts d.c.	volts d.c.	(Sus) volts d.c.	(Sus) volts d.c.	volts d.c.	volts d.c.		$^{\circ}C$	min	typ.	max.					min.
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35	0.05
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—	—
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—	—

Transistor type	h_{ie}	h_{oe}	h_{re}	θ_{ja}
BC 147A	2.7 K Ω	18 μ \bar{U}	1.5×10^{-4}	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ \bar{U}	3.2×10^{-4}	—
BC 147B	4.5 K Ω	30 μ \bar{U}	2×10^{-4}	0.4°C/mw
ECN 100	50 Ω	—	—	—
ECN 149	15 Ω	—	—	—
ECN 055	12 Ω	—	—	—
2N 3055	6 Ω	—	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

$-V_{GS}$ volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I_{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I_{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I_{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V_{DS} max. Volts	V_{DC} max. Volts	V_{GS} max. Volts	P_d max. @25°C	T_j max.	I_{OSS}	g_{m0} (typical)	$-V_p$ Volts	r_d	Derate above 25°C	θ_{jc}
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ \bar{U}	6	50 K Ω	2 mW/ $^{\circ}C$	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ \bar{U}	2.5	50 K Ω	—	0.59°C/mW