

Roll No.

13

Total No. of Questions : 09]

[Total No. of Pages : 03

J-1451 [6410 A]

[2126]

B.Tech. (Semester - 5th)

PULSE AND DIGITAL SWITCHING CIRCUITS (EC - 309)

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:



- 1) Section - A is **compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 x 2 = 20)

- a) What do you understand by an attenuator?
- b) When does a high pass filter circuit acts as a differentiator?
- c) Differentiate between perfect compensation, under compensation and over compensation.
- d) What do you mean by non-regeneration comparator? Give an example.
- e) What is the difference between clipping and clamping?
- f) Define, (i) storage time of diode, (ii) transition time of diode.
- g) Define critical, over and under damping in uncompensated wide band amplifier.
- h) Why monostable multivibrator is called a delay circuit.
- i) Elaborate low frequency compensation in amplifiers.
- j) What do you mean by distributed amplifier?

Section - B

(4 x 5 = 20)


Q2) What is low pass RC circuit? Derive an expression of output voltage for square wave input and draw input-output characteristics of this circuit.

P.T.O.

Q3) Discuss in details transistor as a switch and what are the parameters taken into consideration to bias the transistor.

Q4) An ideal 1 μ sec pulse from a pulse generator is fed to an amplifier. Calculate and plot the output waveform under the following condition. The upper 3 dB frequency is: (a) 10 MHz and, (b) 0.1 MHz. Rise time of capacitor = $2.2 RC$.

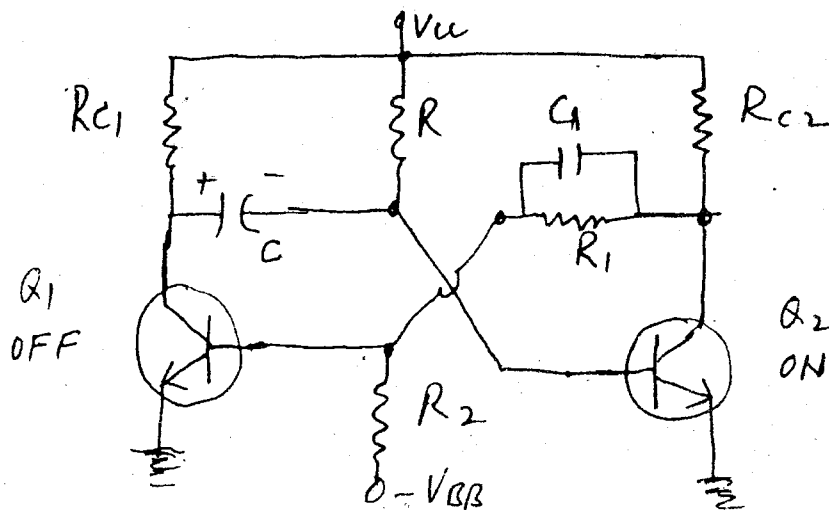Q5) Design a collector coupled one shot multivibrator circuit using n-p-n transistors. Neglect I_{CBO} and junction voltages of the transistor in saturation. Let h_{fe} (min.) = 20. In stable state, the OFF transistor has $V_{BE} = -1$ V. The ON transistor has base current I_B which is 50% in excess of the $I_{B(min)}$ value. $V_{CC} = 8$ V, $I_C(sat.) = 2$ mA, delay time = 2500 μ sec. Chosen $R_1 = R_2$. $I_{B2(actual)} = 1.5 I_{B2(min)}$.



Q6) What do you mean by a clipper? Discuss in details diode as a clipper.

Section - C

(2 x 10 = 20)

Q7) Explain the working of a bistable multivibrator with the help of a neat circuit diagram and waveforms. Derive an expression for the frequency of this circuit.

Q8) (a) For a common emitter circuit, $V_{CC} = 15$ V, $R_C = 1.5$ k Ω and $I_B = 0.3$ mA.

(i) Determine the value of h_{fe} (min.) for saturation to occur.

(ii) If R_C is changed to 500 Ω , will the transistor be saturated?

(b) What is a Schmitt triggering? Explain the working of a Schmitt trigger with the help of a neat circuit diagram and waveforms.

- Q9) (a) Design a diode clamper circuit to restore the bottom peaks of the input signal to zero level. Use a silicon diode with forward resistance, $R_f = 50 \Omega$ and reverse resistance, $R_r = 400 \text{ k}\Omega$. The frequency of the input voltage signal is 5 kHz. Assume $RC = 20 \text{ T}$.
- (b) How frequency response of an amplifier varies with low and high frequency signals. Discuss step response of an amplifier.

