

(Sem III) (Rev) Dec. 01
Electrical Network Analysis and Synthesis

68-07.

(REVISED COURSE)
(3 Hours) 51105

CD-6714

[Total Marks : 100]

Question No. 1 is compulsory

Attempt any four out of the remaining six questions.

Assume suitable data if required.

Figures to the right indicate full marks.


Attempt the following questions

Draw the graph from given incidence matrix and calculate total number of possible trees.


$$A = \begin{vmatrix} 1 & 0 & 0 & 0 & 1 & 1 \\ -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & -1 \end{vmatrix} \quad 4$$

Write a short note on source shifting and source transformation. 4

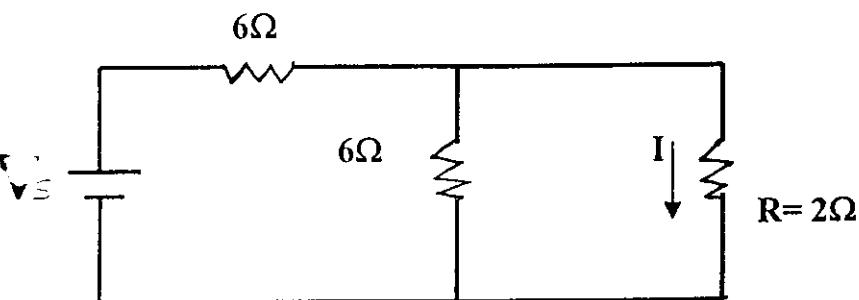Current in 2Ω resistor is $I = 3A$. If R is changed to 3Ω , find new value of I 4



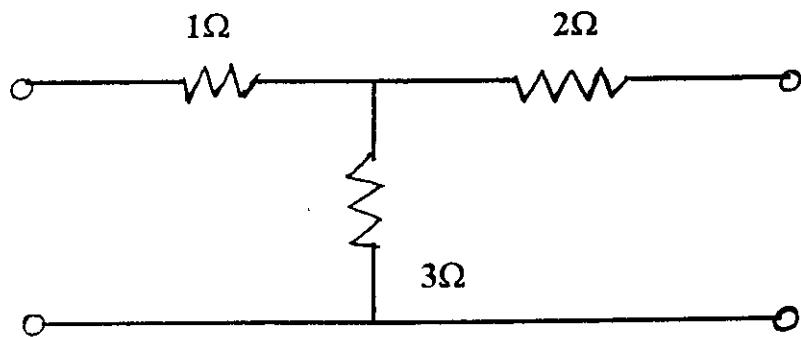Determine parameter Z_{22} and A for the network shown. 4




Write short note on initial condition and its significance. 4

[TURN OVER]


Con/5468-CD-6714-07.

2

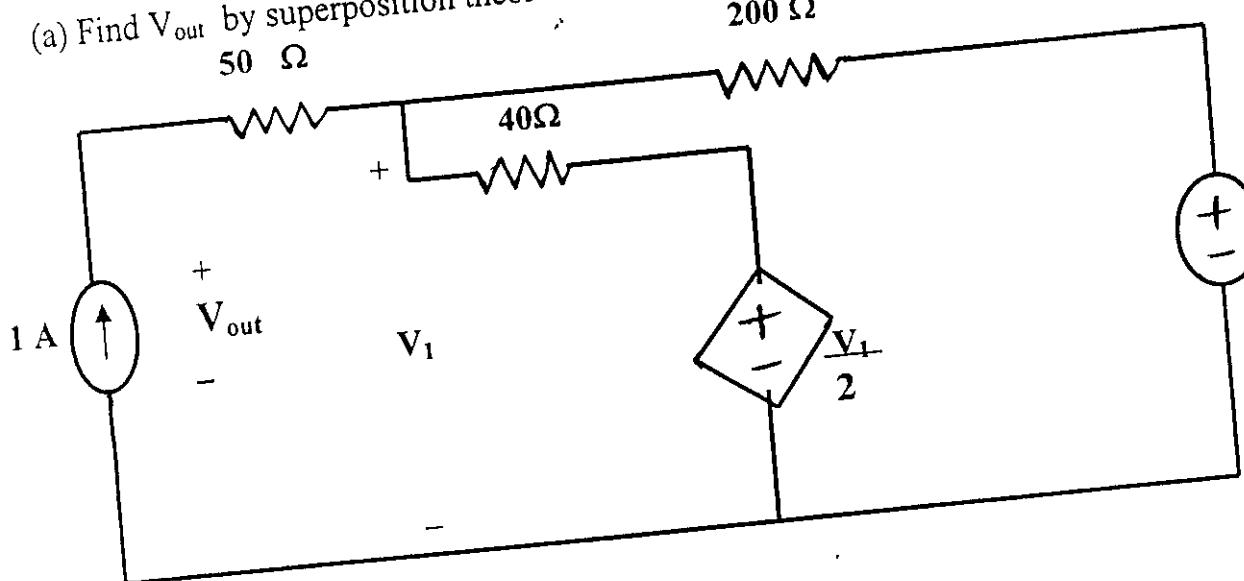
- 2 (a) Find V_{out} by superposition theorem.
 50Ω



- (b) Find I_2 by mesh analysis.

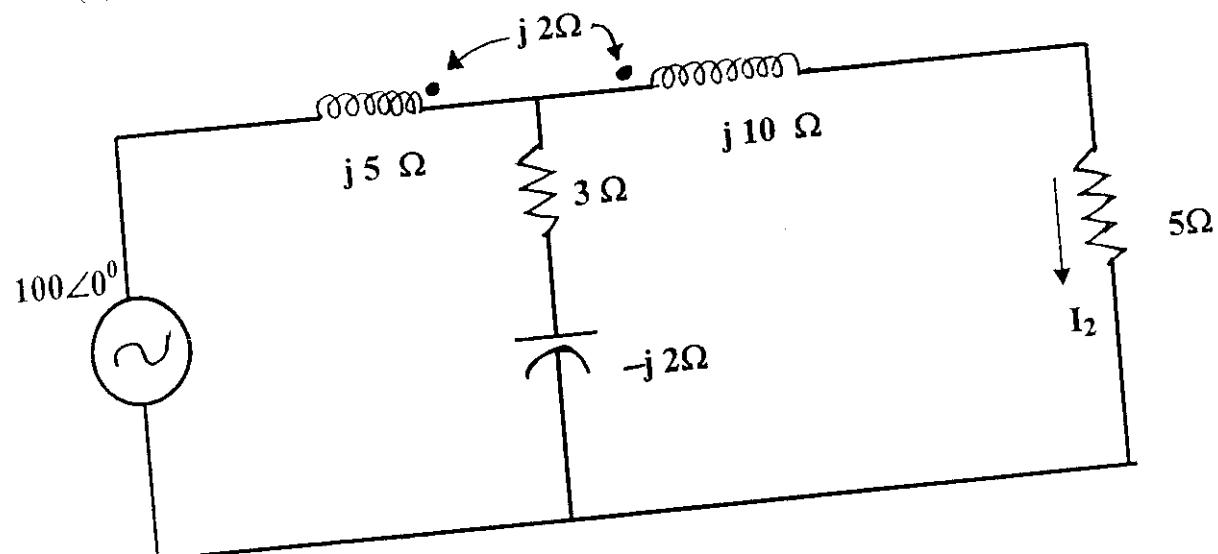


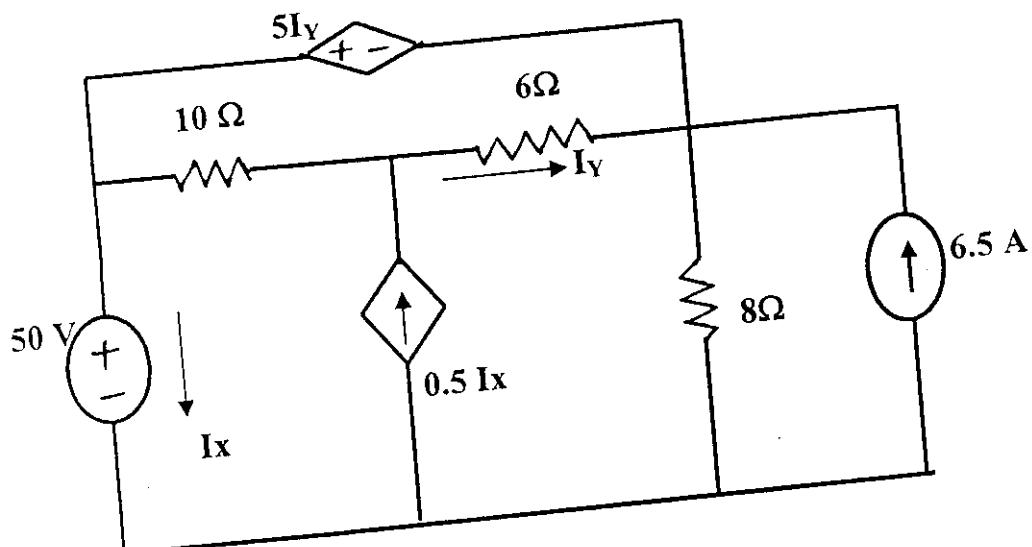- 3 (a) Use mesh analysis and find all branch currents.




Switch S is opened at $t = 0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$

10

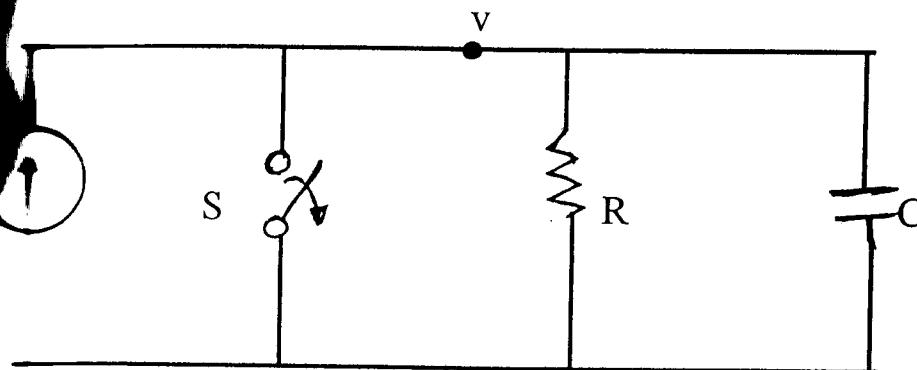

- 4 (a) Find the transmission parameter for the two-port network shown.

10

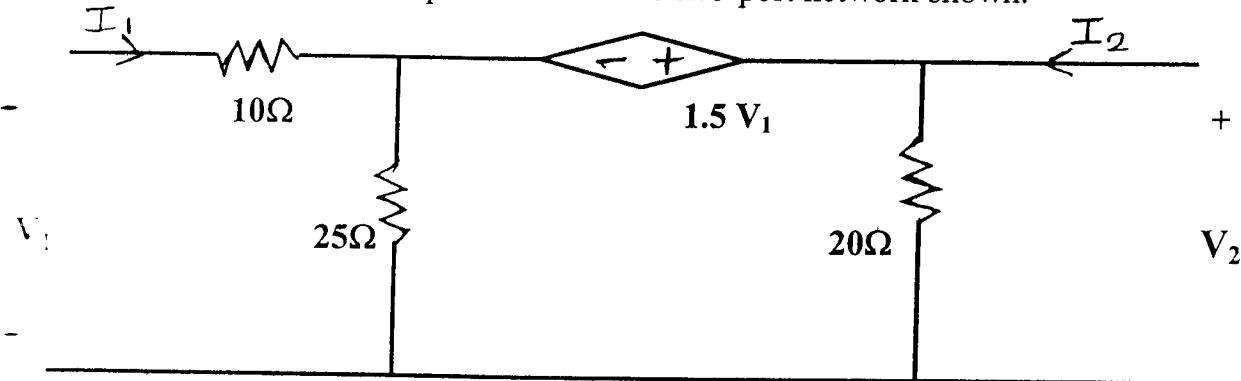

5Ω

- b) The Z parameter of a two port network are $Z_{11} = 20 \Omega$, $Z_{22} = 30 \Omega$, $Z_{21} = Z_{12} = 10 \Omega$. Find Y and ABCD parameter of the network. Also find its equivalent T network

10

- 5 (a) Test whether following functions are positive real or not.

10

$$\text{i) } \frac{S+2}{S^2 + 3S + 2} \quad \text{ii) } \frac{S^2 + 6S + 2}{S^2 + 3S + 5}$$

$$\text{b) } Y(S) = \frac{(S+2)(S+5)}{S(S+4)(S+6)} \text{ synthesize using Cauer-I and Cauer-II form.}$$


10

- (a) Define and with suitable example differentiate between


10

- Tree and Cotree
- f-cutset matrix and Tieset matrix
- Planer and nonplaner graph.

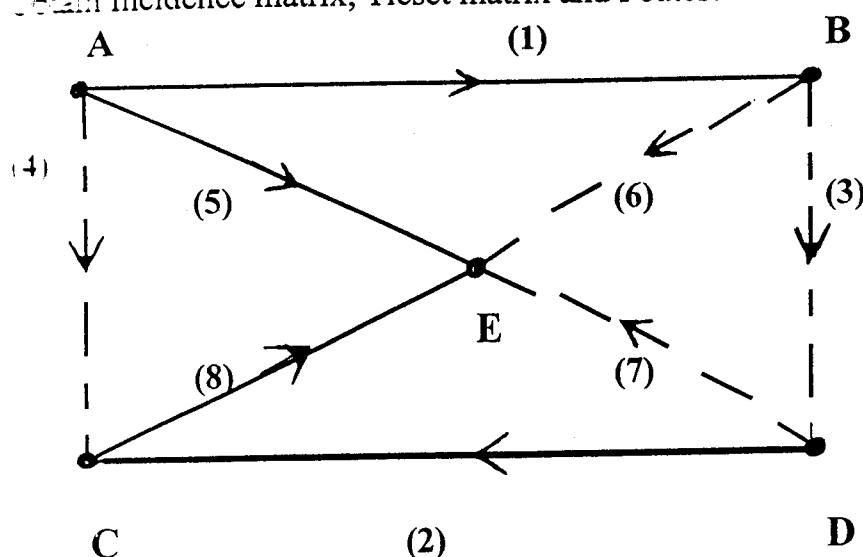6. Obtain Incidence matrix, Tieset matrix and f-cutset matrix for the graph shown.



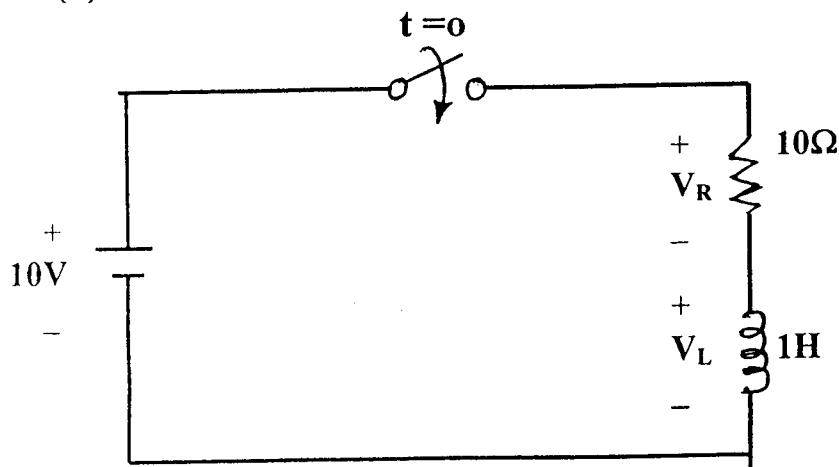7. (a) For a series RL circuit, a constant voltage is applied at $t=0$. At what time does $V_R = V_L$?



- (b) In the network shown the switch is opened at $t = 0$ when steady state condition has been reached previously. Find $i(t)$ for $t > 0$ for open switch position. Use Laplace method.

