

Code No: R5210504

II B.Tech I Semester(R05) Supplementary Examinations, November 2010

DIGITAL LOGIC DESIGN

(Common to Computer Science & Engineering, Information Technology and Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code.
 - The binary numbers listed have a sign bit in the left most position and , if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [8+8]
 - $101011 + 111001$
 - $001111 + 110010$
 - $111001 - 011010$
 - $101111 - 100110$.
- Write short notes about the various digital logic families.
 - Obtain the complement of the following Boolean expressions.
 - $AB + A(B + C) + B'(B + D)$
 - $A + B + A'B'C$.
 - Obtain the dual of the following Boolean expressions. [8+4+4]
 - $A'B + A'BC' + A'BCD + A'BC'D'E$
 - $ABEF + ABE'F' + A'B'EF$.
- Construct K-map for the following expression and obtain minimal SOP expression. Implement the function with 2-level NAND -NAND form.
 $f(A, B, C, D) = (A + C + D)(A + B + \overline{D})(\overline{A} + B + \overline{C})(\overline{A} + B + \overline{D})(\overline{A} + B + \overline{D})$
 - Implement the following Boolean function F using the two - level form: [8+8]
 - NAND-AND
 - AND-NOR $F(A, B, C, D) = \Sigma 0, 1, 2, 3, 4, 8, 9, 12$
- Implement 64×1 multiplexer with four 16×1 and one 4×1 multiplexer. (Use only block diagram).
 - A combinational logic circuit is defined by the following Boolean functions.
 $F_1 = \overline{ABC} + AC$
 $F_2 = \overline{ABC} + \overline{AB}$
 $F_3 = \overline{ABC} + AB$
 Design the circuit with a decoder and external gates. [8+8]
- Draw the circuit diagram of positive edge triggered D- flip-flop with NAND gates and explain its operation using truth table.
 - Write an HDL behavioural description of a D- flip-flop and D- flip-flop with synchronous preset and clear. [8+8]
- Design a 4-bit ring counter using T- flip flops and draw the circuit diagram and timing diagrams.
 - Draw the block diagram and explain the operation of serial transfer between two shift registers and draw its timing diagram. [8+8]
- Give the HDL code for a memory read , write operations if the memory size is 64 words of 4 bits each. Also explain the code
 - Obtain the 15-bit Hamming code for the 11-bit data word 11001001010. [8+8]
- Explain the difference between asynchronous and synchronous sequential circuits.
 - Define fundamental-mode operation.
 - Explain the difference between stable and unstable states.
 - What is the difference between an internal state and a total state.
 - Explain critical and non critical races with the help of examples. [8+8]
