

Code :R7210504

II B.Tech I Semester (R07) Supplementary Examinations, November 2010
DIGITAL LOGIC DESIGN

(Computer Science & Engineering, Information Technology, Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
All questions carry equal marks

1. (a) What is the gray code equivalent of the Hex Number 3A7.
 (b) Find the biquinary number code for the decimal numbers from 0 to 9.
 (c) Find 9's complement $(25.639)_{10}$.
 (d) Find $(72532 - 03250)$ using 9's complement.
2. (a) Prove that if $w'x + yz' = 0$, then
 $Wx + y'(w' + z') = wx + xz + x'z' + w'y'z$
 (b) Factor to obtain a Product of Sums (simplify where possible)
 $i) BCD + C'D' + B'C'D + CD$
 (c) Consider the expression $Z = (A \text{ ex-or } B \text{ ex-or } C \text{ ex-or } D \text{ ex-or } \dots)$. Show that $Z=1$ if an odd number of variables are 1 and that $Z=0$ if an even number of variables are 1.
3. (a) Implement Half adder using 4 NAND gates.
 (b) Implement full subtractor using NAND gates only.
4. Design 4 digit BCD adder using 7483 adders.
5. Explain about Analysis of Clocked Sequential Circuits in Detail?
6. Explain about 4-bit synchronous binary counter?
7. Explain about:
 - (a) Write and Read operations
 - (b) Memory description in HDL
8. Define Latch Excitation table? Explain its implementation with an Example?