

**Code: D-22**  
**Time: 3 Hours**

**Subject: INDUSTRIAL ELECTRONICS**  
**Max. Marks: 100**

**NOTE: There are 11 Questions in all.**

- **Question 1 is compulsory and carries 16 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.**
  - **Answer any THREE Questions each from Part I and Part II. Each of these questions carries 14 marks.**
  - **Any required data not explicitly given, may be suitably assumed and stated.**
- 

**Q.1 Choose the correct or best alternative in the following: (2x8)**

a. Thyristor is a

- (A) Three terminal, three layer device.
- (B) Three terminal three junction four layer device.
- (C) Simple diode in forward as well as reverse mode.
- (D) Two junctions, three terminals, four-layer diode.

b. In R-firing circuit, the firing angle ranges from

- (A)  $0^\circ$  to  $180^\circ$
- (B)  $0^\circ$  to  $360^\circ$
- (C)  $0^\circ$  to  $90^\circ$
- (D)  $3^\circ$  to  $77^\circ$

c. In three phase full wave controlled rectifier

- (A) Each thyristor conducts for  $60^\circ$ .
- (B) Each thyristor conducts for  $120^\circ$ .
- (C) Conduction angle of thyristor depends upon firing angle.
- (D) Some thyristors conduct while others not.

d. In a series inverter

- (A) The R, L and C elements form an under damped circuit
- (B) The R, L and C elements have no role to play
- (C) Power supply may be short circuited
- (D) Highest frequency may be equal to resonant frequency.

e. For dielectric heating the supply requires

- (A) Low frequency
- (B) Very low frequency
- (C) High frequency
- (D) Very high frequency



**Answer any THREE Questions. Each question carries 14 marks.**

---

- Q.7** a. Draw the wave forms of a three-phase half-controlled bridge rectifier. Explain its operation with a circuit diagram. (8)
- b. Explain Jones chopper with a circuit diagram. (6)
- Q.8** a. Give some applications of choppers. (5)
- b. Explain the process of dielectric heating and give a few of its applications. (9)
- Q.9** Explain load and auxiliary commutation circuits of choppers. (14)
- Q.10** a. Explain thermal loss in dielectric heating. (6)
- b. With the help of a circuit diagram, explain the principle of induction heating. (8)
- Q.11** a. Explain the process of resistance welding and give some applications. (7)
- b. Enumerate the advantages of induction heating and give some applications. (7)