

Code: DE22

Time: 3 Hours

**DECEMBER 2008**

Subject: INDUSTRIAL ELECTRONICS

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or best alternative in the following:****(2x10)**

- Holding current
  - Is the same as latching current.
  - Is the minimum value of anode current below which SCR is turned OFF
  - Puts the limit on Max. Current, through the SCR.
  - Is the Maximum value of anode current, above which SCR is turned ON.
- In half wave controlled rectifier
  - One diode and one thyristor are required.
  - One thyristor is required.
  - Either a diode or a thyristor may be used.
  - Two thyristors are required.
- In a series inverter
  - Commutating elements and load are in series.
  - Commutating elements and thyristors are in series.
  - Capacitor may be in parallel with L but in series with load.
  - Capacitor may be in parallel with load.
- The power factor at the input terminals of a cycloconverter is generally
 

(A) Low and leading.	(B) Low and lagging.
(C) High and leading.	(D) High and lagging.
- In controlled heating circuits thyristors act as
 

(A) Rectifiers.	(B) Inverters.
(C) AC regulators.	(D) Choppers.
- A 1-phase fully controlled bridge converter, is fed by a voltage  $V_m \sin \omega t$ . The average and rms values of output voltages are
 

(A) $2V_m / \pi \cos \alpha$ and $V_m / \sqrt{2}$	(B) $V_m / \pi \cos \alpha$ and $V_m / \sqrt{2}$
(C) $2V_m / \pi \cos \alpha$ and $V_m$	(D) $V_m / \pi \cos \alpha$ and $\sqrt{2}V_m$

- g. A load commutated chopper circuit has  
 (A) 1 thyristor. (B) 2 thyristors  
 (C) 4 thyristors (D) 6 thyristors
- h. \_\_\_\_\_ method of heating is based on the transformer principle.  
 (A) Eddy-current. (B) Dielectric.  
 (C) Induction. (D) Resistance.
- i. For small objects the induction heating is done at a frequency of  
 (A) 10kHz (B) 50kHz  
 (C) 10MHz (D) 100kHz
- j. Induction heating requires  
 (A) AC input (B) High frequency AC input  
 (C) DC input (D) No input

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

- Q.2** a. Explain the principle of operation and characteristics of a thyristor. (8)
- b. Explain, resistance-triggering & RC- triggering circuit for a thyristor. (8)
- Q.3** Explain the different methods of turning on a thyristor. (16)
- Q.4** a. With the help of a circuit diagram and waveform, describe the operation of a single-phase fully controlled bridge circuit. (8)
- b. For a full wave controlled rectifier the firing angle  $\alpha = 60^\circ$ , input voltage  $v = 100 \sin 200t$ . Calculate  $V_{rms}$ ,  $V_{av}$  and form factor. (8)
- Q.5** a. Explain the circuit of a single-phase half wave converter with RL load and with free wheeling diode. Draw the waveforms at the output and across the diodes. (8)
- b. What are natural and forced turn off methods? Give examples. (8)

- Q.6** a. Draw the circuit of a 3-phase bridge inverter. Explain the operation for  $120^\circ$  conduction angle with the help of a waveform. (8)
- b. Explain the operation of series inverter. Give a few applications of series inverters. (8)
- Q.7** a. Explain how does a step up chopper work. (8)
- b. Explain load and auxiliary commutation circuits of choppers. (8)
- Q.8** a. Explain thermal loss in dielectric heating and give a few of its applications. (8)
- b. Explain why and how high frequency power source is used for Induction Heating. (8)
- Q.9** Write short notes on
- (i) Resistance welding. (8)
- (ii) Advantages of induction heating & its applications. (8)