

S.E. sem 3 (Rev.)  
Con. 5736-08. Etrx.

Digital system Design-I

12/12/08.

RC-8729**(REVISED COURSE)**

(3 Hours)


**[Total Marks : 100]**

- N.B.:** (1) Question no. 1 is **compulsory**.  
(2) Solve any **four** from remaining **six** questions.

 1. Answer the following questions :—

20

- Generate a 7 bit even parity hamming code for "1010".
- Simplify the following expression using Boolean theorems  
 $(AB+C+D)(\bar{C}+D)(\bar{C}+D+E)$
- Explain lockout condition with the help of 3 bit Ring counter.
- Draw a Karnaugh Map for the given circuit



2. (a) Implement the following function using NAND gates only—

8

$$F = \sum m(1, 2, 4, 7, 11, 13) + d(9, 15)$$

(b) Design a combinational Circuit for controlling panel light of satellite control room. The Light should go ON if :—

- The pressure in fuel and oxidizer tank is equal to or above the required minimum and there are 10 minutes or less for the satellite to lift off.

**Or**

- The pressure in fuel tank is below the required minimum but there are more than 10 minutes for the satellite to lift off.

**Or**

- The pressure in oxidizer tank is below the required minimum but there are more than 10 minutes for the satellite to lift off.

3. (a) Design a 4:1 MUX with active high enable input using NOR gates only.

10

(b) Using Quine McCluskey Simplification Method simplify

10

$$F = \sum m(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$$

4. (a) Design a 4-bit even parity generator and checker. Implement using one 8:1 MUX each.

10

(b) Design a 1 digit BCD adder using IC 7483 and explain the operation for  $(0101)_{BCD} + (1001)_{BCD}$ 


10

**[TURN OVER]**

Con. 5736-RC-8729-08.

2

 5. (a) What are reflective codes? Give suitable example and explain. 4
- (b) Define following parameters for CMOS logic family and give values :— 8
- Fan out
  - Propagation Delay
  - Noise Margin
  - Current Parameters.
- (c) Find the static hazard in the given circuit and modify it to eliminate the hazard— 8



6. (a) Design a synchronous 4 bit universal up/down counter. 10
- (b) Design a MOD 6 asynchronous counter and explain glitch problem. 10
7. (a) Generate "101" sequence by using shift register in SISO mode. Draw timing diagram. 10
- (b) Design XY Flip-Flop using JK Flip-Flop :— 10

X	Y	$Q_{n+1}$
0	0	$\bar{Q}_n$
0	1	$Q_n$
1	0	1
1	1	0