

**ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2007****ANALOG ELECTRONIC CIRCUIT****SEMESTER - 4**

Time : 3 Hours]


[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10
- i) Saturation region operation of a BJT implies
- a) base-emitter junction forward biased, base-collector junction reverse biased
 - b) base-emitter junction forward biased, base-collector junction forward biased
 - c) base-emitter junction reverse biased, base-collector junction reverse biased
 - d) none of these.
- ii) A differential amplifier has the differential gain of 100. If its CMRR = 240, then the common mode gain is
- a) 0.24
 - b) 0.417
 - c) 24000
 - d) 1.
- iii) In an amplifier, if conduction is during the cycle from 0° to 9° and again from 180° to 270°, the amplifier will be termed as
- a) Class A
 - b) Class B
 - c) Class C
 - d) Class AB.
- iv) Thermal runaway in a transistor biased in the active region is due to
- a) heating of the transistor
 - b) change in β which increases with temperature
 - c) base emitter voltage which decreases with rise in temperature
 - d) change in reverse collector saturation due to rise in temperature.




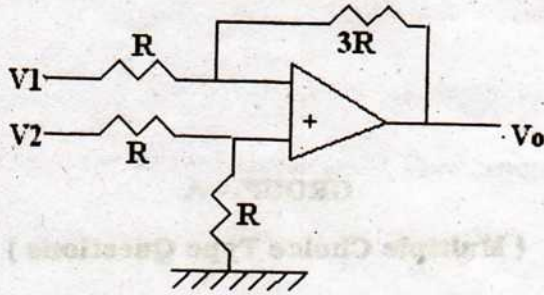v) The value of V_o is given for the following circuit by



- a) $-3 V_1 + 2 V_2$
- b) $-3 V_2$
- c) $1.5 V_2 - 2.55 V_1$
- d) $2 V_2 - 3 V_1$

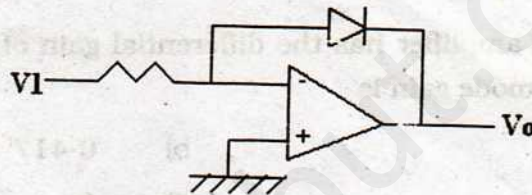vi) The circuit figure shown below uses an ideal Op-Amp. For small positive values of V_1 , the circuit works as



- a) a half-wave rectifier
- b) a differentiator
- c) a logarithmic amplifier
- d) an exponential amplifier.

vii) An instrumentation amplifier

- a) is a differential amplifier
- b) has a gain less than 1
- c) has very high output impedance
- d) has low CMRR.




- viii) The Q point in a voltage amplifier is selected in the middle of the active region because
- a) it gives better stability
 - b) the circuit needs a small d.c. voltage
 - c) the biasing circuit then needs less number of resistors
 - d) it gives a distortionless output.
- ix) A class B push-pull power amplifier has an a.c. output of 10 watts. The d.c. power drawn from the power supply under ideal condition is
- a) 10 watts
 - b) 12.75 watts
 - c) 15 watts
 - d) 20 watts.
- x) An ideal regulated power supply should have regulation which is
- a) maximum
 - b) 50%
 - c) zero
 - d) 75%.
- xi) Multivibrators
- a) generate square wave
 - b) convert sine to square wave
 - c) convert triangular to sine wave
 - d) convert triangular to square wave.
- xii) Can we use a VCO as a function generator ?
- a) Yes
 - b) No
 - c) Depends upon the kind of VCO
 - d) Cannot say.

**GROUP - B****(Short Answer Type Questions)**Answer any *three* of the following.

3 × 5 = 15

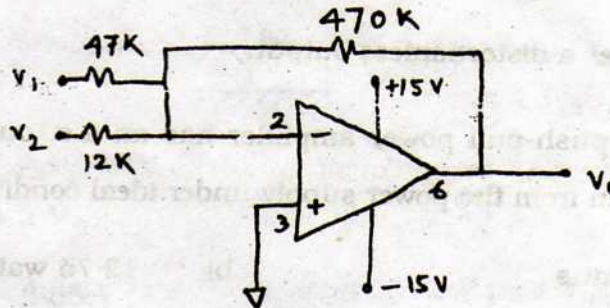2. Calculate the output voltage of the circuit, shown below where $V_1 = 40$ mV and $V_2 = 20$ mV. 5



3. What are the differences between series and shunt regulators ? Draw a circuit of a shunt regulator and explain its operation. 2 + 3
4. a) What do you mean by 'biasing' ?
 b) Draw and explain any one type of biasing arrangement and determine its stability factor. 1 + 4
5. Explain the differences between constant current bias and current mirror. 5
6. What is a multivibrator ? Explain the operation of a monostable multivibrator and draw the output voltage waveform. 1 + 4

GROUP - C**(Long Answer Type Questions)**Answer any *three* questions.

3 × 15 = 45

7. a) What is the significance of CMRR in differential amplifier ? 3
 b) With the circuit diagram, discuss the operation of an instrumentation amplifier and derive its gain equation. Discuss its merit and application. 12
8. a) Describe the function of an Op-Amp on (i) an inverter, (ii) an adder, (iii) an integrator (iv) a differentiator and (v) an amplifier. 10
 b) What are the desirable properties of an ideal Op-Amp ? 5



9. a) In what respects Class B Push-Pull amplifier configuration better than a Class A Push-Pull Amplifier ? What is major drawback of Class B operation and how is this remedied ? 2 + 3
- b) Prove that the maximum efficiency of class B amplifier is 78.5%. 7
- c) What is the function of tuned amplifier ? 3
10. a) Draw the circuit diagram of a voltage to current converter (grounded load) and explain its operation. 5
- b) Draw the circuit arrangement and explain the operation of a Schimdt trigger circuit. 5
- c) Give internal block arrangement of 555 and explain function of each block. 5
11. Write short notes on any *three* of the following : 3 × 5
- a) Logarithmic amplifier
- b) PLL
- c) Switched mode power supply
- d) Precision rectifier
- e) High frequency model of transistor.
-