

m/4/01/10

Roll No. ....

Total No. of Questions : 09]

[Total No. of Pages : 02

www.allsubjects4you.com  
B.Tech. (Sem. - 1<sup>st</sup>/2<sup>nd</sup>)

**BASIC ELECTRICAL & ELECTRONICS ENGINEERING**

**SUBJECT CODE : EE - 101 (2K4 & Onwards)**

**Paper ID : [A0117]**

[Note : Please fill subject code and paper ID on OMR]

**Time : 03 Hours**

**Maximum Marks : 60**

**Instruction to Candidates:**

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Five** questions from Section - B & C.
- 3) Select atleast **Two** questions from Section - B & C.

**Section - A**

**Q1)**


**(Marks : 2 Each)**

- a) Define Temp. coefficient of resistance & give its units.
- b) Define R.M.S. value of A.C.
- c) Give the relation between phase & line values of voltage & current for star connection.
- d) What is the working principle of D.C. motor.
- e) Give the working principle of moving iron instruments.
- f) Draw the static characteristics of thyristor.
- g) Convert 101011 into decimal system & octal system.
- h) Write the working principle of Thermistor & Thermocouple.
- i) State Faraday's laws of electromagnetic induction.
- j) Draw the symbolic representation of BJT and FET.

**Section - B**

**(Marks : 8 Each)**

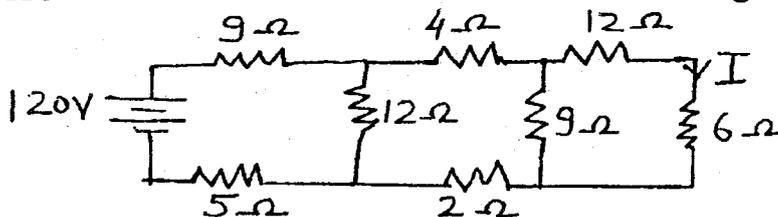**Q2)** State KCL and KVL. Find the current I in the following circuit using KVL.



J-749 [8129]

P.T.O.

**Q3)** Draw & explain the phasor diagram of RLC series circuit and give the condition for resonance in this circuit.

**Q4)** Explain the working principle & construction of three phase induction motor.

**Q5)** Explain the construction & working of induction type energy meter.

**Section - C**

**(Marks : 8 Each)**

**Q6)** What is LVDT. Explain its use for the measurement of displacement.

**Q7)** What is Zener Diode. Explain its use as voltage regulator.

**Q8)** Draw & explain the PIN diagram of IC 7400.

**Q9)** Draw the equivalent circuit & truth table of RS Flip-Flop.

**\* \* \***