

Lib

(3 Hours)

[Total Marks : 100

Electronic Devices & Circuits - II

N.B. : (1) Question Nos. 1 and 2 are compulsory. Answer any three questions from the remaining.

(2) Assume the missing data suitably.

2.30 to 5.30

(3) Draw neat, labeled diagrams wherever necessary.

1. Design a 2 stage RC Coupled Amplifier using BC 147 for the following data :- 20

$A_v = 1000, S_{ICO} \leq 8, F_L \leq 15\text{Hz}, V_{CC} = 16\text{V}.$

Find  $(V_o)_{max}, R_{in}, R_o$  and total current drawn from the supply.

Given :-  $h_{ie} = 2.7\text{K}\Omega, h_{oe} = 18\mu\text{r}, h_{fe} = 200, h_{re} = 1.5 \times 10^{-4}.$


Draw the diagram with their designed values.

2. (a) Find the upper, lower cut-off frequency, Bandwidth and gain-bandwidth product 12

for the circuit shown below. Sketch the frequency response. Given  $C_{be} = 35\text{pF}, C_{bc} = 5\text{pF}, C_{ce} = 1\text{pF}, C_{wi} = 5\text{pF}, C_{wo} = 8\text{pF}, r_o = \infty.$

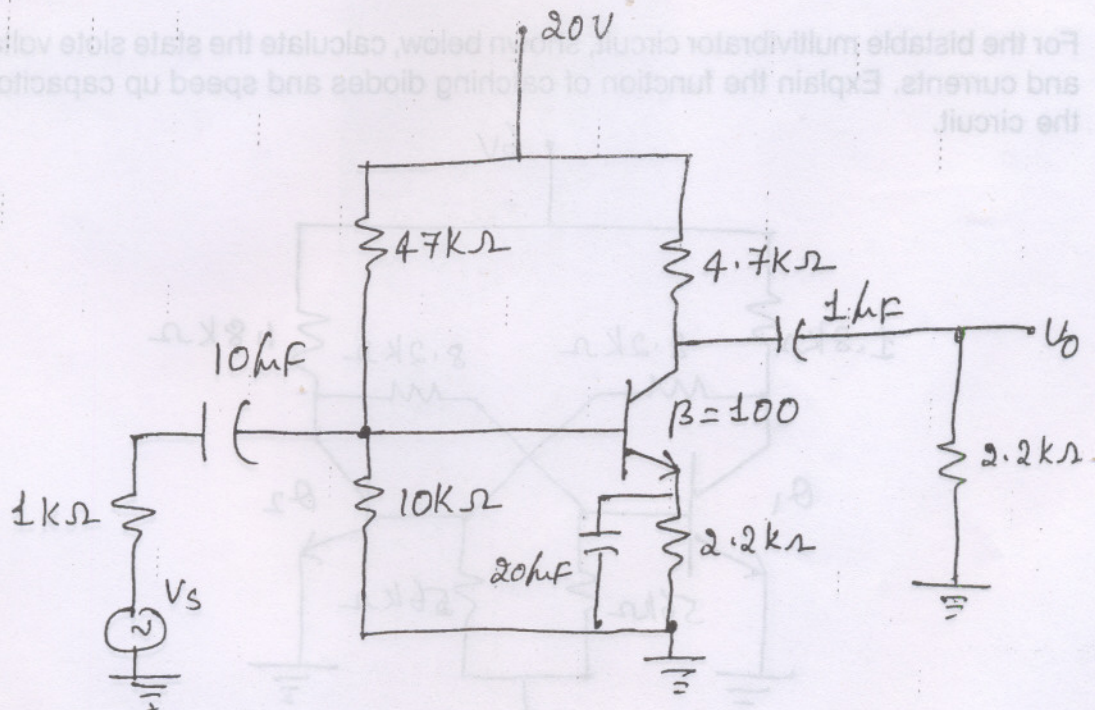(b) Design a class B power Amplifier with the following specifications. 8

Output power = 10 watts.  $R_L = 8\Omega, V_{CC} = 12\text{V}.$  Calculate the overall efficiency at the full load.




3. (a) With neat diagrams explain the various kinds of feedbacks and find their  $R_i, R_o, A_v$  and  $A_i.$  12

(b) Design a RC phase shift oscillator using FET, having  $g_m = 8000/\mu\text{r}, r_d = 40\text{K}\Omega$  to generate a signal of 1.5 KHz. 8


3. (a) With neat diagrams explain the various kinds of feedbacks and find their  $R_i$ ,  $R_o$ ,  $A_v$  and  $A_i$ . 12
- (b) Design a RC phase shift oscillator using FET, having  $g_m = 8000/\mu\text{S}$ ,  $r_d = 40\text{ K}\Omega$  to generate a signal of 1.5 KHz. 8
4. (a) Derive an expression for the small signal voltage gain of a dual input, single output differential amplifier with neat relevant diagrams. 12

[TURN OVER

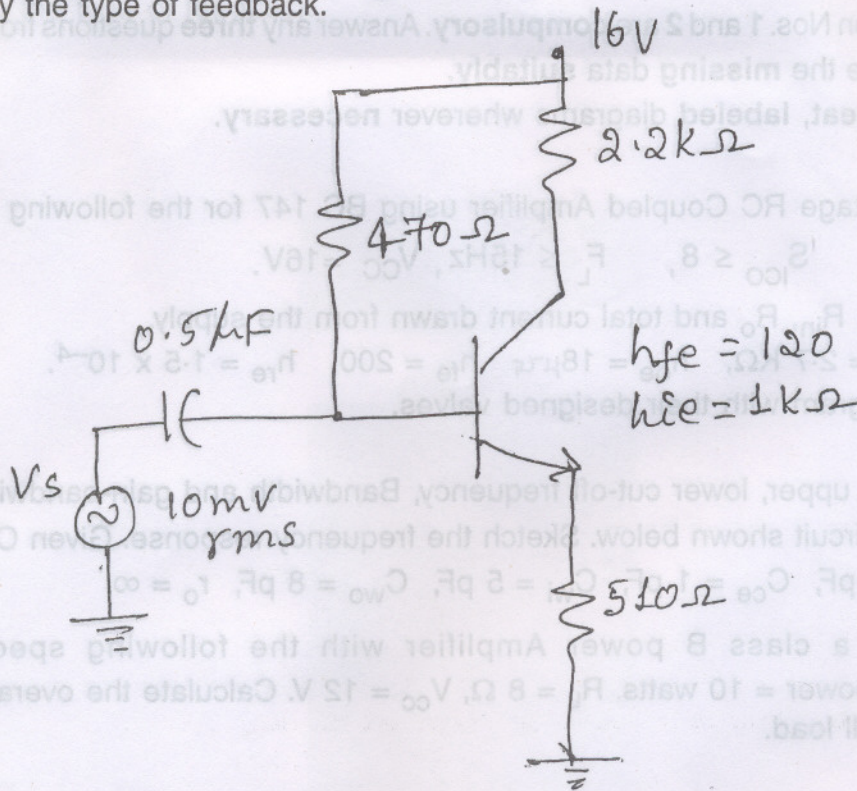- (b) Calculate the voltage gain of the following circuit with and without feedback. Identify the type of feedback. 8



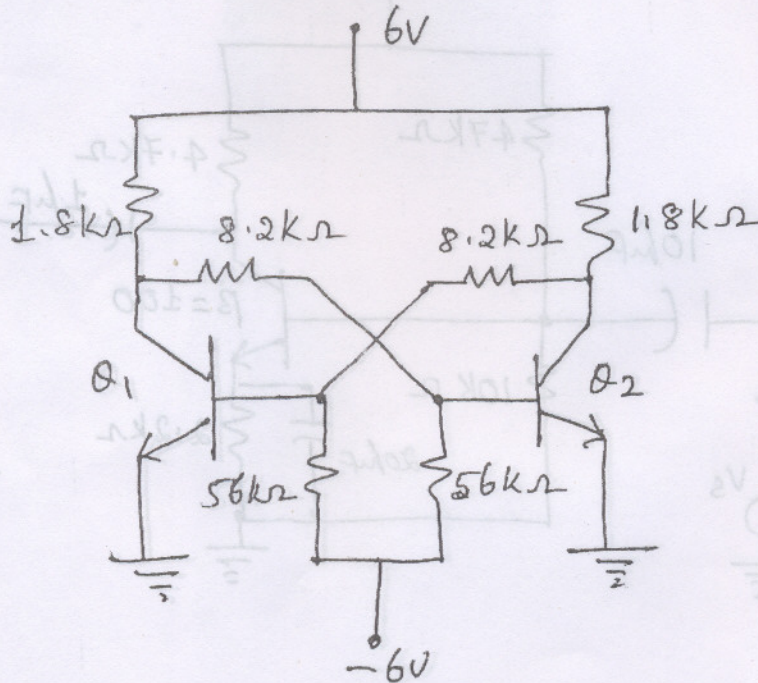5. (a) For the bistable multivibrator circuit, shown below, calculate the state voltages and currents. Explain the function of catching diodes and speed up capacitors in the circuit. 12



- (b) What is a heat sink? Why is it required for power amplifiers? Show the relationship between thermal and electrical analogy with a neat sketch. 8
6. (a) Derive an expression for the frequency of oscillation of a RC phase shift oscillator using FET. 8
- (b) Explain harmonic distortion and crossover distortion in power Amplifier. How are they overcome? 12

7. Write short notes on :-

20

(a) Class C amplifier

(b) Darlington pair

(c) Clapp oscillator

(d) Merits and demerits of negative feedback amplifier.

---