
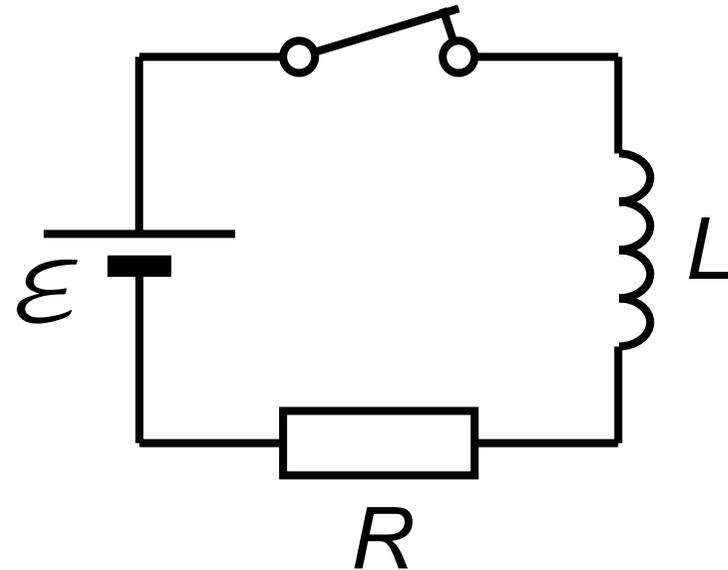


## 2. CAPACITANCE AND INDUCTANCE IN D.C. CIRCUITS
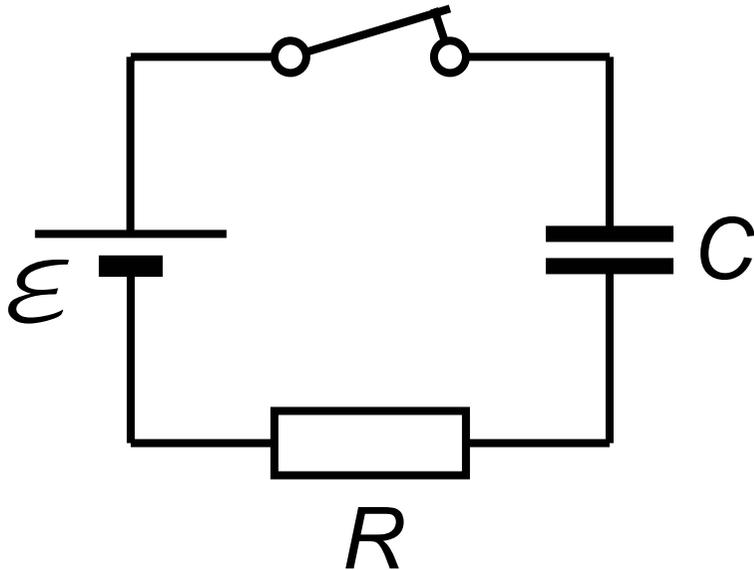
### Main things to learn

- Transients in  $CR$  and  $LR$  circuits
- Time constant




In a steady d.c. circuit:  $C$  is equivalent to the open circuit

$L$  is equivalent to the short circuit

Our aim is to study the **transient processes** in  $CR$  and  $LR$  circuits

What will be happening in such circuits just after the switch is turned on / off ?

## TRANSIENT IN A CR CIRCUIT

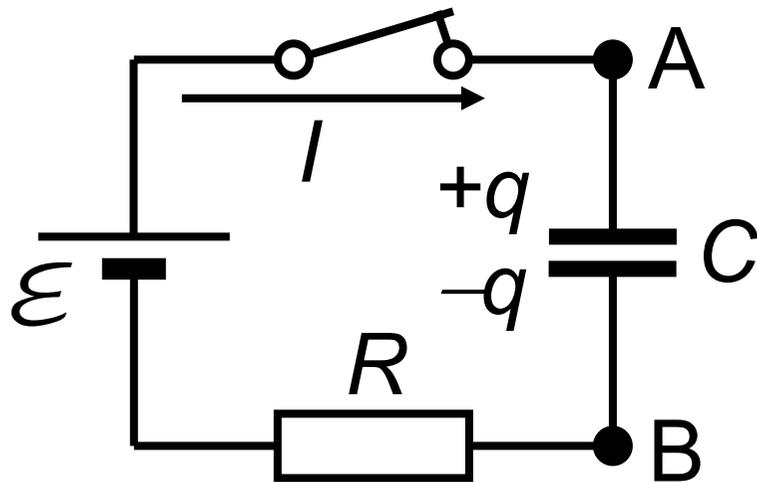

$q$  - charge at the plates of the capacitor

$\varepsilon$  - electromotive force in the battery

$I$  - current in the direction of the arrow

$U_{AB}$  - potential difference between A and B

Before the switch is turned on:  $q = 0$  ,  $U_{AB} = 0$  ,  $I = 0$

Long time after (established):  $U_{AB} = \varepsilon$  ,  $q = C \cdot \varepsilon$  ,  $I = 0$

After the switch is turned on, a transient from  $q = 0$  to  $q = C \cdot \varepsilon$  takes place

How to analyse the transient? - The transient is **slow**, therefore

at **every moment of time**  $t$  , the 2nd Kirchhoff's law is valid

$$U_{AB}(t) - \varepsilon = -I(t) \cdot R$$

$$q(t) = C \cdot U_{AB}(t)$$

Relation between charge and current (note sign):  $I(t) = \frac{dq(t)}{dt}$

These three equations result in a differential equation

$$\frac{q(t)}{C} - \mathcal{E} = -R \frac{dq(t)}{dt}$$

We denote

$$\frac{dq(t)}{dt} = -\frac{1}{RC} (q(t) - C\mathcal{E})$$

$$y(t) = q(t) - C\mathcal{E}$$

$$\tau = RC$$

$$\frac{dy}{dt} = -\frac{y}{\tau} \quad \therefore \quad y = y_0 \exp(-t/\tau)$$

$$(y_0 - \text{value of } y \text{ at } t = 0: \quad y_0 = -C\mathcal{E})$$

$$q(t) = C\mathcal{E} [1 - \exp(-t/RC)] = C\mathcal{E} [1 - \exp(-t/\tau)]$$

$$U_{AB} = \mathcal{E} [1 - \exp(-t/RC)] = \mathcal{E} [1 - \exp(-t/\tau)]$$


$$I(t) = \frac{\mathcal{E}}{R} \exp(-t/RC) = \frac{\mathcal{E}}{R} \exp(-t/\tau)$$

$$\tau = RC$$

- time constant

$t$	$\tau$	$2\tau$	$3\tau$	$4\tau$
$\exp(-t/\tau)$	0.37	0.14	0.05	0.02

## ANALYSIS OF OBTAINED RESULTS

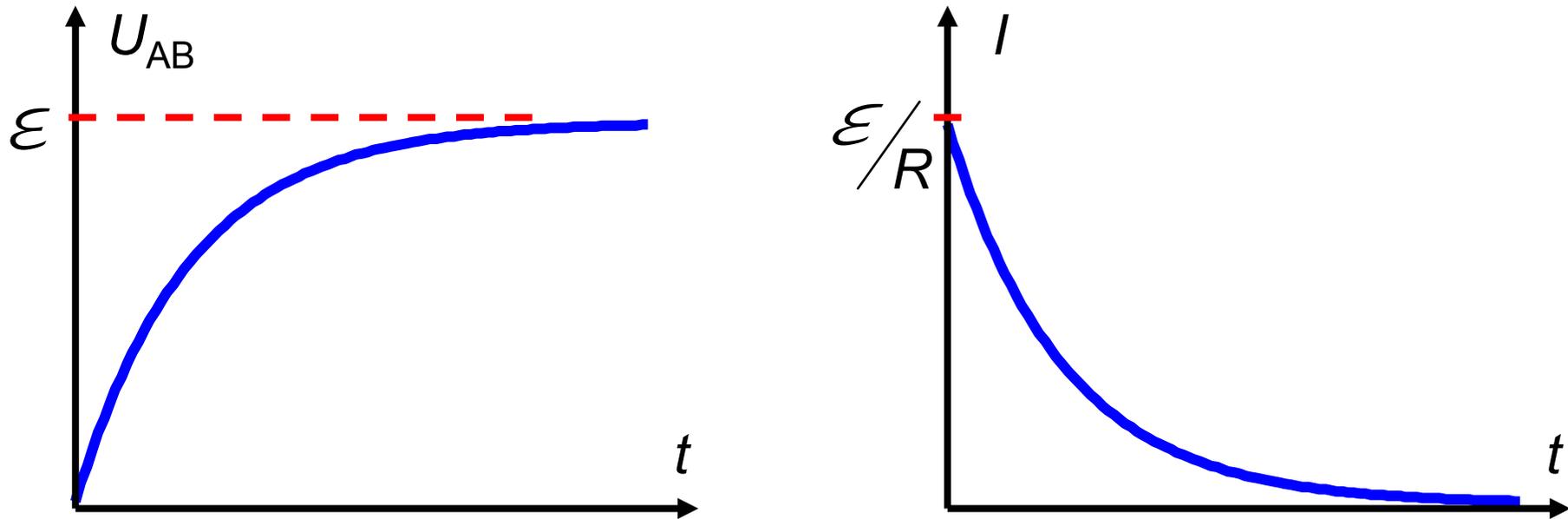

$$\text{At } t = 0: \quad q = 0; \quad U_{AB} = 0; \quad I = \varepsilon/R$$

$$\text{At } t = \infty: \quad q = C\varepsilon; \quad U_{AB} = \varepsilon; \quad I = 0$$


Though the capacitor provides the open circuit,  
**the current at  $t = 0$  is such as if it is a short circuit !**

This happens because at  $t = 0$ ,  $U_{AB} = 0$

$$\tau = RC$$

$$R = 1 \text{ M}\Omega \text{ and } C = 1 \text{ }\mu\text{F} : \quad \tau = 1 \text{ sec}$$

## TRANSIENT IN A $LR$ CIRCUIT

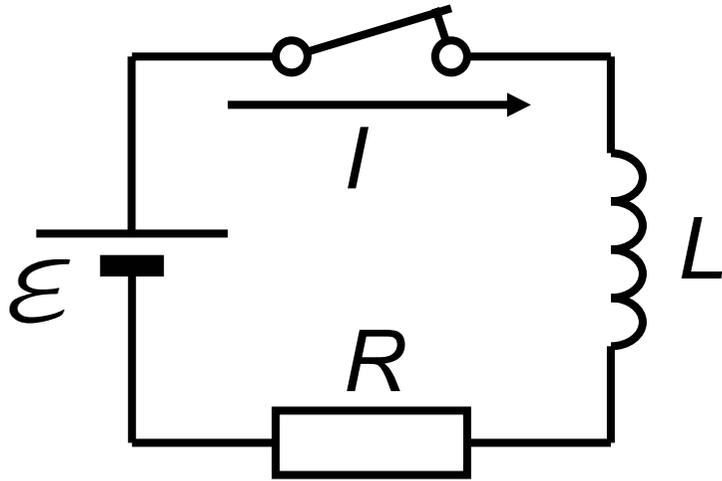

$L$  - self-inductance of the coil

$\mathcal{E}_i$  - EMF of the electromagnetic induction

$\Phi$  - flux of magnetic field through the coil

$$\Phi = L \cdot I$$

Reminder: Electromagnetic induction in the coil

$$\mathcal{E}_i = -\frac{d\Phi(t)}{dt} = -L \frac{dI(t)}{dt}$$

Before the switch is turned on:  $I = 0$

Long time after (established):  $I = \mathcal{E}/R$

After the switch is turned on, a transient from  $I = 0$  to  $I = \mathcal{E}/R$  takes place

At **every moment of time**  $t$ , the 2nd Kirchhoff's law is valid

$$\mathcal{E} + \mathcal{E}_i = I \cdot R$$

A differential equation is obtained

$$\mathcal{E} - L \frac{dI(t)}{dt} = I \cdot R$$

We denote

$$\frac{dI(t)}{dt} = -\frac{R}{L} \left( I(t) - \frac{\mathcal{E}}{R} \right)$$

$$y(t) = I(t) - \frac{\mathcal{E}}{R} \quad \text{and} \quad \tau = L/R$$

$$\frac{dy}{dt} = -\frac{y}{\tau} \quad \therefore \quad y = y_0 \exp(-t/\tau)$$

$$(y_0 - \text{value of } y \text{ at } t = 0: \quad y_0 = -\frac{\mathcal{E}}{R})$$


$$I(t) = \frac{\mathcal{E}}{R} \left[ 1 - \exp\left(-\frac{t \cdot R}{L}\right) \right] = \frac{\mathcal{E}}{R} \left[ 1 - \exp\left(-\frac{t}{\tau}\right) \right]$$

$$\mathcal{E}_i(t) = \mathcal{E} \exp\left(-\frac{t \cdot R}{L}\right) = \mathcal{E} \exp\left(-\frac{t}{\tau}\right)$$

$$\tau = L/R$$

- time constant for an LR circuit

## ANALYSIS OF OBTAINED RESULTS

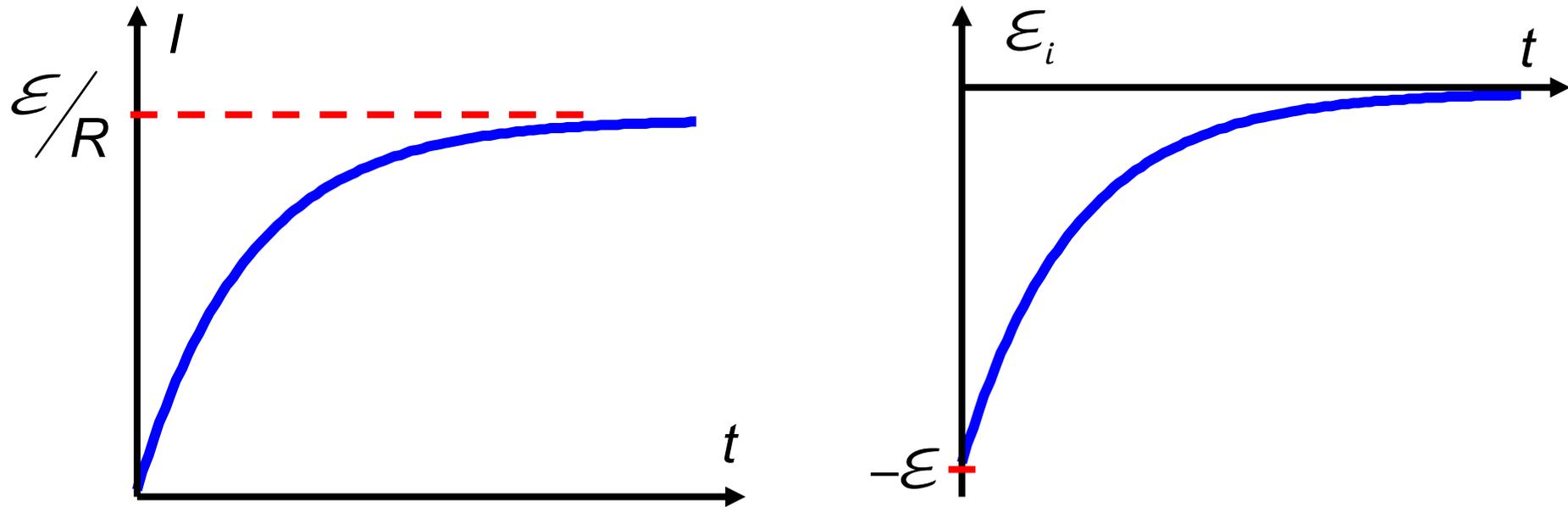

$$\text{At } t = 0: \quad I = 0; \quad \mathcal{E}_i = -\mathcal{E}$$

$$\text{At } t = \infty: \quad I = \frac{\mathcal{E}}{R}; \quad \mathcal{E}_i = 0$$

Though the coil provides the short circuit (its resistance is almost zero),

**the current at  $t = 0$  is such as if it is an open circuit**

At  $t = 0$ , the external EMF is **fully** compensated by the EMF of self-inductance

$$\tau = L/R$$

$$R = 1 \, \Omega \text{ and } L = 1 \text{ henry} : \quad \tau = 1 \text{ sec}$$

# CONCLUSION

If a circuit includes a capacitance or an inductance,  
**final** values of currents or charges **cannot** establish **instantaneously**

There are always **transient processes** which are characterised  
**by time constants**



For an  $RC$  circuit  
time constant

$$\tau = RC$$

For an  $LR$  circuit  
time constant

$$\tau = L/R$$
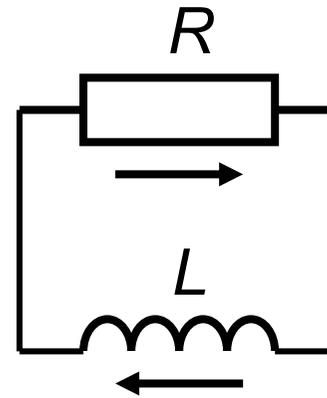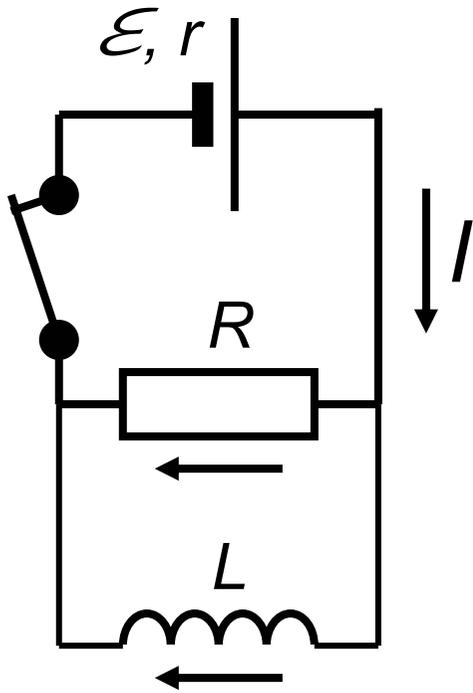
## ENERGY STORED IN A SELF-INDUCTANCE (\*)



After the switch is turned off, the current is driven by the EMF  $\mathcal{E}_i$  which is due to the self-inductance  $L$

$$\mathcal{E}_i = -L \frac{\Delta I}{\Delta t} \quad (I \text{ changes from } I_0 \text{ to } 0)$$

**Work done by the self-inductance EMF**

$$A = \sum \mathcal{E}_i \cdot I \Delta t = -L \sum I \Delta I = -\sum \Phi \Delta I = \frac{\Phi \cdot I_0}{2} = \frac{L \cdot I_0^2}{2}$$

This work was done due to energy  $W$  which was accumulated in the coil

$$W = \frac{L \cdot I^2}{2} \quad \text{- energy stored in a self-inductance}$$

## ENERGY OF MAGNETIC FIELD (\*)

$$W = \frac{L \cdot I^2}{2} = \frac{1}{2} \cdot \mu_0 \cdot n^2 \cdot V \cdot I^2$$

$$B = \mu_0 \cdot n \cdot I$$

$$W = \frac{1}{2\mu_0} \cdot B^2 \cdot V \quad - \text{energy of magnetic field in the volume } V$$

$$w = \frac{B^2}{2\mu_0} \quad - \text{energy density of magnetic field}$$

$$\text{It is similar to } w = \frac{\epsilon_0 E^2}{2} \quad - \text{energy density of electric field}$$

**This similarity reflects the fact that both electric and magnetic fields are manifestations of **the electromagnetic field****