

21/06/06


(3 Hours)

[Total Marks : 100

- N.B. (1) Question No.1 is compulsory. From the remaining questions solve any four questions.
 (2) Figures to the right indicate full marks.
 (3) Assume any suitable data wherever required but justify the same.

Q.1 (a) Derive the equation for Z_i , Z_o , A_v and A_i for the circuit shown in figure.

12

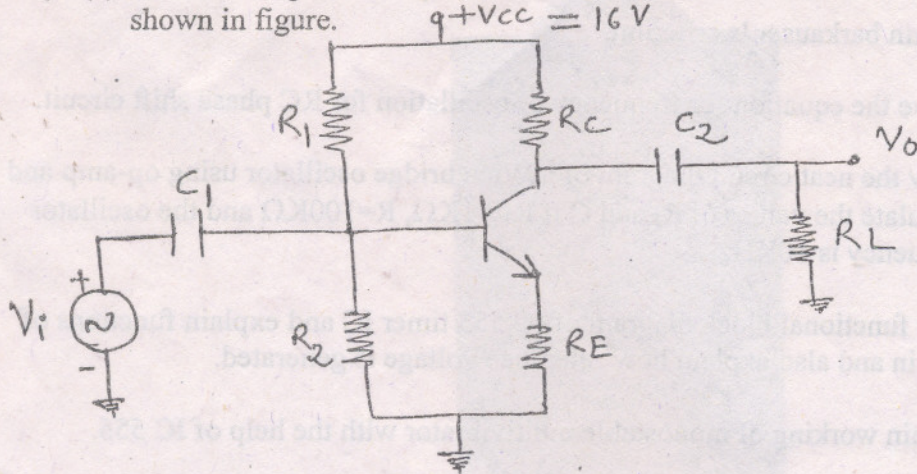


- (b) If $R_1=100K\Omega$, $R_2=10K\Omega$, $R_C=2.2K\Omega$, $R_E=0.68K\Omega$,
 $R_L=10K\Omega$, $\beta=200$, $V_{BE}=0.7V$, $V_{CC}=16V$.

- Find (i) Voltage gain A_v
 (ii) Output impedance Z_o
 Use approximate analysis.

8

Q.2 (a) For the differential amplifier shown in figure determine DC bias Q-point (V_{CEQ} and I_{CQ}).

6

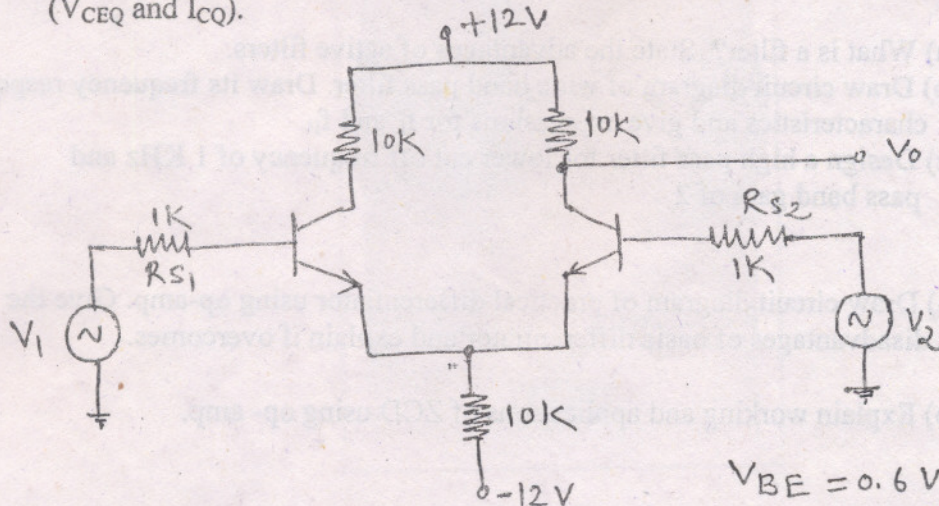

$V_{BE} = 0.6V$

- (b) Write a note on current mirror circuit. 8
- (c) For op-amp explain following terms & give practical values. 6
- (i) Supply voltage rejection ratio
 - (ii) Slew rate
 - (iii) CMRR
- Q.3 (a) Explain Barkhausen's criterion. 4
- (b) Derive the equation for frequency of oscillation for RC phase shift circuit. 10
- (c) Draw the neat circuit diagram of a Wien bridge oscillator using op-amp and calculate the values of R_f and C if $R_1 = 1K\Omega$, $R = 100K\Omega$ and the oscillator frequency is 10KHz. 6
- Q.4 (a) Draw functional block diagram of IC 555 timer IC and explain functions of each pin and also explain how reference voltage is generated. 8
- (b) Explain working of monostable multivibrator with the help of IC 555. 6
- (c) Design a square wave generator using IC 555 for frequency of 10 KHz. 6
- Q.5 (a) Draw and explain functional block diagram of IC 723. Also list its features. 8
- (b) Design a voltage regulator using IC 723, which gives a 5 V output. The maximum load current is 120 mA. Fold back current limiting is to be provided with $I_{SC} = 60mA$. Assume $V_{sense} = 0.6 V$. 12
- Q.6 (a) What is a filter? State the advantages of active filters. 4
- (b) Draw circuit diagram of wide band pass filter. Draw its frequency response characteristics and give expressions for f_L and f_H . 8
- (c) Design a high pass filter for lower cut off frequency of 1 KHz and pass band gain of 2 8
- Q.7 (a) Draw circuit diagram of practical differentiator using op-amp. Give the disadvantages of basic differentiator and explain if overcomes. 12
- (b) Explain working and applications of ZCD using op- amp. 8