

Electronic Devices & Linear Circuits (3 Hours)

- N.B.: (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assume suitable data if necessary.
 (4) Figures to right indicate full marks.

Q. 1. Attempt any four of the following:

20

- Compare BJT & FET.
- Why Common Emitter Configuration is widely used in amplifier circuits?
- What do you mean by CMRR? What are the various methods to improve CMRR?
- Explain summing amplifier.
- List features of IC 555.

Q. 2. a) Classify & explain feedback amplifiers.

10

- Explain graphical determination of the h-parameters using characteristic curves of C.E. amplifier.

10


Q. 3. a) FET amplifier shown below has following parameters

$$IDSS = 3\text{mA}, \quad V_p = -4V \quad r_d \gg RD$$

Determine, V_{GS} , I_D , V_{DS} & A_v (small signal voltage gain)

10

$$V_D = 30V$$

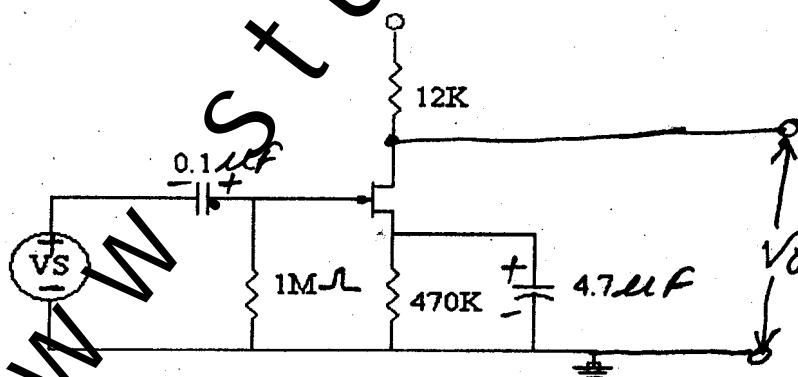

- Explain construction & working of n-channel JFET with the help of characteristic curves.

10

- Explain any two applications of Astable multivibrator using IC 555.

10

- Explain any two applications of IC 565 PLL.

10

- Explain a high voltage low current regulator & low voltage high current regulator.

10

- Design a regulator using LM 723 for $V_o = 9V$ & $I_o = 3\text{Amps}$.

10

Q .5. a) Explain a high voltage low current regulator & low voltage high current regulator.

10

b) Design a regulator using LM 723 for $V_o = 9V$ & $I_o = 3Amps.$

10

Q .6. a) Draw and explain successive Approximation Resister type ADC.

10

b) Explain working of practical Integrator. Also explain its advantages over a simple integrator.

10

Q .7. Write a short notes on (any four) :

20

a) Switching regulators

b) Differentiator

c) Digital to analog convertor using R - 2R registers.

d) Virtual ground of Op-Amp

e) Inverting Schmitt trigger.