

(REVISED COURSE)


(3 Hours)

[Total Marks : 100]


- N.B.: (1) Question No. 1 is compulsory.
 (2) Attempt any four out of remaining six questions.
 (3) Assume suitable data wherever required and justify the same.

1. Attempt any four :-

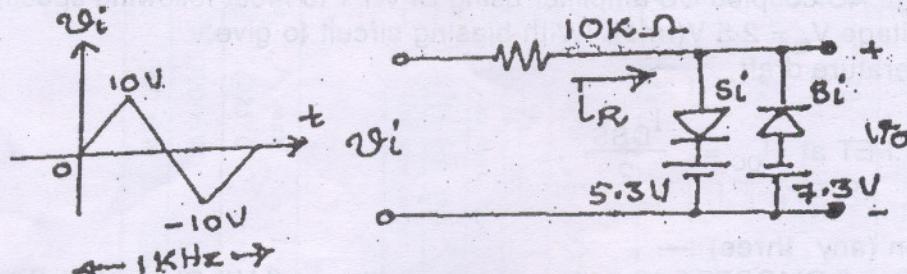- (a) Explain the phenomenon of thermal runaway of BJ transistor. 20
 (b) Complete the sentence : The reverse saturation current of transistor _____ for every _____ °C rise in the C-B junction. Hence calculate the reverse saturation current of a transistor for junction temperature of 87°C if its reverse saturation current at 23°C is 10nA.
 (c) Prove that for a JFET the gate-source bias for zero temperature drift of drain current is at $(V_p - 0.63)$ volts.
 (d) Compare CE and CS amplifiers.
 (e) Draw the circuit diagram of voltage multiplier circuit and explain its operation.
2. (a) Draw a circuit diagram of a full wave rectifier with 'C' filter. Derive expressions for ripple factor. Explain the basic rectifier operation. 10
 (b) For the clipper circuit shown below sketch the waveforms for current I_R and voltage V_0 . 10



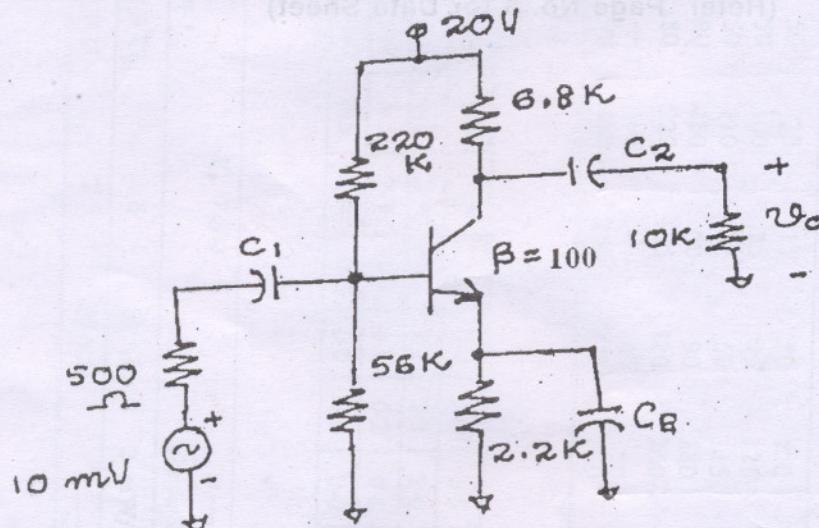3. (a) Draw the common emitter r- π equivalent circuit of the BJ transistor with R_E un-bypassed 10 and derive the expressions for –
- (i) Input resistance
 - (ii) Output resistance
 - (iii) Voltage gain.
- (b) For the transistor circuit given below determine I_B , I_C , V_{CE} , V_{RE} , A_V and R_i 10




4. Design a single stage RC coupled CE amplifier to meet the following specifications : 20
- (a) V_o peak = 3 V
 - (b) $|A_v| \geq 120$; $S = 8$; f_L better than 10 Hz.
 - (c) $R_i = 3 \text{ k } \Omega$.

Choose a suitable transistor with proper justification from the data sheet.

[TURN OVER

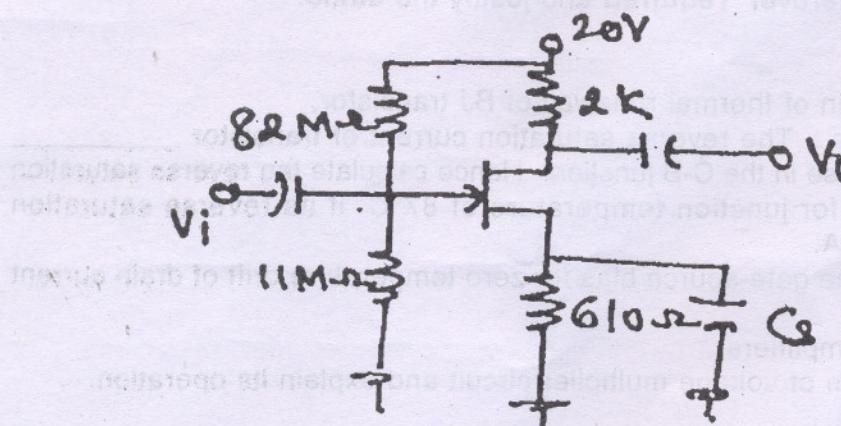5. (a) Draw the neat circuit diagram of a JFET amplifier with source resistance by passed and derive the expression for the voltage gain. 10
- (b) Determine for the circuit below, I_D , V_{DS} , V_{GS} , A_v , Z_1 , and Z_0 .
Determine Z_1 , Z_0 and V_o for circuit shown if $V_1 = 20$ mV. 10



$$I_{DSS} = 12 \text{ mA}, \quad V_p = -3V \quad \gamma_d = 100 \text{ k}\Omega.$$

6. Design a single stage AC coupled CS amplifier using BFWI 1 to meet following specifications. 20
| $| A_v | = 9$ output voltage $V_o = 2.5 \text{ V(rms)}$. With biasing circuit to give.
(a) Zero temperature draft

$$(b) \text{ To operate FET at } I_{DC} = \frac{I_{DSS}}{2}.$$

7. Write short notes on (any **three**) :— 20
(a) EMOSFET and DMOSFET (Construction, operation and V/I Characteristics)
(b) Photovoltaic Cells and Photo Diodes
(c) 3 biasing methods of BJ transistors and their stability factors.
(d) Zener diode : Principle of operation, V/I Characteristics, Application and typical circuits.

DBEC DATA SHEET

Transistor type	P _{dmax} @ 25°C Watts	I _{cmax} @ 25°C Amps	V _{CE} volts d.c.	V _{CBO} volts d.c.	V _{CEO} (Sus) volts	V _{CER} (Sus) volts	V _{CEx} volts d.c.	V _{BEO} volts d.c.	T _j max °C	D.C. min	current typ.	gain	Small min.	Signal typ.	h _{fe}	V _{BE} max.	θ _f °C/W	Derate above 25°C W/°C
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	3.5	0.05
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—	—
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—	—

Transistor type	h _{ie}	h _{oe}	h _{re}	θ _{ja}
BC 147A	2.7 K Ω	18 μV	1.5 × 10 ⁻⁴	0.4°C/mW
2N 525 (PNP)	1.4 K Ω	25 μV	3.2 × 10 ⁻⁴	—
BC 147B	4.5 K Ω	30 μV	2 × 10 ⁻⁴	0.4°C/mW
ECN 100	50 Ω	—	—	—
ECN 149	15 Ω	—	—	—
ECN 055	12 Ω	—	—	—
2N 3055	6 Ω	—	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I _{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I _{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I _{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V _{DS} max. Volts	V _{DG} max. Volts	V _{GS} max. Volts	P _d max. @25°C mW	T _j max. °C	I _{DSS}	s _{mo} (typical)	-V _p Volts	r _d	Derate above 25°C mW/°C	θ _{ja}
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μV	6	50 KΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μV	2.5	50 KΩ	—	0.59°C/mW