

Con. 2685-09.

VR-3300

## Basic of Electronic Circuits

(REVISED COURSE)

(3 Hours)



[Total Marks : 100]

- N.B. : (1) Question No.1 is compulsory.  
 (2) Attempt any four out of remaining seven questions.  
 (3) Assume suitable data wherever required and justify the same.


1. Attempt any four :—

20

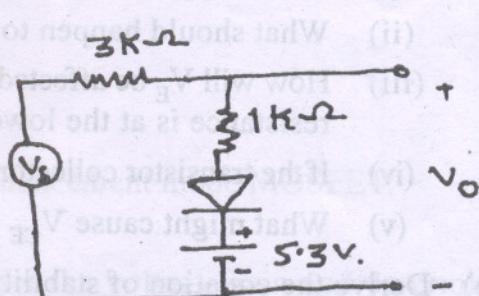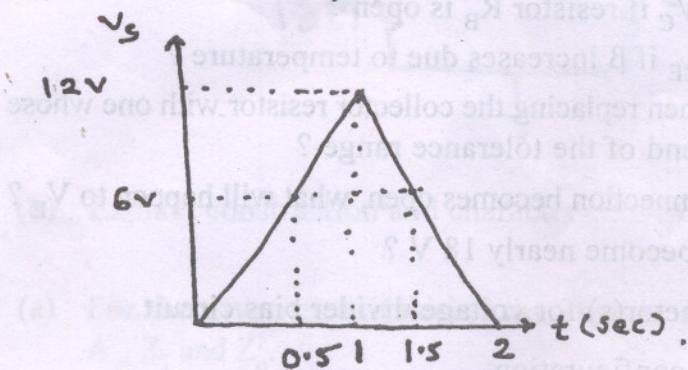- (a) Sketch the output voltage  $V_o$  in the following circuit for the variable input voltage  $V_s$ . Assume  $V_y = 0.7 \text{ V}$ .




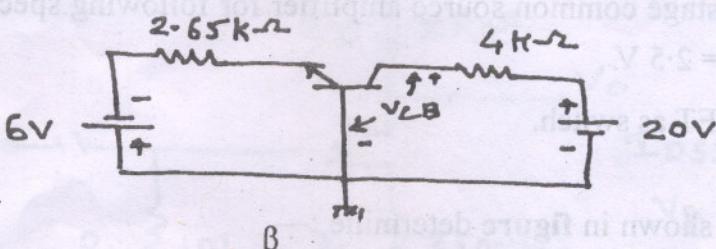- (b) Draw D.C. load line for below circuit.




- (c) Derive the relation  $\alpha = \frac{\beta}{\beta + 1}$ .

- (d) Sketch the d.c. load line.

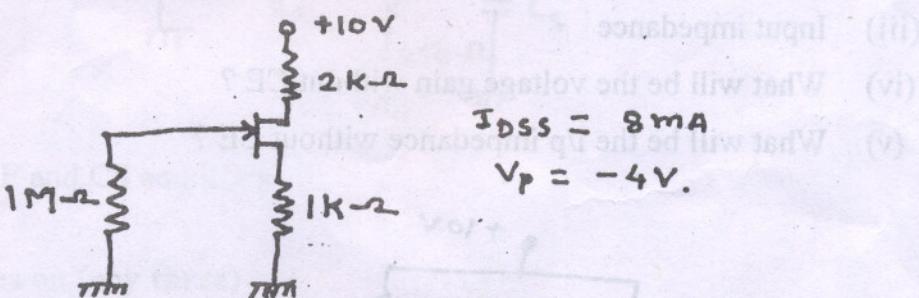

- (e) Explain necessity of Biasing for BJT Amplifier.

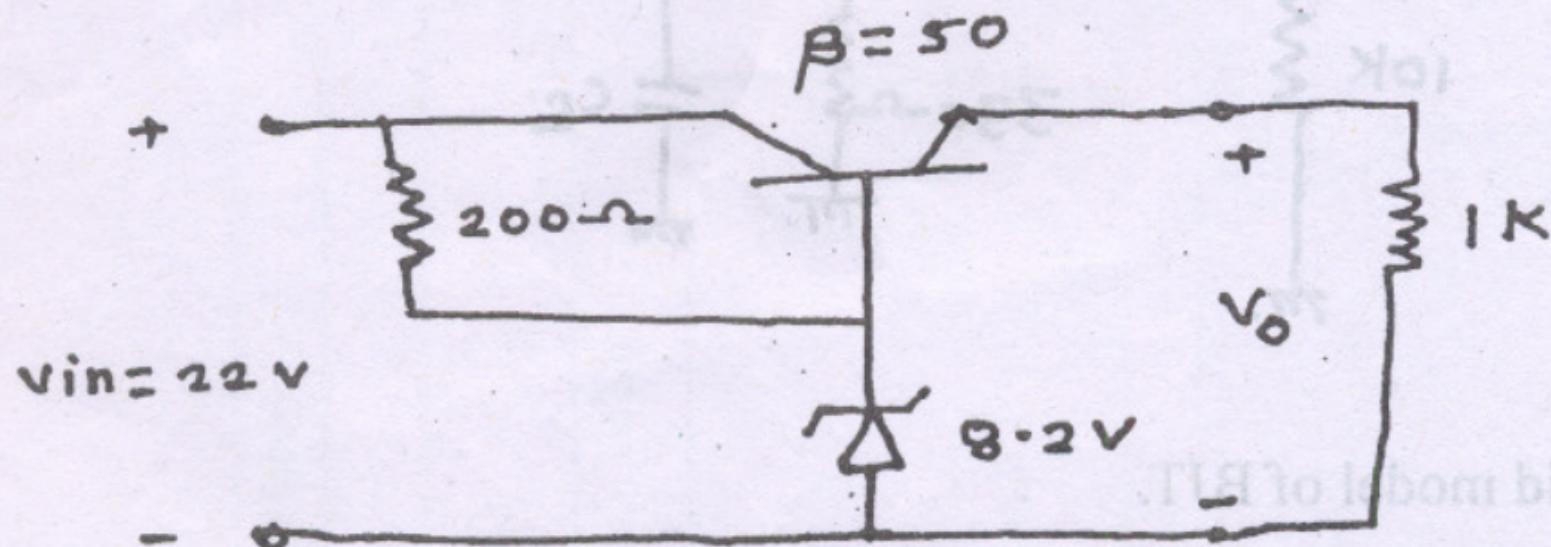2. (a) Explain Bridge rectifier circuit and derive the formula for ripple Factor, TUF and efficiency of rectification. 14
- (b) Determine output voltage and zener current for following circuit. 6




[TURN OVER

Con. 2685-VR-3300-09.

2

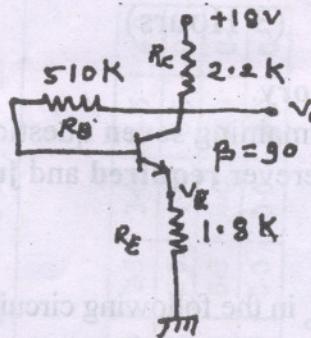3. (a) Answer the following questions for the given circuit. 10



30


- (i) What happens to voltage  $V_C$  if resistor  $R_B$  is open ?
  - (ii) What should happen to  $V_{CE}$  if  $\beta$  increases due to temperature ?
  - (iii) How will  $V_E$  be affected when replacing the collector resistor with one whose resistance is at the lower end of the tolerance range ?
  - (iv) If the transistor collector connection becomes open, what will happen to  $V_E$  ?
  - (v) What might cause  $V_{CE}$  to become nearly 18 V ?
- (b) Derive the equation of stability factor(s) for voltage divider bias circuit. 6
- (c) Compere Biasing methods of CE configuration. 4

4. (a) Design single stage common source amplifier for following specifications. 16
- $A_V = -25, V_o = 2.5 \text{ V}.$
- (b) Explain MOSFET as switch. 4

5. (a) For the circuit shown in figure determine :—

15

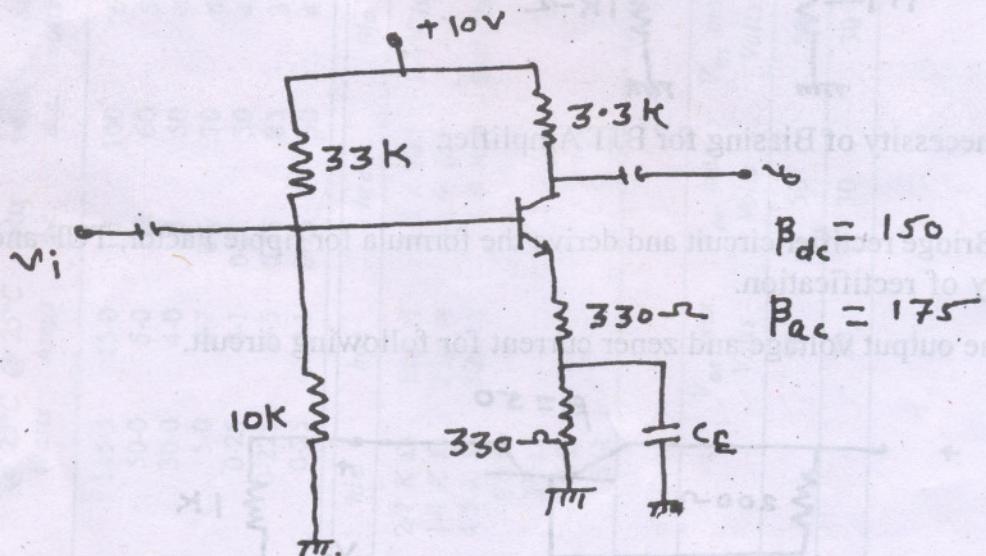- (i) Operating point
- (ii) Voltage gain
- (iii) Input impedance
- (iv) What will be the voltage gain without CE ?
- (v) What will be the i/p impedance without CE ?




(b) Explain hybrid model of BJT.

5

Con. 2685-VR-3300-09.


3

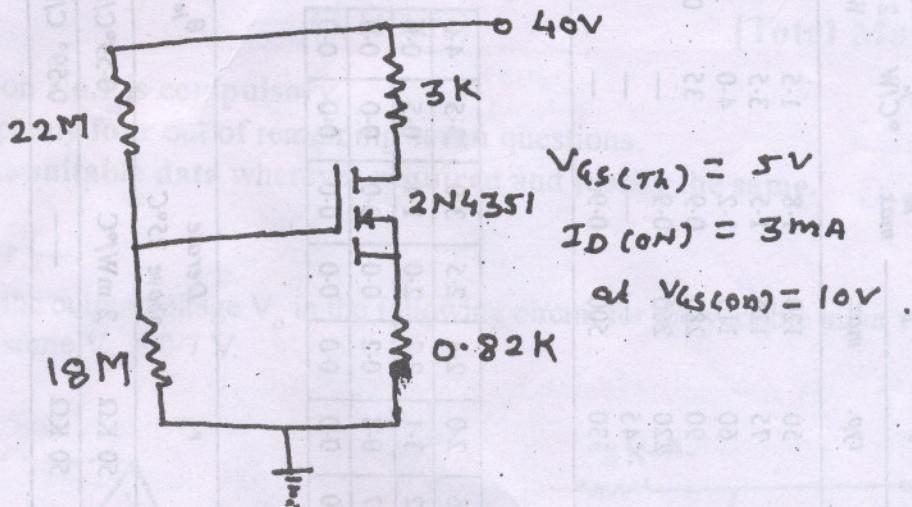6. (a) Determine  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DS}$  for given network.



- (b) Explain construction and characteristics of enhancement mode MOSFET. 8

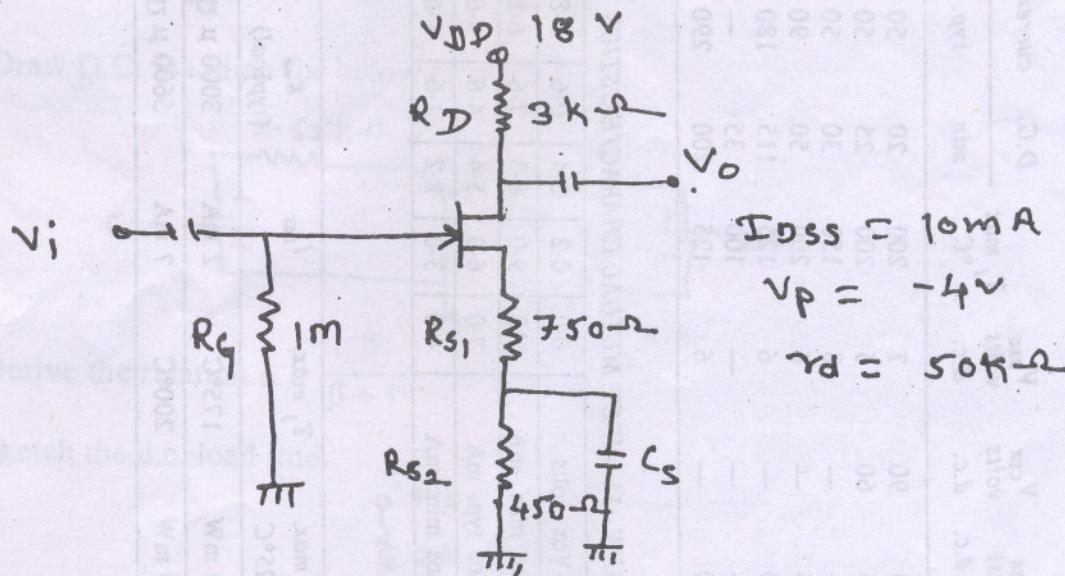7. (a) For the given circuit derive the expression for the voltage gain and determine  $A_v$ ,  $Z_i$  and  $Z_o$ . 16



- (b) Compare CE and CS amplifier. 4

8. Write short notes on (any three) :—

- Photo diodes and Photo voltaic cells.
- Switching characteristics of BJT.
- Voltage Multiplier.
- Bias compensation.

4

20

12

# DBEC DATA SHEET

Transistor type	Pdmax @ 25°C Watts	Icmax @ 25°C Amps	V <sub>CE</sub> (sat) volts	V <sub>CBO</sub> volts	V <sub>CEO</sub> (Sus) volts	V <sub>CER</sub> (Sus) volts	V <sub>CEx</sub> volts	V <sub>BEO</sub> volts	T <sub>j</sub> max °C	D.C. min	current typ.	gain	Small	Signal	h <sub>fe</sub>	V <sub>BE</sub> max.	θ <sub>fe</sub> °C/W	Dera above 25°C W/I%
			d.c.	d.c.	volts d.c.	d.c.	d.c.	d.c.	d.c.	°C		max.	min.	typ.	max.			
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.1
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.1
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35	0.0
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—	—
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—	—
Transistor type	hie	hoe	hre	θja														
BC 147A	2.7 K Ω	18μ V	1.5 × 10 <sup>-4</sup>	0.4°C/mw														
2N 525 (PNP)	1.4 K Ω	25μ V	3.2 × 10 <sup>-4</sup>	—														
BC 147B	4.5 K Ω	30μ V	2 × 10 <sup>-4</sup>	0.4°C/mw														
ECN 100	50Ω	—	—	—														
ECN 149	15Ω	—	—	—														
ECN 055	12Ω	—	—	—														
2N 3055	6Ω	—	—	—														

## BFW 11—JFET MUTUAL CHARACTERISTICS

-V <sub>GS</sub> volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I <sub>DS</sub> max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I <sub>DS</sub> typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I <sub>DS</sub> min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

## N-Channel JFET

Type	V <sub>DS</sub> max. Volts	V <sub>DG</sub> max. Volts	V <sub>GS</sub> max. Volts	P <sub>d</sub> max. @25°C mW	T <sub>j</sub> max. °C	I <sub>DSS</sub>	g <sub>mo</sub> (typical)	-V <sub>P</sub> Volts	r <sub>d</sub>	Derate above 25°C mW/°C	θ <sub>ja</sub>
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ V	6	50 KΩ	2 mW/°C	0.59°C/m
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ V	2.5	50 KΩ	—	0.59°C/m