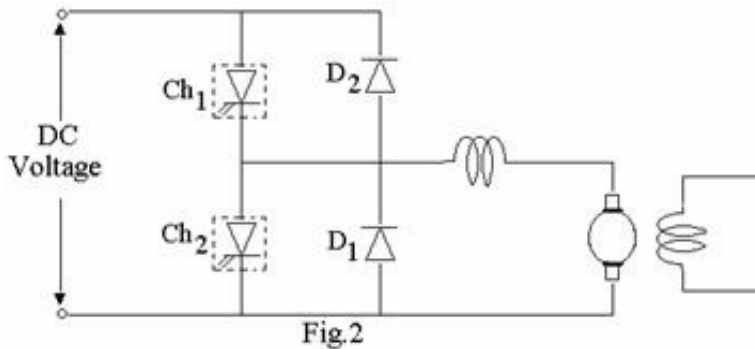





e. In the two quadrant chopper shown in Fig.2 the devices \_\_\_\_\_ are connected to the source for one part of the period  $\tau$  and the devices \_\_\_\_\_ for the other part.

- (A)  $Ch_1$  and  $D_1$ ,  $Ch_2$  and  $D_2$
- (B)  $D_1$  and  $D_2$ ,  $Ch_1$  and  $Ch_2$
- (C)  $Ch_1$  and  $D_2$ ,  $Ch_2$  and  $D_1$
- (D) none of these.



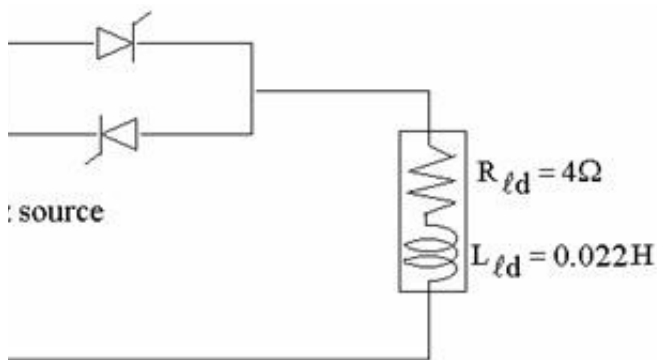f. For the single phase chopper of Fig.3, the control of load voltage is possible for a firing angle that approximately obeys the inequality




- (A)  $\alpha > \frac{\pi}{4}$
- (B)  $\alpha > \frac{\pi}{3}$
- (C)  $\alpha > \frac{\pi}{2}$
- (D)  $\alpha > \frac{2\pi}{5}$

g. As compared to simultaneous control of a cycloconverter, nonsimultaneous control has the drawback of \_\_\_\_\_.

- (A) large ratings of the thyristor
- (B) more  $I^2R$  loss




relevant  
operation.

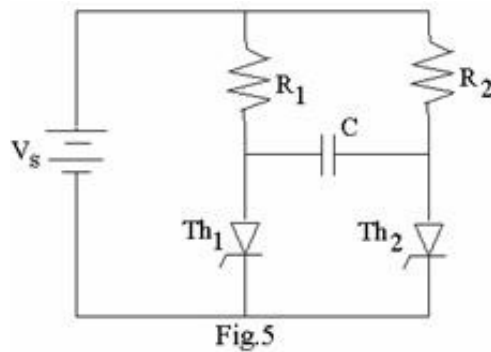

explain  
(8) the

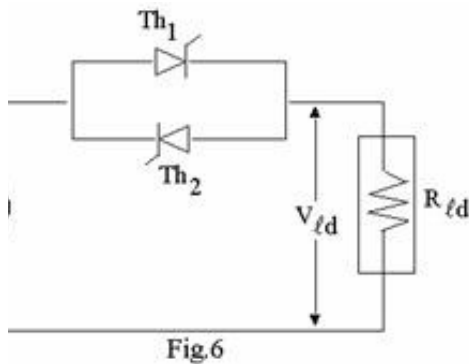- Q.6** a. For the circuit of Fig.6 derive the expressions for the output voltages for the following two conditions:
- the input voltage is connected to the load for  $n$  cycles and disconnected for  $m$  cycles.
  - a bi-directional control is implemented with a firing angle of  $\alpha$ .
- Derive the expressions for the output voltages in both the cases. (6)




- b. With the help of a block diagram describe the features of a switch mode regulator. Explain the part played by the control voltage and the saw tooth waveform in this regulator. (8)

## PART II

**Answer any THREE Questions. Each question carries 14 marks.**

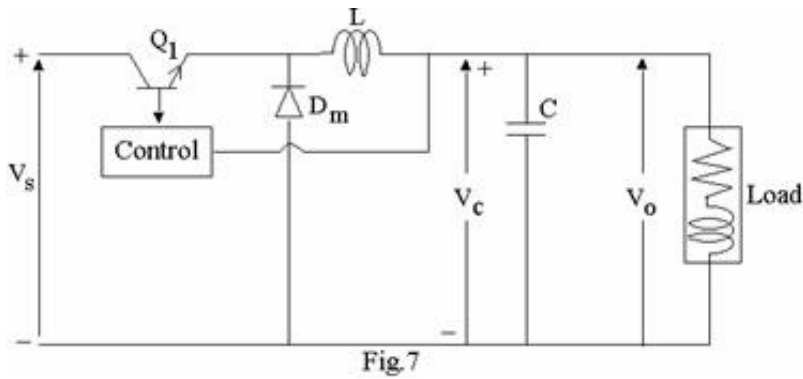- Q.7** a. Describe the features of a PWM in which a sinusoidal reference signal is compared with a triangular wave. With the help of waveforms explain its merits with respect to multiple PWM. (8)
- b. Describe the phase-displacement technique that is applied for the voltage control of a single-phase inverter. (6)
- Q.8** a. Give the circuit and waveforms of a three-phase inverter in which 180-degree conduction type of control is applied. (6)
- b. The buck regulator in Fig.7 has an input voltage ( $V_s$ ) as 16V. The required average output voltage ( $V_a$ ) is 7V. The peak-to-peak output ripple voltage is 22mV and the switching frequency is 28 KHz. If the peak-to-peak ripple current of the inductor is limited to 0.75A, determine the sizes of the filter inductor  $L$  and the filter capacitor  $C$ . (8)



**Q.9** a. Explain the principle of a Current Source Inverter (CSI); also describe the operation of a single phase CSI. **(8)**

b. In a typical UJT triggering circuit  $R$  is given as a  $50\text{ K}\Omega$  and  $V_{B1}$  as  $18.2\text{V}$ , given  $V_s = 35\text{V}$ ,  $\eta = 0.53$ ,  $I_p = 12\mu\text{A}$ ,  $V_v = 3.8\text{V}$ ,  $I_v = 9\text{mA}$ . Check the correctness of  $R$  and  $V_{B1}$ ; and in the latter case compute the percentage error with respect to the correct value. **(6)**

**Q.10** a. Give the circuit of a dual converter which is constituted of two three phase bridge converters and explain how it is made free of circulating current. Discuss any other uses of the dual converter. **(8)**

b. Write briefly as to how constant Torque and constant power operation can be obtained from a separately excited DC motor using a solid-state converter, for a wide range of speed. **(6)**

**Q.11** Write notes on any **TWO** of the following:

- (i)  $\frac{di}{dt}$  and  $\frac{dv}{dt}$  protection of a thyristor.
- (ii) IGBT vs MOSFET.
- (iii) PUT.

**(2x7)**