

## ELECTRONICS

1. In case of amplitude modulation if three sine waves simultaneously modulate the carrier with individual modulation indices  $m_1$ ,  $m_2$  and  $m_3$ , then total modulation index is given by :
  - (A)  $\sqrt{m_1^2 + m_2^2 + m_3^2}$
  - (B)  $m_1 + m_2 + m_3$
  - (C)  $\sqrt[3]{m_1 m_2 m_3}$
  - (D)  $(m_1 + m_2 + m_3)/2$
2. Identify the false statement with regard to advantages and disadvantages of FM :
  - (A) FM is, or can be made, relatively immune to the effects of noise
  - (B) A much smaller channel is required by FM, up to 1/10 times as small as that needed by AM
  - (C) FM transmitting and receiving equipments tend to be more complex
  - (D) The amplitude of the FM wave is constant. It is thus independent of modulation index
3. The absorption of radio waves by the atmosphere depends on :
  - (A) the distance from the transmitter
  - (B) the polarization of the wave
  - (C) the frequency of the wave
  - (D) both the distance and the polarization of the wave
4. The most suitable method out of the following in measurement of the resistance of expected value less than  $1 \Omega$  is :
  - (A) Limit bridge method
  - (B) Wheatstone's bridge method
  - (C) Loss of charge method
  - (D) Kelvin's bridge method

5. The diffusion current density is :
- (A) directly proportional to the concentration gradient of charge carriers
  - (B) inversely proportional to the concentration gradient of charge carriers
  - (C) independent of the concentration gradient of charge carriers
  - (D) directly proportional to concentration of charge carriers
6. With increase in temperature :
- (A) the resistivity of a conductor decreases while that of a semiconductor increases
  - (B) the resistivity of both conductor and semicondnuator increases
  - (C) the resistivity of both conductor and semiconductor decreases
  - (D) the resistivity of a conductor increases and that of semiconductor decreases
7. The ratio of electron and hole concentrations in case of an intrinsic semiconductor is :
- (A) greater than one
  - (B) less than one
  - (C) equal to one
  - (D) equal to square of the intrinsic carrier concentration

8. In case of a centre-tap full-wave rectifier if  $V_{\max}$  is the peak voltage across the secondary of the transformer, the voltage appearing across the non-conducting diode is :
- (A)  $V_{\max}$
  - (B)  $2 V_{\max}$
  - (C)  $\sqrt{2}V_{\max}$
  - (D)  $V_{\max}/\sqrt{2}$
9. In common base configuration if  $I_E$  is the emitter current and  $\alpha$  is the current gain, the part of the emitter current which forms the collector current is :
- (A)  $\alpha I_E$
  - (B)  $(1 - \alpha)I_E$
  - (C)  $(1 - \alpha)I_E + \alpha$
  - (D)  $(1 + \alpha)I_E$
10. The configuration having the highest input resistance, lowest output resistance and voltage gain less than unity is :
- (A) CE
  - (B) CC
  - (C) CB
  - (D) Both CE and CB
11. The graph plotted between the drain current  $I_D$  and gate-source voltage  $V_{GS}$  for a given drain source voltage  $V_{DS}$  of a MOSFET is called its :
- (A) output characteristics
  - (B) input characteristics
  - (C) transfer characteristics
  - (D) load line

12. The process used in growing thin layers of the material on the semiconductor surface in fabrication of the semiconductor devices is known as :
- (A) Lithography
  - (B) Metallization
  - (C) Diffusion
  - (D) Epitaxy
13. The operation of N-channel JFET involves flow of :
- (A) electrons
  - (B) holes
  - (C) both electrons and holes
  - (D) doping impurity ions
14. The principle of superposition is a fundamental consequence of :
- (A) non-linearity
  - (B) linearity
  - (C) reciprocity
  - (D) both non-linearity and reciprocity
15. The branch relationship of a two terminal resistive element is linear if it is :
- (A) homogeneous
  - (B) additive
  - (C) homogeneous and additive
  - (D) none of the above

16. In model analysis of networks the choice of a reference node :
- (A) alters the currents flowing through its branches
  - (B) effects the operation of the network
  - (C) alters the voltage across the elements
  - (D) affects the voltage of various nodes
17. The drain-source voltage at which the channel opening of a JFET reduces to zero is known as :
- (A) cut-in voltage
  - (B) punch-through voltage
  - (C) pinch-off voltage
  - (D) breakdown voltage
18. The quality factor of any circuit is given by :
- (A)  $2\pi$  times the energy dissipated per cycle divided by the energy stored per cycle
  - (B)  $2\pi$  times the energy stored per cycle divided by the energy dissipated per cycle
  - (C)  $2\pi$  times the energy stored per cycle
  - (D)  $2\pi$  times the energy dissipated per cycle

19. The normal binary code of Gray 11011 is :
- (A) 11111
  - (B) 11110
  - (C) 11010
  - (D) 10010
20. At resonance frequency  $\omega$ , the Q of a series LCR circuit is given by :
- (A)  $\omega L/R$
  - (B)  $\omega C/R$
  - (C)  $R/\omega L$
  - (D)  $\omega/RL$
21. A device said to be active if its I-V characteristic lies in the :
- (A) 1st quadrant
  - (B) 2nd and 4th quadrants
  - (C) 1st and 3rd quadrants
  - (D) 3rd quadrant
22. The threshold voltage of *p*-channel enhancement MOSFET is :
- (A) zero
  - (B) positive
  - (C) negative
  - (D) independent of device geometry



23.  $\frac{b}{s^2 + as + b}$  is a second order filter gain function that realizes the characteristics of a :
- (A) band pass filter
  - (B) band reject filter
  - (C) high pass filter
  - (D) low pass filter
24. Identify the false statement from the following. The RC filters offer :
- (A) increased circuit reliability because for all the processing steps can be automated
  - (B) improvement in performance because high quality components can be realized
  - (C) an increase in parasitic
  - (D) simpler design process
25. The frequency response curve of a first order filter rolls-off at a rate of :
- (A) 10 db/decade
  - (B) 20 db/decade
  - (C) 10 db/octave
  - (D) 20 db/octave
26. The total number of sets of input conditions that will produce a high output from a three-input OR gate is :
- (A) 7
  - (B) 8
  - (C) 15
  - (D) 16

27. The logic expression  $\overline{A + B} + \overline{A + B}$  on simplification reduces to :
- (A)  $A + B$
  - (B)  $A$
  - (C)  $AB$
  - (D)  $B$
28. A NAND gate with all inputs connected together will function as :
- (A) OR gate
  - (B) AND gate
  - (C) NOT gate
  - (D) NOR gate
29. According to De Morgan's theorem :
- (A) the complement of the product of two or more variables is equal to the sum of the variables
  - (B) the complement of the product of two or more variables is equal to the product of the variables
  - (C) the complement of the product of two or more variables is equal to the product of the complements of the variables
  - (D) the complement of the product of two or more variables is equal to the sum of the complements of the variables



30. When 2's complement of a binary number is taken twice, the result will be :
- (A) square of the original number
  - (B) double of the original number
  - (C) original number
  - (D) half of the original number
31. When binary number 1110101 is divided by the number 1001, the result is :
- (A) 1001
  - (B) 1101
  - (C) 1010
  - (D) 0101
32. In Schottky TTL families a Schottky diode clamping between base and collector of the transistor is used to :
- (A) prevent transistor saturation
  - (B) prevent transistor breakdown
  - (C) prevent short circuit failure
  - (D) increase the fan-in
33. Identify the false statement. Excess-3 code :
- (A) is an unweighted code
  - (B) is used in representing a alphanumeric data
  - (C) is a self-complementing code
  - (D) uses only 10 of the 16 possible 4-bit code groups

34. In logic circuits the positive logic is one in which :
- (A) logic 0 and logic 1 are represented by negative and positive voltages respectively
  - (B) logic 0 and logic 1 are represented by zero and positive voltages respectively
  - (C) the voltage corresponding to logic 0 is lower than that corresponding to logic 1
  - (D) the voltage corresponding to logic 0 is higher than that corresponding to logic 1
35. With a NAND RS-latch a low R and low S produces :
- (A) high output
  - (B) low output
  - (C) no change
  - (D) race condition
36. A multivibrator which continuously switches between two quasi-stable states without external excitation is known as :
- (A) bistable multivibrator
  - (B) monostable multivibrator
  - (C) astable multivibrator
  - (D) flip-flop

37. The logical value of the logical function  $A + \bar{A}$  is :
- (A) 0
  - (B) 1
  - (C) A
  - (D)  $\bar{A}$
38. The minimum number of JK flip-flops required for designing a modulus-10 counter is :
- (A) 4
  - (B) 6
  - (C) 8
  - (D) 10
39. Identify the *correct* statement from the following :
- (A) Static RAM is volatile while dynamic RAM is non-volatile
  - (B) Static RAM is non-volatile while dynamic RAM is volatile
  - (C) Both static and dynamic RAM are volatile
  - (D) Both static and dynamic RAM are non-volatile
40. Dynamic RAM :
- (A) uses bipolar or MOS flip-flop
  - (B) uses MOSFET's and capacitors
  - (C) needs no refreshing of the data
  - (D) contains less memory cells than a static RAM on the same chip area

41. The 8085 A microprocessor has :
- (A) 10 restart instructions
  - (B) 8 restart instructions
  - (C) 6 restart instructions
  - (D) 4 restart instructions
42. The execution of RST2 instruction vectors to location :
- (A)  $0000_H$
  - (B)  $0008_H$
  - (C)  $0010_H$
  - (D)  $0018_H$
43. The hardware restart of 8085A microprocessor which has the highest priority and when active branches the program to location  $0024_H$  is :
- (A) RST 7.5
  - (B) RST 6.5
  - (C) RST 5.5
  - (D) Trap
44. The decrease in gain of an RC coupled amplifier at low frequency is mainly due to :
- (A) junction capacitances of the transistor
  - (B) emitter resistance
  - (C) coupling capacitor
  - (D) voltage divider resistances used for self-biasing of the amplifier

45. If  $R_i$  and  $R_o$  are the input and output resistances of an amplifier, its power gain in decibels equals its voltage gain in decibels when :
- (A)  $R_i = 2R_o$
  - (B)  $R_i = R_o$
  - (C)  $R_i = R_o/2$
  - (D)  $R_i = 5R_o$
46. A phasor is :
- (A) a vector representing the magnitude and phase of an alternating quantity
  - (B) graph representing the frequency and phase of an amplifier
  - (C) an instrument used for determination phase difference between two time varying quantities
  - (D) a colour tag for distinguishing between different phases of 3-phase supply
47. When the output flows for less than one-half cycle of the input signal, the amplifier is said to operate in :
- (A) Class-A mode
  - (B) Class-AB mode
  - (C) Class-B mode
  - (D) Class-C mode

48. If an amplifier has an overall current gain of 200 and input resistance of  $20\text{ k}\Omega$  with a load resistance of  $10\text{ k}\Omega$ . The overall voltage gain of the amplifier is :
- (A) 20 dB
  - (B) 40 dB
  - (C) 60 dB
  - (D) 80 dB
49. Two amplifiers having mid band voltage gains 20 dB and 40 dB are connected in cascade. The overall voltage gain of the cascade configuration will be :
- (A) 800 dB
  - (B) 60 dB
  - (C) 30 dB
  - (D) 2 dB
50. A class-B push-pull amplifier suffers from :
- (A) intermodulation distortion
  - (B) excess harmonic distortion
  - (C) cross-over distortion
  - (D) none of the above
51. An amplifier with a voltage gain of 1000 uses 1/100th of its output in negative feedback, the gain with feedback is :
- (A) 90.9
  - (B) 80.9
  - (C) 20.9
  - (D) 10.9



52. A program that accepts a high-level language program as input and generates a corresponding machine language program as output is called :
- (A) Linker
  - (B) Loader
  - (C) Compiler
  - (D) Editor
53. Out of the following bridges which one is used for determination the capacitance :
- (A) Schering bridge
  - (B) Wheatstone bridge
  - (C) Kelvin bridge
  - (D) Hay bridge
54. Which one of the following operators does *not* belong to unary operator group ?
- (A) ++
  - (B) <=
  - (C) --
  - (D) size of
55. Identify the *false* statement from the following :
- (A) an integer quantity cannot be added to or subtracted from a pointer variable
  - (B) a pointer variable can be assigned the address of an ordinary variable
  - (C) a pointer variable can be assigned the value of another pointer variable
  - (D) a pointer variable can be assigned a null (zero) value

56. If  $i = 1$ , then on execution of  $++ i$  statement the value of  $i$  will be :
- (A) 1
  - (B) 2
  - (C) 3
  - (D) 4
57. Identify *false* statement. In C programming :
- (A) a preprocessor directive may appear at any place in a source file
  - (B) only one preprocessor directive can occur in a line
  - (C) a preprocessor directive is terminated by a semicolon
  - (D) all preprocessor directives begin with the sharp sign (#)
58. In C programming when working with stream-oriented data file, one has to establish first a buffer area. This is accomplished by :
- (A) `fwrite`
  - (B) `fopen`
  - (C) `fclose`
  - (D) `FILE`
59. Which of the following operators enjoys the highest precedence in C programming ?
- (A) Unary operators
  - (B) Logical operators
  - (C) Relational operators
  - (D) Arithmetic operators
60. Identify the *false* statement from the following :
- (A) A Union contains members whose individual data types may differ from one another
  - (B) The members that compose a union each are assigned its unique storage area within the computer's memory
  - (C) The members that compose a union all share the same storage area within the computer's memory
  - (D) A union can be member of a structure and a structure can be a member of a union.