

Con. 5133-07.

CD-6712

(REVISED COURSE)

(3 Hours)

[Total Marks : 100

N.B.(1) Question No. 1 is compulsory.

(2) Attempt any four questions out of the remaining six questions.

(3) Assume suitable additional data if required.

1. (a) Fill in the blanks :— 5

(i) A number in any number system can be represented by the following equation


(ii) The excess 3 code is _____

(iii) While adding two BCD numbers, if the sum gives an invalid BCD code, then to make it valid _____

(iv) Two's complement of a number is _____

(v) Eight bits make a _____ and four bits make a _____

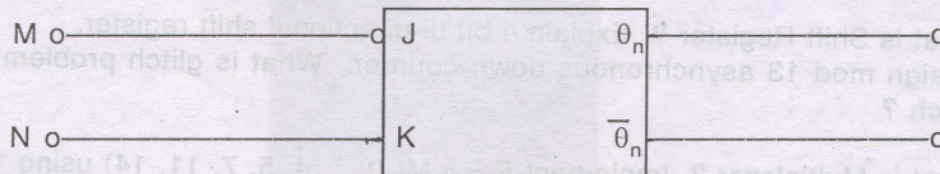(b) Consider the MN FF as shown. Obtain its characteristic table, characteristic equation and excitation table. 5



(c) Carry out following arithmetic without converting to any other base. 4

(i) $(B6A)_{16}$

(ii) $(756)_9$

$-(2FE)_{16}$

$\times (53)_9$

(d) A seven bit Hamming Code is received as 100010. Correct it for any errors. Why Hamming Code is called as error correcting code? Justify. 4

(e) Subtract $(365)_8$ from $(173)_8$. Use 8's complement addition to perform subtraction. 2

2. (a) Simplify using Boolean Theorems and implement using AOI gates only. 10

(i) $[(C + \bar{C}D)(C + \bar{C}\bar{D})] [(AB + \bar{A}\bar{B}) + (A \oplus B)]$

(ii) $\overline{AB + \bar{A}\bar{B}} + (A+B) \cdot (\bar{A} + B)$

(b) Given the logical expression—

$Y = (A + B + \bar{C} + \bar{D}) \cdot (\bar{A} + C + \bar{D}) \cdot (\bar{B} + C)(\bar{B} + \bar{C}) \cdot (A + \bar{B})(\bar{B} + \bar{D})$

(i) Express in std POS form 3

(ii) Draw K map for the equation. 3

(iii) Minimize and realise using NOR gates only. 4

3. (a) Realise FULL Subtractor circuit using 4 : 1 Multiplexer and 3L : 8L Decoder. 10
 [Active high I/p and Active low O/p decoder]
- (b) Using Quine McCluskey Method, determine the minimal SOP form for : 10
 $F(A, B, C, D, E, F, G) = \sum m (20, 28, 38, 39, 52, 60, 102, 103, 127)$
4. (a) The Computer Engineering Society wishes to select members on its board of Governors. 10
 The following criterias are applied. The candidate should be a member of the society for a minimum period of 12 years. A male candidate should have a professional experience of 20 years or more. A female candidate will be eligible if she has an experience of 15 years. Design and implement the above circuit.
- (b) Design and implement two 2 bit multiplier circuit. 10
5. (a) For synchronous sequence counter with sequence 2 — 6 — 5 — 3 — 1 — 0 — 2
- (i) Give present state/next state table 2
- (ii) Write state transition table using D flip-flops. 3
- (iii) Simplify and realize the circuit. Draw state diagram. 5
- (iv) If the counter enters any unused state will it go to lockout condition. Justify. 2
- (b) Draw neat diagram of two I/p TTL NAND gate and explain its operation. 8
6. (a) What is Shift Register ? Explain 4 bit bi-directional shift register. 10
- (b) Design mod 13 asynchronous down counter. What is glitch problem ? How to avoid glitch ? 10
7. (a) What is Multiplexer ? Implement $F = \pi M (0, 1, 4, 5, 7, 11, 14)$ using 16 : 1 multiplexer. 8
- (b) Write short notes on [any **two**] 12
- (i) Master slave JK flip-flop
- (ii) 74180 parity generator and checker
- (iii) PAL and PLA.