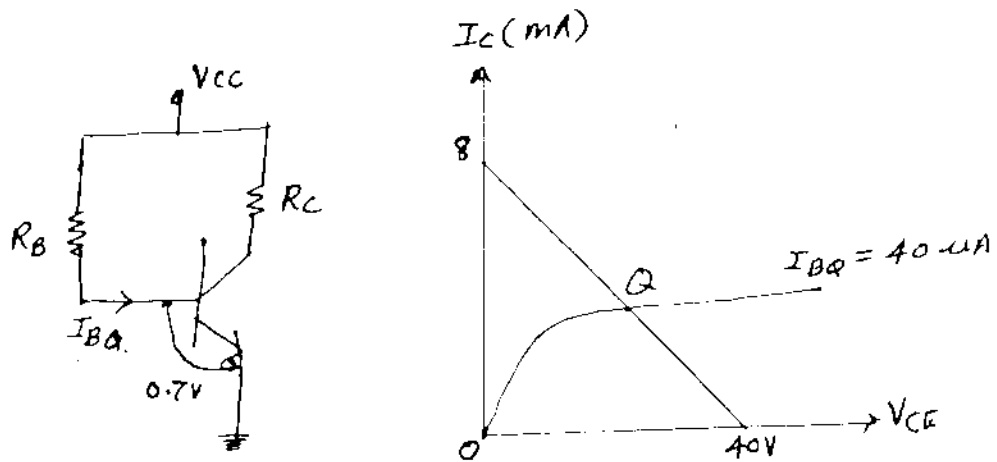



- (1) Question No. 1 is **compulsory**.  
 (2) Attempt any **four** questions from **remaining**.  
 (3) **Figures** to the **right** indicate **full** marks.  
 (4) Assume **additional** data wherever **necessary**.

- (a) Prove that the mid band voltage gain falls by  $\frac{1}{\sqrt{2}}$  at the lower cut-off frequency. Hence obtain the expression for that. 20  
 (b) For what type of a load, 'L' filter and 'C' filter is used ?  
 Also write the significance of bleeder resistance in LC filter.  
 (c) Give the device characteristics. Determine  $V_C$ ,  $R_B$  and  $R_C$  for the following fixed biased configuraion.




- (d) Condition for 'zero temp. drift' in FET. Explain.

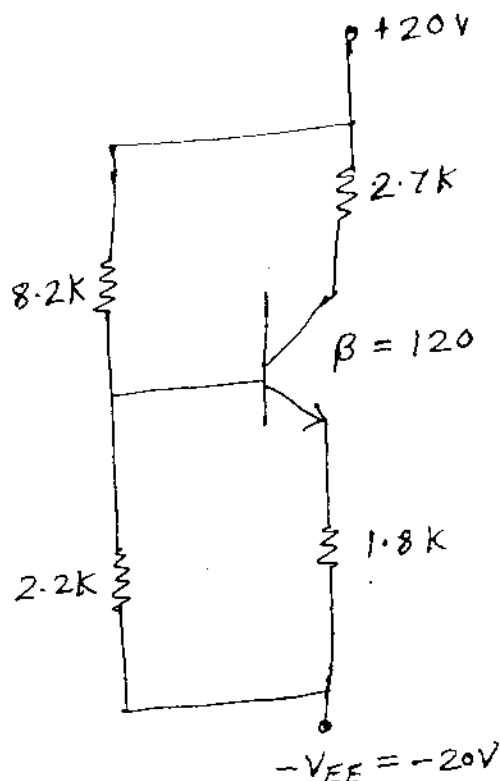- (a) Determine the co-ordinates of Q Point. 10




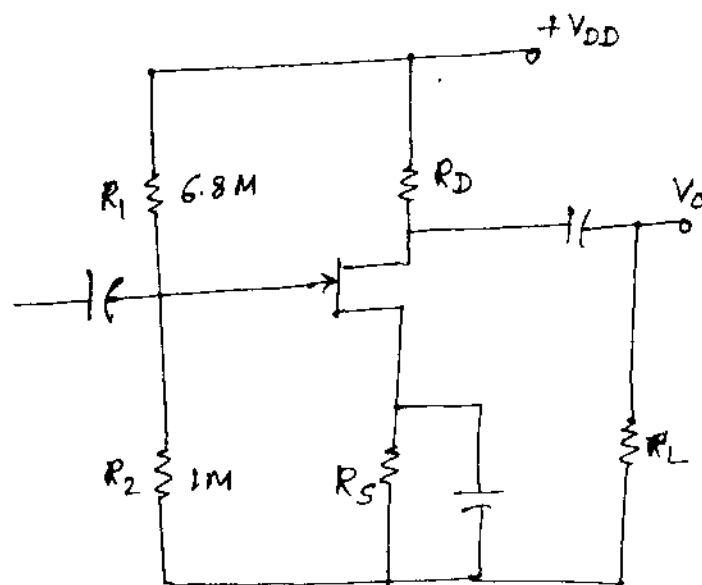(b) For the circuit shown below, determine  $A_V$ ,  $Z_i$  and  $Z_o$ .



$V_{DD} = 20 \text{ V}$      $I_{DSS} = 10 \text{ mA}$   
 $R_D = 1.5 \text{ k}$      $V_p = 3 \text{ V}$   
 $R_S = 1 \text{ k}$      $r_d = 50 \text{ k}$   
 $R_L = 10 \text{ k}$      $I_{DQ} = 3.8 \text{ mA}$

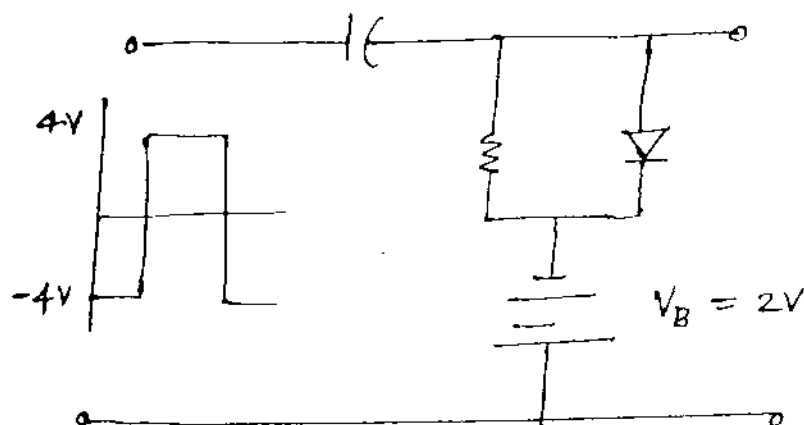3. (a) Design a single stage RC coupled amplifier for the following specifications—  
 gain = 10,  $f_L = 20 \text{ Hz}$ ,  $V_0 = 2.5 \text{ V}$   
 (b) Draw o/p waveform for,




4. (a) Draw various biasing schemes used for BJTs.  
 (b) Draw a neat diagram with proper biasing of JFET CG amplifier. Derive expressions for voltage gain, input impedance and o/p impedance.
5. Design a single stage RC coupled CE amplifier using transistor for the following specifications

$$|A_V| \geq 100, \quad f_L = 20 \text{ Hz}, \quad V_{CC} = 20 \text{ V}, \quad S < 10.$$

- a) The differential amplifier circuit is shown in the **figure** biased at  $I_Q = 0.5 \text{ mA}$ . The transistor parameters are  $\beta = 150$ ,  $V_{A_1} = V_{A_2} = 125 \text{ V}$  and  $V_{A_3} = V_{A_4} = 85 \text{ V}$ . 20

Draw equivalent circuit of BJT differential amplifier with active load.

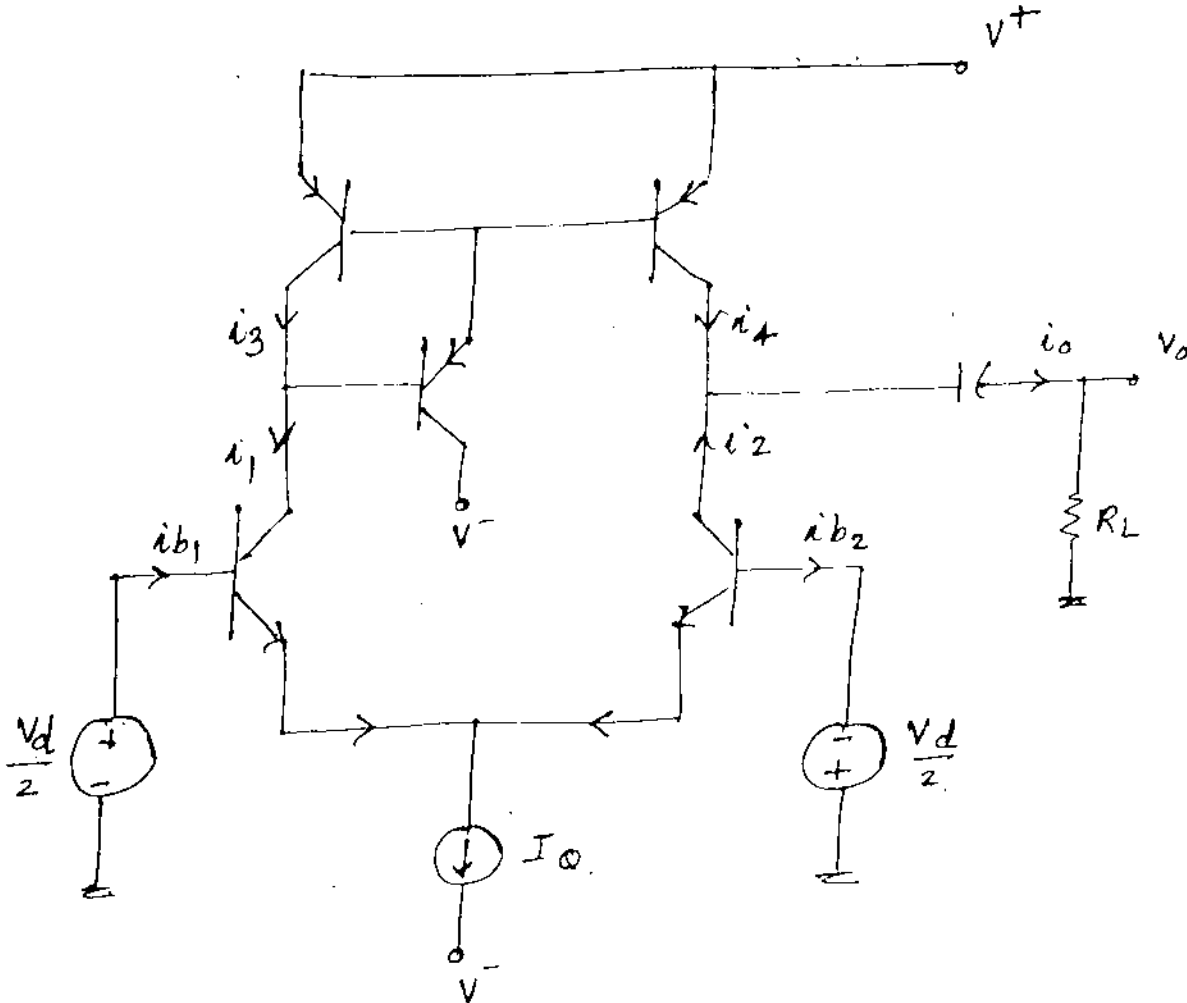- b) Determine the open circuit differential mode voltage gain.  
 c) Find the differential mode voltage gain with  $R_L = 100 \text{ k}$ .  
 d) Find the o/p resistance looking back from the load  $R_L$ .



Write short notes on any **four** :—

20

- Cascode amplifier
- Short circuit and open circuit time constants
- High frequency model of BJT and FET
- LED
- VMOS.

(Refer Page No. 4 for DATA SHEET)

[ TURN OVER