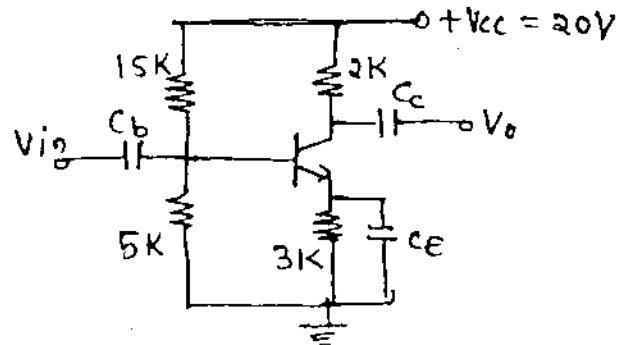
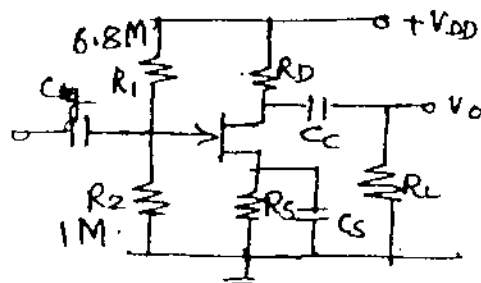


3. Question No. 1 is compulsory.
  2. Solve any four from remaining questions.
  3. Assume suitable data if necessary.
- a. Compare BJT and FET amplifiers. 8
  - b. Determine  $I_{CBO}$  at  $75^\circ$  if it has a value of  $10 \mu A$  at  $30^\circ C$ . 4
  - c. What is the role of circuit resistance  $R$  in clipping circuits. Find its value if the diode used in clipper has forward resistance of  $50 \Omega$  and reverse resistance of  $10 M \Omega$ . 5
  - d. Why CE configuration is preferred over CB and CC, when used as a switch. 3
  - e. Draw a circuit diagram of a full wave rectifier with  $\pi$  filter. Derive expressions for ripple factor. Explain the basic rectifier operation. 10
  - f. For CE amplifier derive the expressions for  $A_v$ ,  $A_i$ ,  $Z_i$  and  $Z_o$ . 10
  - g. Determine the Q point and draw the dc load line for the circuit shown below :— 10



- h. For the circuit shown below determine  $A_v$ ,  $Z_i$  and  $Z_o$ . 10



$$\begin{aligned}
 V_{DD} &= 20V \\
 R_D &= 1.5K\Omega \\
 R_S &= 1K\Omega \\
 R_L &= 10K\Omega
 \end{aligned}$$

$$\begin{aligned}
 I_{DSS} &= 10mA \\
 V_{as(OFF)} &= V_P = 3V \\
 r_d &= 50K\Omega \\
 I_{DQ} &= 3.8mA
 \end{aligned}$$

- i. Design a single stage RC coupled CE amplifier to meet the following specification. 16  
 $V_o = 2V$ ,  $A_v \geq 70$ ,  $S \leq 10$ , Audio frequency range.  $R_L \geq 10K\Omega$ . Use BJT BC 147A.
- j. For above designed circuit determine maximum expected voltage gain  $Z_i$  and  $Z_o$ . 4
- k. Design a single stage RC coupled CS amplifier to meet the following specifications :— 20  
 $f_L = 20Hz$   
 $V_o = 2V$   
 $I_D = 3.3 \pm 0.6mA$   
 $A_v \geq 11$   
 $S.V = 11$  (FET Type)  
 Calculate  $R_g$ ,  $R_o$  and  $V_{o,max}$  for the designed amplifier.
- l. What is clipping? Explain. How a diode circuit can be used for single level and double level clipping? 10
- m. Compare EMOSFET and DMOSFET on basis of their construction, working principle, characteristics and biasing circuits. 10
- n. Short notes on any three :— 20
  - a. Thermal stabilization and compensation
  - b. Photo diode
  - c. Condition for zero temp. drift in FET
  - d. Avalanche and zener breakdown mechanism
  - e. Small signal equivalent circuit of BJT.