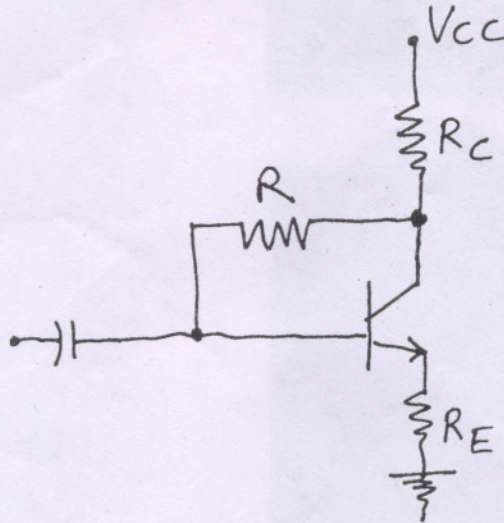


(3 Hours)

[Total Marks : 100

- N.B.** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** from the remaining questions.
 (3) Assume **suitable** data if **necessary**.

1. (a) Derive the expression for stability factor S for collector to base bias and self bias circuit. **12**
 (b) In the circuit shown below, $V_{CC} = 24\text{ V}$, $R_C = 10\text{ K}$ and $R_E = 270\ \Omega$. If a silicon transistor is used with $\beta = 45$ and if under quiescent conditions $V_{CE} = 5\text{ V}$, determine — (i) R (ii) the stability factor S . **8**



2. (a) For dual input balanced output differential amplifier find out expressions for I_{CQ} , V_{CEQ} , differential mode voltage gain, input and output resistances. **10**
 (b) The following specifications are given for the dual input, balanced output bipolar differential amplifier :— **10**
 $R_C = 2.2\text{ K}$, $R_E = 4.7\text{ K}$, $R_S = 50\ \Omega$, $V_{CC} = 10\text{ V}$, $V_{EE} = -10\text{ V}$, $\beta = 100$, $V_{BE} = 0.7\text{ V}$.
 Determine —
 (i) I_{CQ} and V_{CEQ}
 (ii) Differential mode voltage gain
 (iii) Input and output resistances.
3. (a) Explain current limit and current foldback protection of LM 723 using suitable diagrams. **8**
 (b) Design a regulator using LM 723 for $V_0 = 9\text{ V}$, $I_0 = 3\text{ Amp}$. **12**
4. (a) Draw the functional block diagram of IC 555 timer and explain function of each pin. Also explain how reference voltage is generated. **10**
 (b) Design a symmetrical square wave generator using IC 555 for output 1 KHz. **10**
5. (a) Draw and explain the functional block-diagram of voltage controlled oscillator IC. Explain any one application of VCO. **10**
 (b) Derive the equation for frequency of oscillation and condition for oscillation for RC phase shift oscillator. **10**
6. (a) Explain the flash conversion and successive approximation technique. What are their limitations? **10**
 (b) Draw the circuit diagram of practical differentiator using Op-Amp. Give the advantages of basic differentiator. **10**
7. Write short notes on any **two** :— **20**
 (a) Second order Butterworth active filter.
 (b) Instrumentation Amplifier using Op-Amp.
 (c) Digital to Analog converter using R—2R resistors.
 (d) Zero-crossing detector using Op-Amp working and applications.