
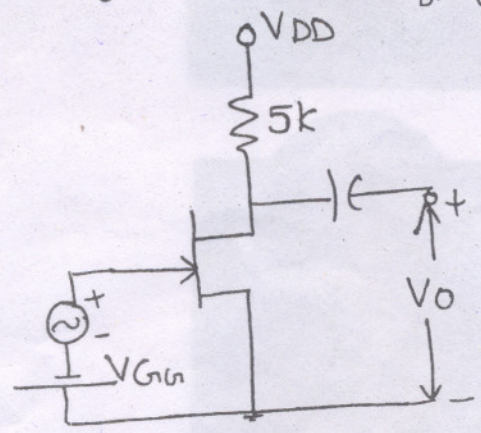


- N.B.** (1) Question No. 1 is compulsory.
 (2) Attempt any **four** questions out of the remaining **six** questions.
 (3) Answer to questions should be **grouped** and written **together**.
 (4) Assume any **suitable** data wherever **required** but justify the **same**.

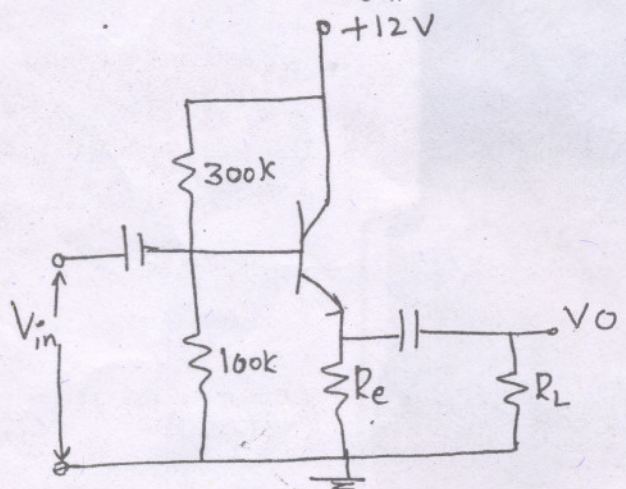1. (a) Derive the expressions for A_v , Z_i , Z_o , A_i for CE Amplifier. 10
 (b) Compare JFET and BJT. 5
 (c) Consider the following circuit. Determine I_D , V_{GS} for $(I_{DSS}) = 4 \text{ mA}$ 5



2. (a) Explain the Graphical determination of the h-parameters using characteristic curves of CE Amplifier. 10
 (b) For the amplifier shown in below figure. Determine the following parameters :— 10
 (i) DC bias Q-point (V_{CEQ} and I_{CQ})
 (ii) Current gain (i_o/i_n)



Assume :
 $r_e = 100 \Omega$
 $V_{BE} = 0.6 \text{ V}$
 $\beta = 100$
 $R_e = 3k \Omega$
 $R_L = 5k \Omega$

3. (a) Draw the block diagram of typical Op-Amp. Explain function of each block. 6
 (b) Explain the following terms for an Op-Amp :— 4
 (i) Input offset voltage
 (ii) CMRR.
 (c) Explain three Op-Amp Instrumentation Amplifier and also derive the overall gain A_v . 10

4. (a) Explain how an Op-Amp can be used as : 15
(i) Integrator (ii) Differentiator (iii) Summing amplifier.
- (b) Using practical Op-Amp realize the following relation :— 5
$$V_O = 5V_1 - 5V_2 + 3V_3.$$
5. (a) Explain the operation of Monostable multivibrator using IC 555. 10
(b) Explain any two applications of Astable multivibrator. 10
6. (a) Explain a high voltage Low Current Regulator and Low Voltage High Current Regulator. 10
(b) Design a regulator using LM 723 for $V_O = 9V$, $I_O = 3Amp$. 10
7. Write short notes on any **three** of the following :— 20
(a) PLL
(b) Non-Inverting Schmitt Trigger
(c) Digital to Analog Converter using R-2R Resistors.
(d) Properties of Ideal Op-Amp.
-