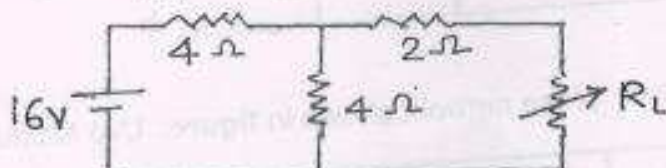


- N.B. (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assume any data if required.
 (4) Figures to the right indicate full marks.


1. Attempt any five :—

20


- (a) Find R_L and $P_{\max}$ of the given circuit.



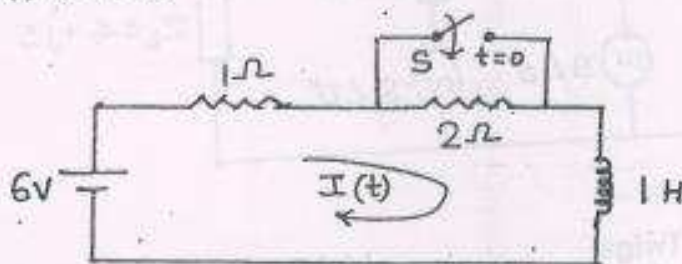- (b) When switch S is open, steady state is reached. When switch S closed at $t = 0$, find $i(t)$ for $t > 0$.




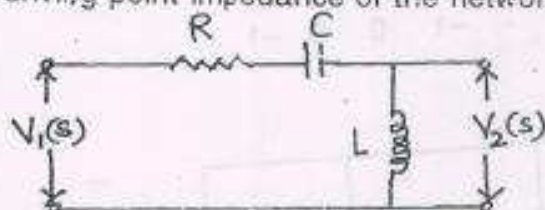- (c) Find the final value of $F(s) = \frac{s+6}{s(s+3)}$. Check the result by solving it for $f(t)$.
 (d) Find condition for symmetry in Y-parameters.
 (e) Find driving point impedance of the network.




- (f) Write properties of R-C impedance function.

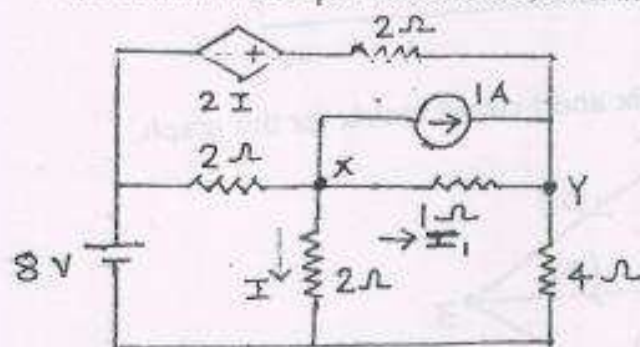2. (a) Determine the current I and I_1 in the circuit shown in figure by using nodal analysis. 10




[TURN OVER]

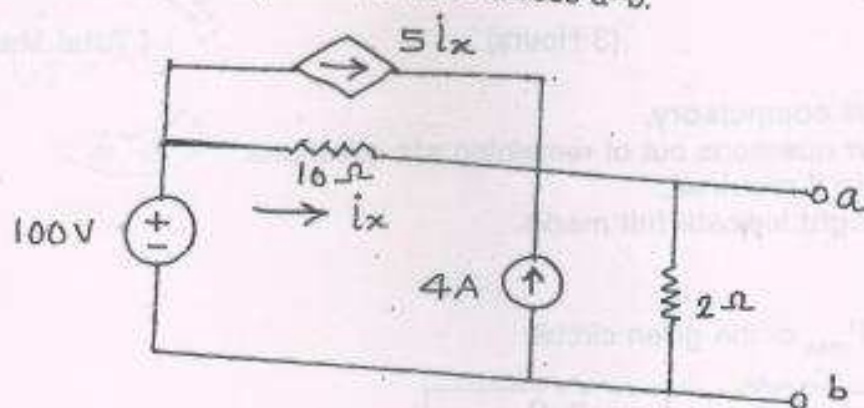- (b) Find Norton's equivalent circuit across a-b.



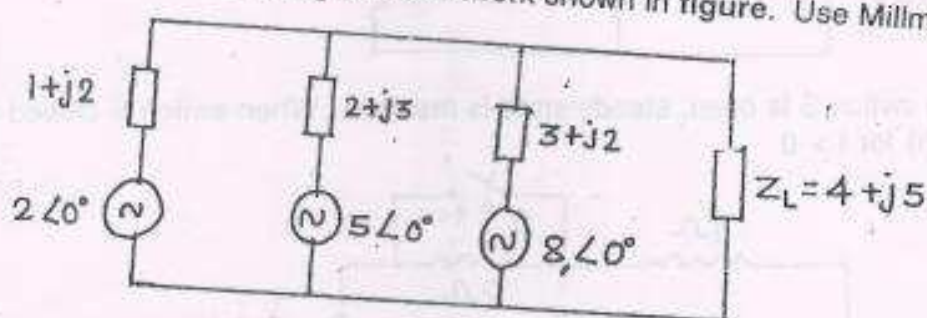3. (a) Find the current through Z_L of the network shown in figure. Use Millman's theorem.




- (b) F-cutset matrix is given as —


	Twigs				Links			
	1	2	3	4	5	6	7	8
1	1	0	0	0	1	1	0	0
2	0	1	0	0	0	-1	-1	0
3	0	0	1	0	0	0	1	1
4	0	0	0	1	-1	0	0	-1

Draw oriented graph.


- (c) Draw dual of network.

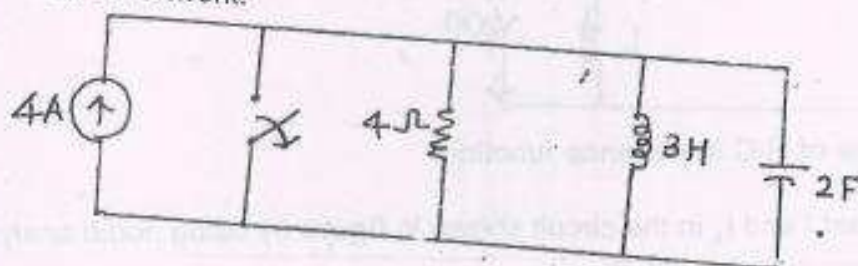

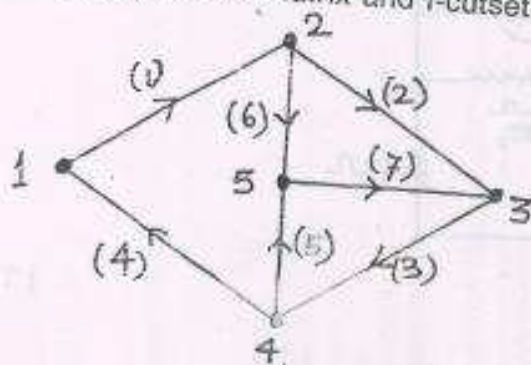4. (a) Find incidence matrix, tie-set matrix and f-cutset matrix for the graph.




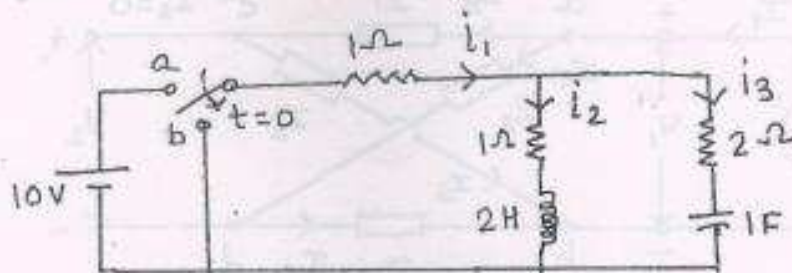- (b) Find $i_1(0+)$, $i_2(0+)$, $i_3(0+)$, $\frac{di_2}{dt}(0+)$ and $\frac{di_3}{dt}(0-)$.




10

5. (a) Find $V(t)$ for $t > 0$.


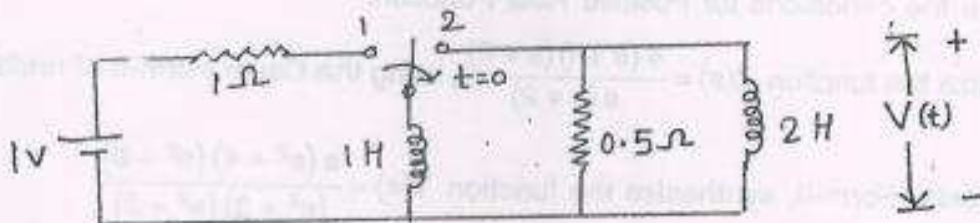


10

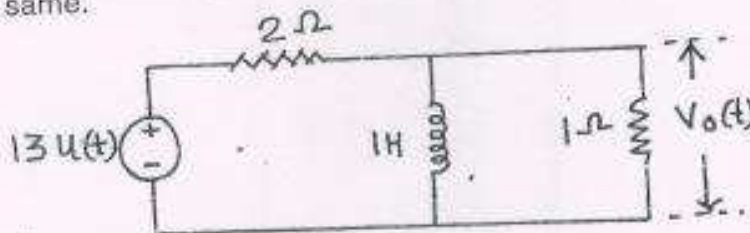- (b) (i) Find $V_0(t)$ in figure. Assume initial current to be 1A, and
(ii) Calculate $V_0(t)$ if the supply voltage becomes $5e^{-t}u(t)$. The initial condition remains the same.




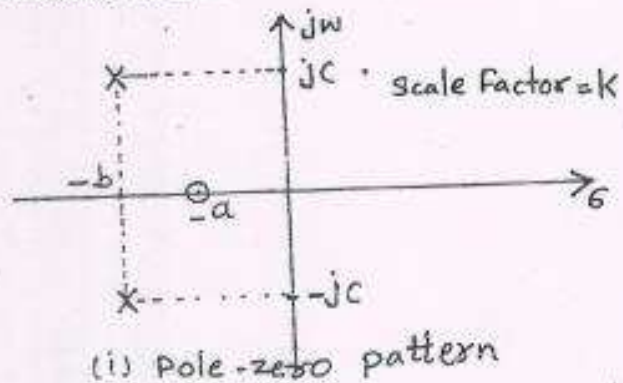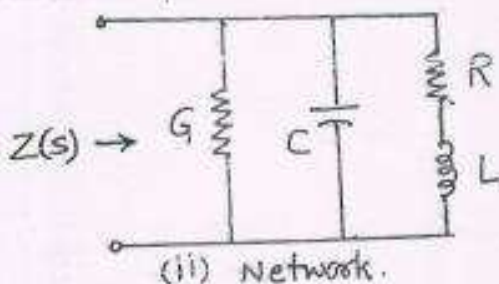6. (a) The pole-zero pattern for driving point impedance of a network and given network are shown in figures (i) and (ii) respectively. Determine an expression for $Z(s)$ and find parameters R , L , G and C as functions of a , b and c if $Z(0) = 1$.



[TURN OVER

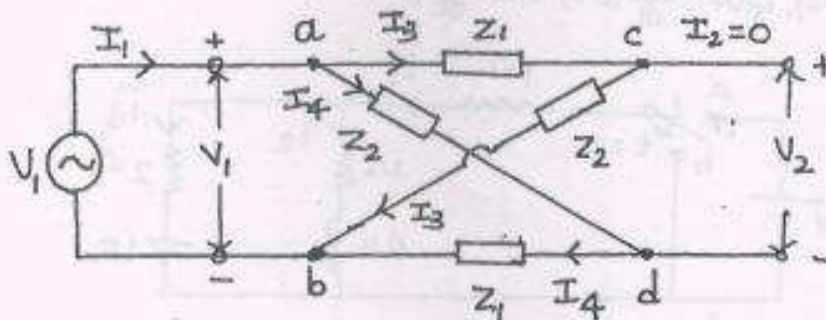(b) Calculate the Z-parameters for the network.



7. (a) Express Z-parameters in terms of Y-parameters.
(b) What are the conditions for Positive Real Function.

(c) Synthesize the function $Z(s) = \frac{4(s+1)(s+3)}{s(s+2)}$, using the Cauer Form-II of realization.

(d) Using Foster Form-II, synthesize the function $Y(s) = \frac{s(s^2+4)(s^2+6)}{(s^2+3)(s^2+5)}$.

