

A

Roll No.

Total No. of Questions : 9]

[Total No. of Printed Pages : 7

EC-309

PULSE & DIGITAL SWITCHING CIRCUITS (NEW)

(B.Tech., 5th Semester, 2055)

Time : 3 Hours

Maximum Marks : 60

:- Section A is compulsory. Attempt any *Four* questions from Section B and any *Two* questions from Section C.

Section-A Marks : 2 Each

- (a) What are the disadvantages of RL linear waveshaping circuit compared to RC circuit ?

EC-309

Turn Over

(2)

- (b) Draw V-I characteristics of an ideal diode.
- (c) Sketch diagram of a circuit that will clip all levels below -20 V and above 30 V .
- (d) What are advantages and disadvantages of symmetrical and unsymmetrical triggering?
- (e) Why step input amplifier response is not flat topped?
- (f) List uses of distributed amplifier.
- (g) How Schottky diode reduces storage time in transistor?
- (h) Describe clamping circuit theorem.
- (i) Draw transistor based circuit diagram of Schmitt trigger.
- (j) Design astable multivibrator using OP-AMP?

H-38

EC-309

Turn Over

(3)

Section-B


Marks : 5 Each

2. Obtain the response of a low pass circuit to a ramp input. Discuss the effect of RC on the response.

3. Find the output response of the circuit :

- (a) if input is a 100 V peak to peak square wave having a period of $200\text{ }\mu\text{s}$ if $L_1 = 100\text{ mh}$.

- (b) 500 mh .

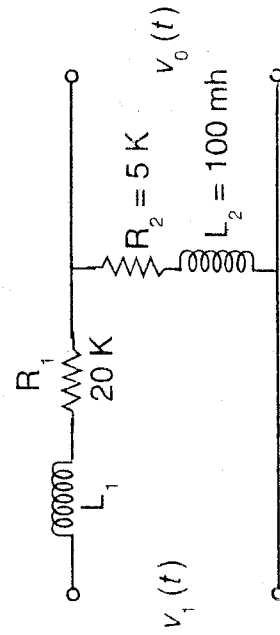

H-38

EC-309

(4)

4. At low frequencies the short circuit CE current gain β is related to short-circuit CB current gain α by :

$$\alpha = \frac{\beta}{1 + \beta}$$

Assuming this relationship remains valid at high frequencies and using $\beta = -A_v$, prove that :

$$\alpha = \frac{\alpha_0}{1 + j \left(\frac{f}{f_\alpha} \right)}$$

where

$$a_0 = \frac{h_{fe}}{1 - h_{fe}} \text{ and } f_\alpha = \frac{f_\beta}{1 - \alpha_0}$$

A_v = Current amplification under short circuit condition.


H-38

EC-309

Turn Over

(5)

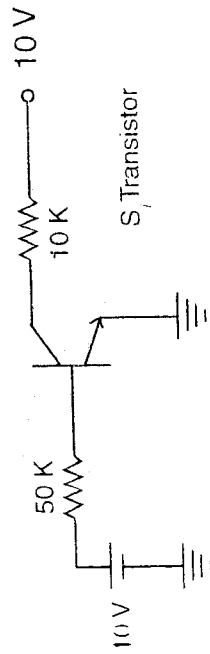5. Find the value of minimum h_{fe} required to saturate the transistor.



6. With the help of diagram, explain the operation of Bistable Multivibrator.

Section-C Marks : 10 Each

7. Explain the working of a practical Boot strap time base generator. Sketch the output voltage waveshape and calculate the slope error.

H-38

EC-309

(6)

8. (a) A fixed bias binary uses *npn* Silicon transistors with $h_k = 20$, $V_{CC} = 12\text{ V}$, $V_{BB} = 3\text{ V}$, $R_C = 1\text{ K}$, $R_1 = 5\text{ K}$, $R_2 = 10\text{ K}$.

Verify one transistor is cutoff and other transistor is saturation. Find stable currents and voltages if :

(i) $V_{CE(\text{sat})} = V_{BE(\text{sat})} = 0$

(ii) $V_{CE(\text{sat})} = 0.4\text{ V}$ $V_{BE(\text{sat})} = 0.8\text{ V}$

- (b) Find the input impedance of RC differentiating circuit. Is it same as that of RL differentiating circuit.

6,4

9. Design an Astable multivibrator using transistors and explain its action. Sketch

H-38

EC-309

H-38

EC-309

(7)

waveform at various points. Design an Astable circuit using Ge transistors to generate a square waveform of amplitude 10 V at a frequency of 10 kHz with a duty cycle of 0.4. Choose $C_1 = C_2 = 0.01\text{ }\mu\text{F}$.