

(iii) Voltage / turn

(iv) Secondary current when it supplies a load of 200 KW at 0.8 power factor lagging. [12]

Q-6. (a) Explain the principle of operation of d.c. motors. How d.c. motors are classified? What is back *emf* in d.c. motors? What is its effect? [5+5+5]

(b) How torque is produced in  $3\phi$  induction motor? [5]


Q-7. (a) Explain essentials of indicating instruments. [10]

(b) Explain principle & construction of dynamometer wattmeter. [10]

Q-8. (a) Define (i) MMF (ii) flux (iii) flux density (iv) reluctance. [4]

(b) Compare electric & magnetic ckt. [8]

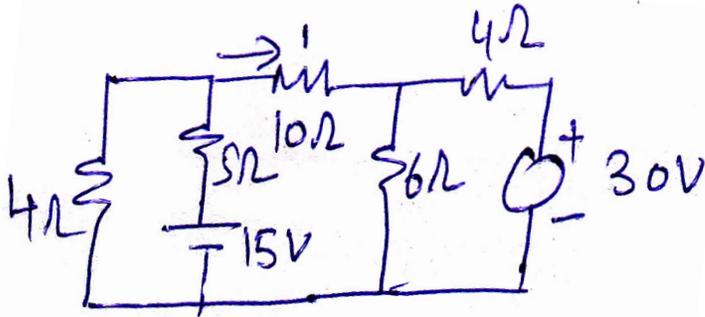(c) Using Nodal Analysis, find current  $I$  through  $10\Omega$  resistor in the figure shown below. [8]



Roll No. ....

**Lingaya's University**  
**B.Tech 1<sup>st</sup> Year (Term – III)**  
**Examination – May 2011**  
**Electrical Engineering (EL - 101)**

[Time: 3 Hours]

[Max. Marks: 100]

Before answering the question, candidate should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

**Note:** – Attempt five questions in all. All questions carry equal marks. Question no. 1 (Section A) is compulsory. Select two questions from Section B and two questions from Section C.

**Section – A**

**Q-1. Part – A**

Select the correct answer of the following multiple choice questions. [10×1=10]

- (i) Kirchoff's laws are valid for
  - (a) Linear ckt only
  - (b) Passive time invariant ckt
  - (c) Non linear ckt only
  - (d) Both linear & non linear ckt
- (ii) Which of the following is an active element in a ckt?
  - (a) Current source
  - (b) Resistance
  - (c) Inductance
  - (d) Capacitance
- (iii) Thevenin's resistance  $R_{th}$  is determined
  - (a) By short circuiting the given two terminals
  - (b) By removing resistance
  - (c) Between same open terminals as for  $V_{th}$
  - (d) Between any two open terminals


- (iv) The time period of an alternating quantity is 0.01 sec. Its frequency will be  
 (a) 25 Hz (b) 50 Hz (c) 100 Hz (d) .01 Hz
- (v) The average value of sinusoidal quantity is given by the relation.  
 (a)  $I_m/\sqrt{2}$  (b)  $0.707 I_m$   
 (c)  $2I_m/\pi$  (d) None of the above
- (vi) The peak factor of an alternating current is given by the relation  
 (a)  $I_{rms}/I_{av}$  (b)  $I_m/I_{rms}$   
 (c)  $I_{av}/I_{rms}$  (d)  $I_{rms}/I_m$
- (vii) The operator  $j$  has a numerical value of  
 (a)  $\sqrt{-1}$  (b)  $\sqrt{+1}$  (c)  $-1$  (d)  $1$
- (viii) Induction wattmeter can be used to measure  
 (a) AC power (b) DC power  
 (c) AC & DC power (d) None of the above
- (ix) The transformation ratio of a transforms is  
 (a)  $I_2 / I_1$  (b)  $N_1 / N_2$  (c)  $N_2 / N_1$  (d)  $E_1 / E_2$
- (x) The rotating part of a d.c. machine is called the  
 (a) Yoke (b) Field  
 (c) Armature (d) Stator

### Q-1. Part – B

- (a) State & explain superposition theorem. [5]  
 (b) Define Q factor for series resonant ckt and express it in the terms of circuit parameters. [5]
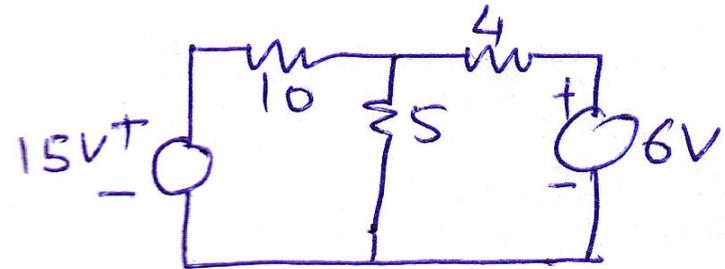
### Section – B

- Q-2. State Thevenin's Theorem & give a proof. Apply this theorem to calculate the current through the 4Ω resistor of ckt given below. [6+14]



- Q-3. (a) Define amplitude, frequency, *rms* value, phase angle, average value of series R-L-C series ckt. [5]  
 (b) A coil of resistance 15Ω and inductance 0.05H is connected in parallel with a non inductive resistor of 20Ω. Find:  
 (i) The current in each branch ckt.  
 (ii) The total current supplied and  
 (iii) Phase angle of the combination,  
 when a voltage of 230V at 50 Hz is applied. Draw relevant phasor diagram. [15]
- Q-4. Three 100Ω resistances are connected in (a) star (b) delta across a 440V, 3ϕ line, calculate the line & phase current and power taken from the mains in each case. Find also what values would be for each case, if one of the resistances were disconnected? [20]

### Section – C

- Q-5. (a) Explain the working principle of a transformer & derive its *emf* equation. [8]  
 (b) 3300 / 300 V single phase 300 KVA transformer has 1100 primary turns, find:  
 (i) Transformation ratio  
 (ii) Secondary turns