

- N.B. :** (1) Question No. 1 is **compulsory**.  
 (2) Attempt any **four** questions out of remaining **six** questions.  
 (3) Assume **suitable** data and state it **clearly**.

1. (a) Convert  $(157.63)_8$  into decimal, binary and hexadecimal system. 4
- (b) Simplify using boolean laws : 4  

$$\overline{\overline{AB} + \overline{A} + AB}$$
- (c) Design full adder using half adders. 4
- (d) State and prove De Morgan's theorem. 4
- (e) Implement the boolean function with NAND – NAND logic 4  

$$F(A, B, C) = \sum m(0, 1, 3, 5)$$
2. (a) Using boolean laws, prove NAND and NOR gates as universal gates. 10
- (b) Draw 3-bit binary up-down counter and explain the operation. 10
3. (a) What is race condition ? How it is overcome in Master-slave J-K flip flop ? Explain. 10
- (b) State truth table of 3 bit gray to binary conversion and design using 3 : 8 decoder and additional gates. 10
4. (a) Simplify using K-map,  $f(A, B, C, D) = \pi M(0, 2, 3, 6, 7, 8, 9, 12, 13)$  Write simplified SOP and POS equations and draw logical diagram using NAND gates only. 10
- (b) Simplify the function using Quine McClusky method.  $f(A, B, C, D) = \sum m(4, 5, 8, 9, 11, 12, 13, 15)$  Draw the logical diagram using NAND gates. 10
5. (a) Draw a 2-input TTL NAND gate and explain its operation. 10
- (b) Simplify  $F(P, Q, R, S) = \pi M(3, 4, 5, 6, 7, 10, 11, 15)$  and implement using minimum no. of gates. 10
6. (a) Design MOD-6 synchronous counter and explain its operation. 10
- (b) Draw 4 bit universal shift register and explain its operation. 10
7. Write short notes on :- 20
  - (a) Multiplexer and demultiplexer
  - (b) ALU
  - (c) Asynchronous vs synchronous counter
  - (d) Octal to binary encoder.