

DECEMBER 2006

Code: A-09

Subject: ANALOG & DIGITAL ELECTRONICS

Time: 3 Hours

Max. Marks: 100

NOTE: There are 9 Questions in all.

- **Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.**
- **Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.**
- **Any required data not explicitly given, may be suitably assumed and stated.**

**Q.1 A. Choose the correct or best alternative in the following:
(2x10)**

- a. The unity gain bandwidth of 741 OPAMP is typically
- (A) 4 MHz. (B) 2 MHz.
(C) 6 MHz. (D) 1 MHz.
- b. The conversion time of a dual-slope ADC is typically in the range of
- (A) 5 to 10 ns. (B) 10 to 100 ns.
(C) 100 to 200 ns. (D) 2 to 3 ns.
- c. In a transistor switch, the voltage change from base-to-emitter which is adequate to accomplish the switching is only about
- (A) 0.2 V. (B) 0.4 V.
(C) 0.1 V. (D) 0.5 V.
- d. Worst case ECL noise margins are approximately
- (A) 100 mV. (B) 50 mV.
(C) 250 mV. (D) 400 mV.
- e. A certain multiplexer can switch one of 32 data inputs to its output. How many different inputs does this MUX have?
- (A) 30 data inputs & 5 select inputs.
(B) 32 data inputs and 4 select inputs.
(C) 32 data inputs and 5 select inputs.

Q.3 a. What are the advantages of an active filter? Draw the circuit of a second order Low-pass active filter and explain its functioning. (11)

b. Design a unity gain Low-pass active filter to meet the following specifications:
Roll off rate = - 40 dB/decade
Passband as flat as possible
Cut off frequency = 2 KHz,
dc gain = 5. (5)

Q.4 a. Write the equation for the squared magnitude response of an N^{th} order Chebyshev filter with equiripple passband and monotonic stopband and explain the typical magnitude response characteristic for the above filter. (8)

b. Explain how a transistor can be used as a switch to connect and disconnect a load R_L from the source V_{CC} . (8)

Q.5 a. What is the advantage of using Schottky transistors in a TTL gate with totempole output? Draw the circuit of a 2-input Schottky TTL gate and explain its features? (12)

b. What are the advantages and disadvantages of ECL? (4)

Q.6 a. What is a full adder? Write the schematic and truth table of a full adder. Describe how a full adder can be implemented using EX-OR/OR/AND gates. (11)

b. What do you mean by a data selector? Draw the logic circuit for a two-input multiplexer using basic gates and briefly explain its operation. (5)

Q.7 a. What is an ADC? Draw the schematic of an ADC that uses a binary counter and explain its operation. (10)

b. The parameters of a counter type ADC are given below:

Clock frequency = 1 MHz,
Comparator threshold = 0.1 mV,
Full scale output of DAC used = 10.23,
DAC input = 10-bits,

Find the following:

- (i) The digital equivalent obtained for an analog input of 3.728 V.
- (ii) The conversion time.
- (iii) The resolution of the converter. (6)

- Q.8** a. What is a flip-flop (FF)? What are the other names by which it is known? How many outputs a flip-flop has and what are they called? What are the two types of inputs does a clocked FF have? (7)
- b. What is a shift register? With a neat schematic explain how J-K flip-flops can be arranged to operate as a four-bit shift register. (9)
- Q.9** a. How are digital circuits employing MOSFETS categorised? Define each one of them and mention their important features. How does CMOS internal circuitry differ from N-MOS? (8)
- b. What is meant by of the term RAM? What is its meaning? How is it used in computers and what is its major disadvantage? Distinguish between a Static RAM and a Dynamic RAM. (8)