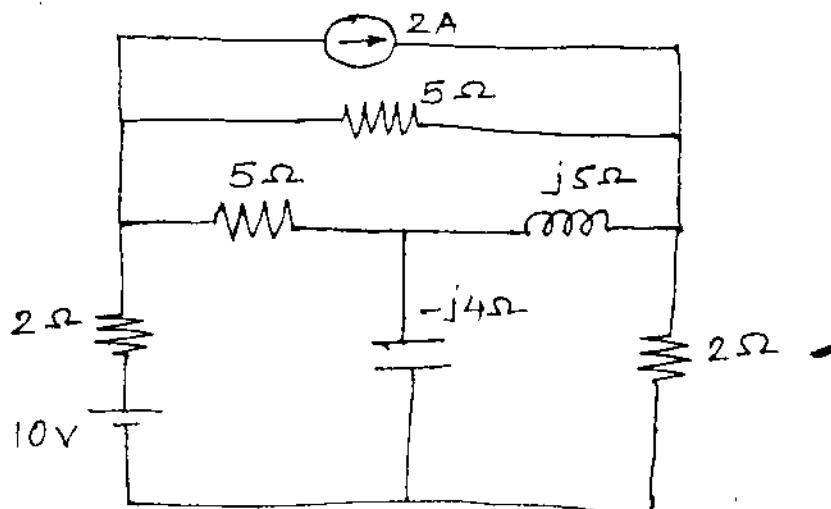


- 4.B.: (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assume suitable data if necessary.

1. (a)



10

- (i) Write down Tie-Set matrix
 (ii) Network equilibrium equation in matrix form using KVL.
 (b) The reduced incidence matrix of an oriented graph is—


10

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

- (i) Draw the graph
 (ii) Write Tie-set and cut-set matrix.
 (iii) How many no. of trees are possible ?


2. (a) Using superposition Theorem, Find I_x .

10

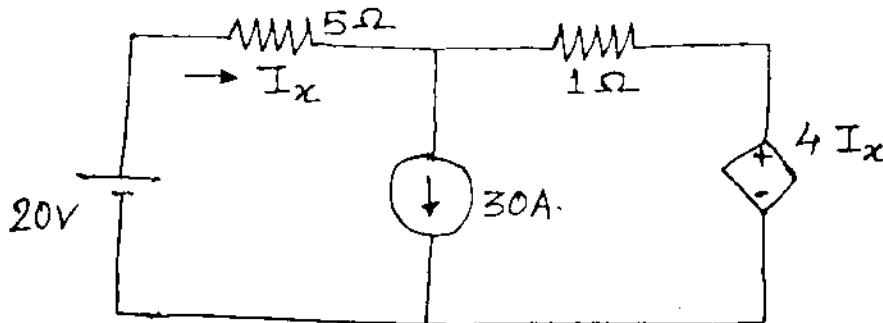


(b) Using Mesh Analysis, Find current in 5 Ω resistance.

10

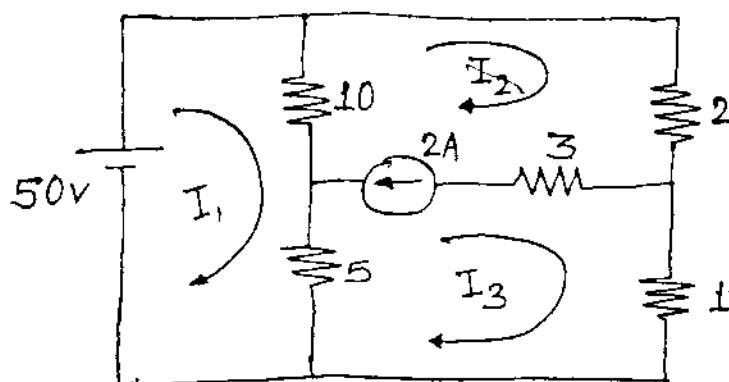


[TURN OVER]

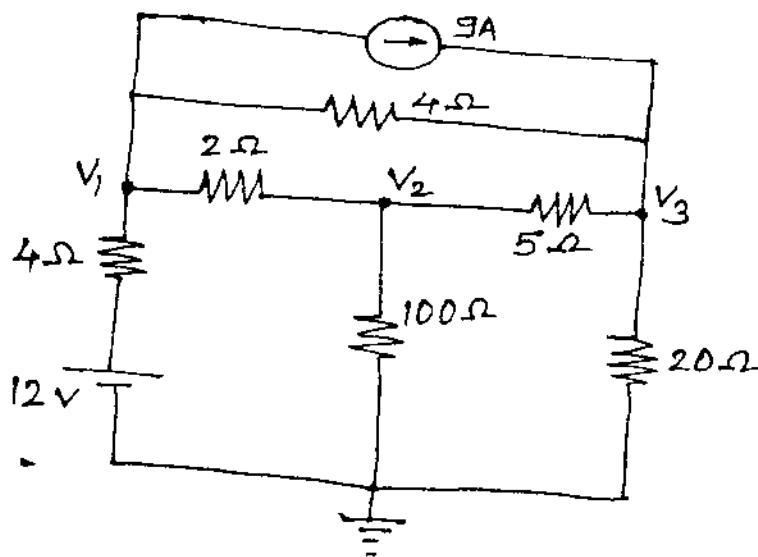
3. (a) Using nodal analysis, find voltage across $5\ \Omega$ resistance.



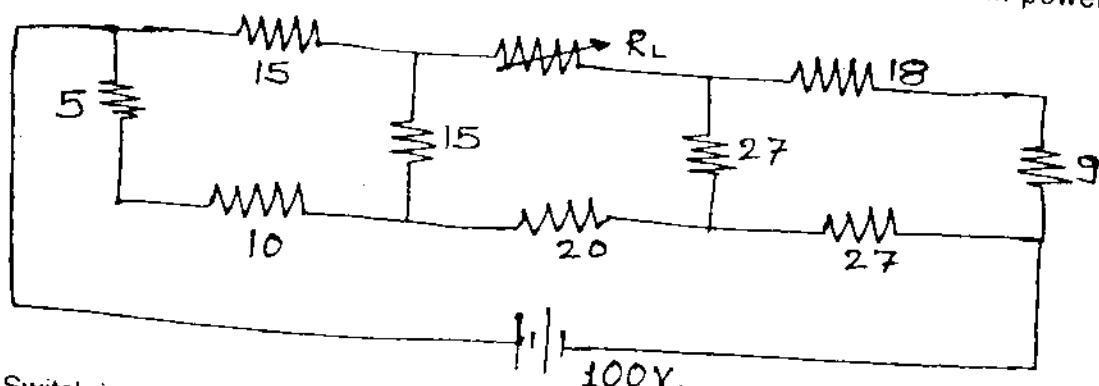
- (b) Find the value of R_L for maximum power and calculate the maximum power.



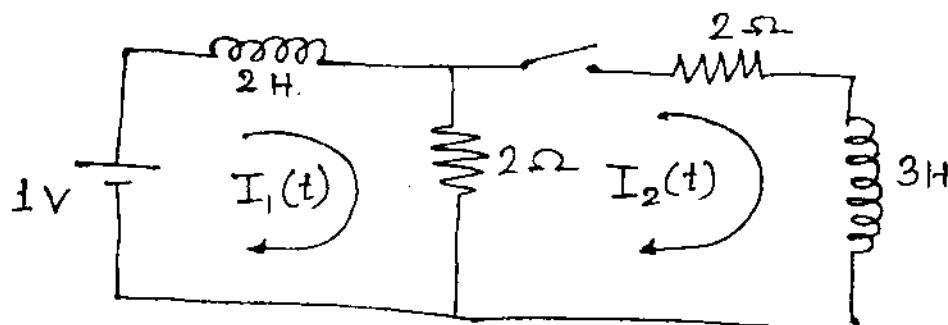4. (a) Switch is closed at $t = 0$, the steady state being reached before $t = 0$. Determine current through the inductor of 3 H.



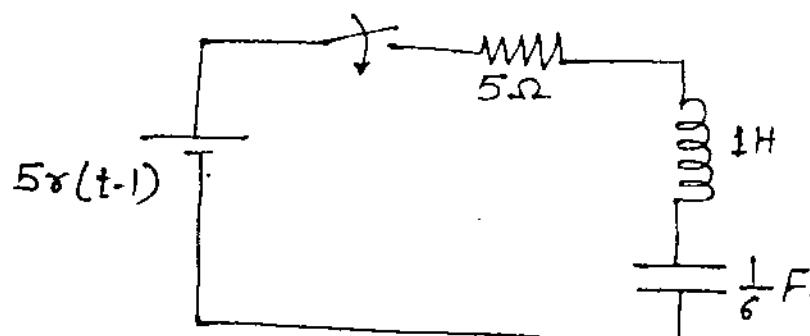- (b) Determine the current $i(t)$, when the switch is closed at $t = 0$ with zero initial condition.



(b)

7. (a) D

+

V

-


-

V₁


Find

(b) Curr
netw

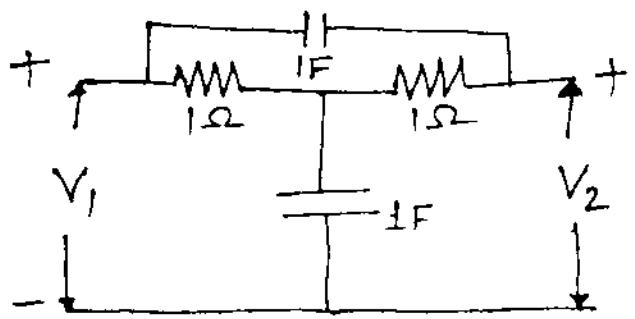
5. (a) Test whether $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$ is positive real function. 10
 (b) State Maximum power transfer theorem and give the proof. 5
 (c) Explain the terms : (i) Time constant (ii) Initial condition. 5
6. (a) Determine $Z_{11}(s)$, $Z_{12}(s)$, $G_{12}(s)$. 10



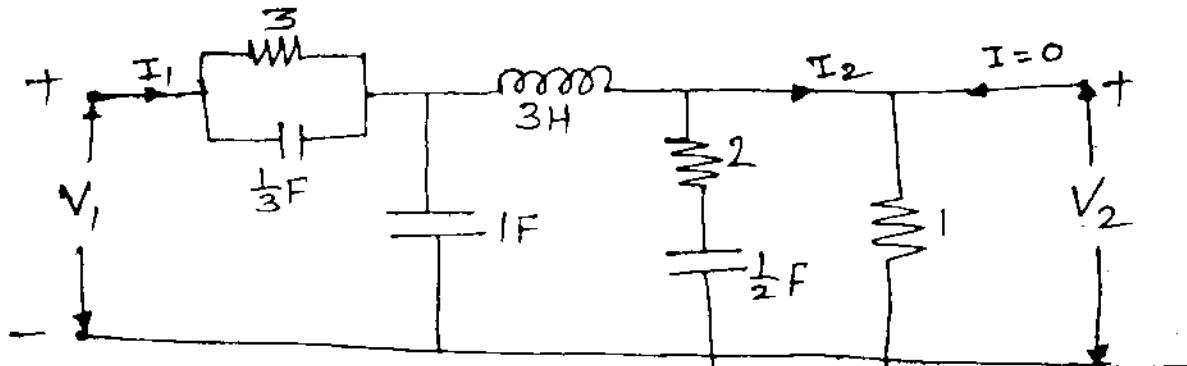- (b) Determine $\frac{V_2}{V_1}, \frac{I_2}{I_1}, \frac{V_2}{I_1}, \frac{V_1}{I_2}$ 10



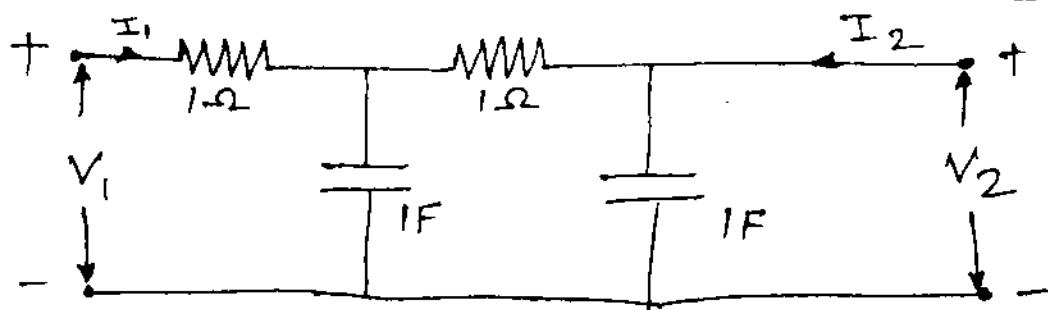7. (a) Determine short-circuit admittance parameters ($Y_{11}, Y_{12}, Y_{21}, Y_{22}$). 10



- (b) Currents I_1 and I_2 entering at Port 1 and Port 2 respectively of two port network are given by following equations. 10

$$I_1 = 0.5 V_1 - 0.2 V_2$$

$$I_2 = -0.2 V_1 + V_2.$$

Find Y , Z and $ABCD$ parameters.