

EC-309 PULSE AND DIGITAL SWITCHING CIRCUITS

(B.Tech., 5th Semester, 2125)

Time : 3 Hours

Maximum Marks : 60

Note : Section A is compulsory. Attempt any four questions from Section B and any two questions from Section C. Assume missing data.

Section - A

1. (a) Define Linear wave shaping and give examples.
- (b) Indicating salient points distinguish between compensate and uncompensated attenuators.
- (c) What is expression of time constant (τ) for an RC-circuit with $R=500\Omega$ and $C=20\text{ }\mu\text{F}$? Show that the unit of τ is second.
- (d) Elaborate the term "low-frequency compensation" in amplifier.
- (e) Explain the term "distributed amplifier".
- (f) Show the circuit diagram of a transistor being used as switch.
- (g) What is clipping circuit? Give various configurations of clipping circuits.
- (h) What is ringing circuit? Sketch a ringing circuit arrangement with non zero initial conditions.
- (i) Distinguish between monostable multivibrators and bistable multivibrators.
- (j) List applications for voltage and current sweep generators.

Section - B

2. Draw the highpass R-C circuit. Derive for step-voltage response of this circuit and show the input-output characteristics of this circuit.

3. Consider an R-C circuit shown in Fig. 1. A symmetrical square wave shown in Fig. 2 is applied as input to this circuit. Obtain an expression for peak to peak value of the output voltage. What is peak to peak voltage for $\tau = RC$.


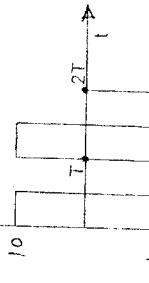


Fig. 2. A sym. Square wave of voltage (V_i)

4. What is meant by frequency response of an amplifier? Show plots for frequency and time-response of a R-C coupled a.c. amplifier.
5. Discuss behaviour of MOS transistor as a switch. Also enumerate some applications of MOS transistors.
6. With the help of basic circuit diagram discuss the working of a Schmitt trigger circuit. Also show how it is considered as a bistable circuit.

Section - C

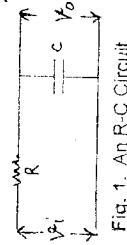7. Discuss procedures of realisation of multivibrators using transistors
8. Give a detail description on switching characteristics of electronic switches. Also explain the terms (i) delay time (ii) rise time (iii) storage time & (iv) fall time.
9. Write technical notes on
 - (i) User of Schotkey Diode
 - (ii) Sweep generators.



$(2 \times 10 = 20)$

$(10 \times 2 = 20)$

$(2 \times 10 = 20)$