

Con. 1714-06.

(REVISED COURSE)


TV-7965

(3 Hours)

[ Total Marks : 100

- N.B. (1) Question No. 1 is compulsory.  
 (2) Answer any four out of remaining six questions.  
 (3) Assume suitable data wherever required.

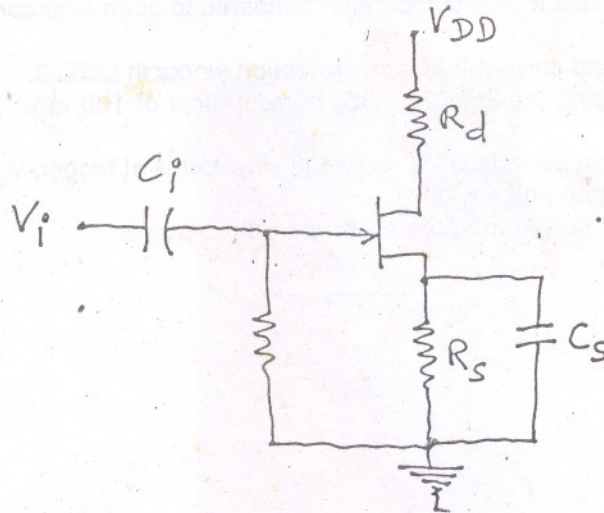1. (a) The amplifier of figure utilizes an n-channel FET for which  $V_p = -2.0$  V,  $g_{m0} = 1.60$  mA/V and  $I_{DSS} = 1.65$  mA. 12  
 It is desired to bias the circuit at  $I_D = 0.8$  mA using  $V_{DD} = 24$  V. Assume  $r_d \gg R_d$ .  
 Find — (i)  $V_{GS}$ , (ii)  $g_m$ , (iii)  $R_S$ , (iv)  $R_d$ , such that voltage gain is atleast 20 dB, with  $R_S$  by passed with a very large capacitance.



- (b) What method is used to bias an FET against device and temperature variation? Explain how this is effective. 8

Con. 1714-06.


(REVISED COURSE)

TV-7965

(3 Hours)


[ Total Marks : 100

- N.B. (1) Question No. 1 is compulsory.  
 (2) Answer any four out of remaining six questions.  
 (3) Assume suitable data wherever required.
1. (a) The amplifier of figure utilizes an n-channel FET for which  $V_p = -2.0$  V,  $g_{m0} = 1.60$  mA/V and  $I_{DSS} = 1.65$  mA. 12  
 It is desired to bias the circuit at  $I_D = 0.8$  mA using  $V_{DD} = 24$  V. Assume  $r_d \gg R_d$ .  
 Find — (i)  $V_{GS}$ , (ii)  $g_m$ , (iii)  $R_S$ , (iv)  $R_D$ , such that voltage gain is atleast 20 dB, with  $R_S$  bypassed with a very large capacitance.

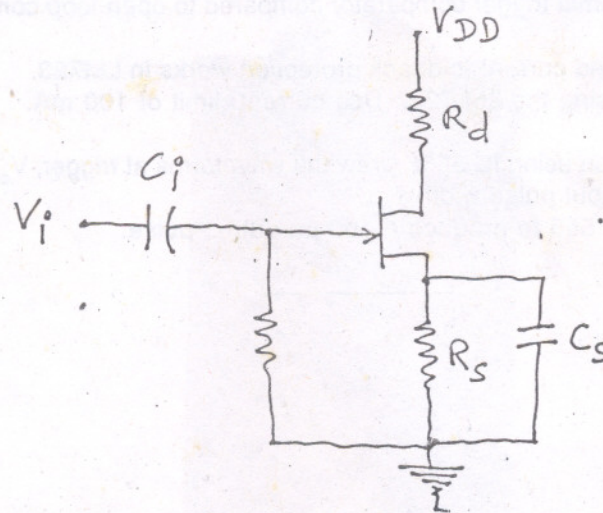

- (b) What method is used to bias an FET against device and temperature variation? Explain how this is effective. 8

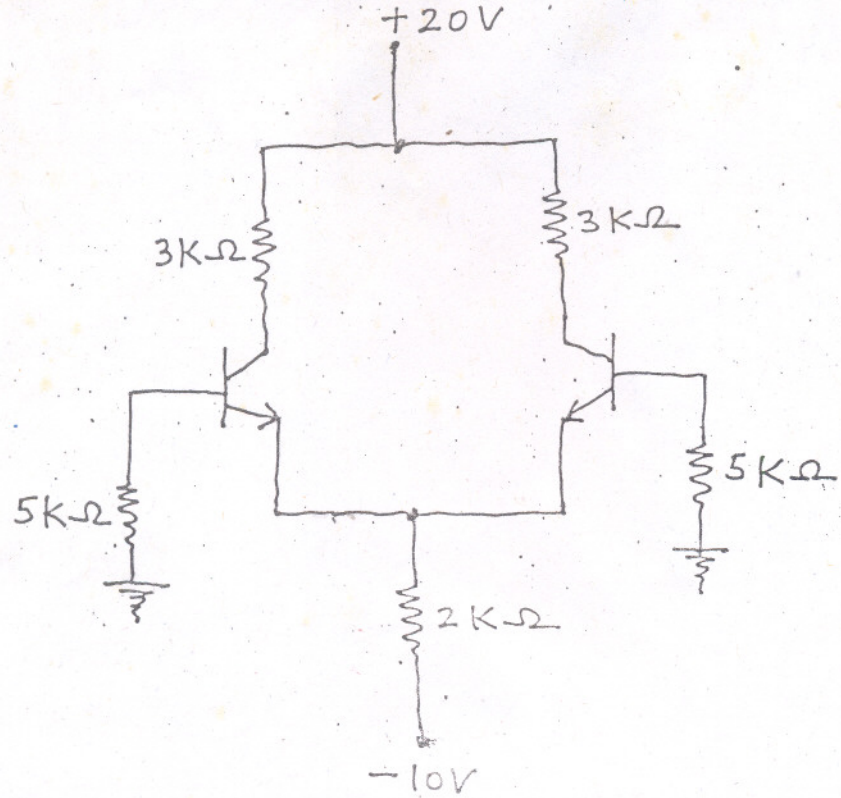2. (a) Draw and explain current-mirror circuit.  
(b) For the circuit shown in **figure**, determine the following :—
- (i)  $I_E, I_{E1}, I_{E2}$
  - (ii) Collector to ground voltage
  - (iii) base-voltage.



Given —  
 $V_{BE} = 0.7 \text{ V}$   
 $\beta = 100$   
both the transistors are matching.

[ TURN OVER

## Con. 1714-TV-7965-06.

2

3. (a) Explain the difference between the integrator and differentiator and give one application of each. 8  
 (b) What are the advantages of using an instrumentation amplifier versus simple OP-AMP differential amplifier ? 12  
 Explain how to construct basic instrumentation amplifier from general purpose OP-AMP.  
 Derive an expression for  $V_{out}$
4. (a) Draw circuit diagram of second order Butterworth active filter using OP-AMP. Give its frequency response curve. Give practical application of this filter. 15  
 (b) Compare active and passive filters. 5
5. (a) Draw and explain phase-shift oscillator using OP-AMP. Derive expression for frequency of oscillation and gain factor  $\beta$  of ladder network. 12  
 (b) Give the advantages of Schmitt trigger comparator compared to open-loop comparator using OP-AMP. 8
6. (a) Explain how current-limit and current foldback protection works in LM723. 8  
 (b) Design a +9 V regulator using the LM 723. Use current limit of 100 mA. 12
7. (a) Explain monostable operation using IC 555. Draw the waveforms at trigger,  $V_{out}$ , and across capacitor. 15  
 Derive the equation for output pulse width  $T_{out}$ .  
 (b) Design the circuit using IC 555 to produce a 100  $\mu$ s output pulse. 5
-