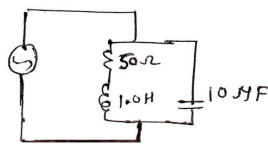


A coil is connected in series with a non-inductive resistance of  $30\Omega$  across a  $240\text{V}$ ,  $50\text{Hz}$  supply. The reading of a voltmeter across the coil is  $180\text{V}$  and across the resistance is  $130\text{V}$ . Calculate

- (i) Power consumed by coil  
(ii) Power factor of whole circuit (2+8=10)  
(b) Compare a series resonance with parallel resonance: (4+6=10)  
For the circuit given below, determine

- (i) Resonant frequency  
(ii) Total impedance of circuit at resonance  
(iii) Band width  
(iv) Quality factor



Q-7. (a) Compare an a.c. system with d.c. system. A balanced 3 phase star connected load of  $240\text{ kW}$  takes a leading current of  $170\text{ amperes}$ , when connected across a 3 phase  $2200\text{ volts}$ ,  $50\text{ Hz}$  supply. Obtain the values of the resistance, impedance and capacitance of the load per phase and also calculate the power factor of the load. (3+7=10)

(b) Draw the phasor diagram of line currents and phase currents in a mesh connected 3 phase system. Three similar resistance connected in star draw a line current of  $10\text{ A}$  from a  $400\text{V}$ , 3 phase mains. To what value should the line voltage be changed to obtain the same line current with the resistances connected in delta? (4+6=10)

Q-8. (a) Define all day efficiency of a transformer.

In a  $100\text{ KVA}$ , 1 phase  $6600/230\text{V}$  transformer, the iron losses and full load copper losses were found to be as  $1000\text{ watts}$  and  $1300\text{ watts}$  respectively. Calculate efficiency at half load and  $0.6$  power factor. Determine maximum efficiency and corresponding load. (1+4=5)

(b) The primary and secondary windings of a  $80\text{ KVA}$ ,  $13.2\text{ KV} / 250\text{V}$  single phase transformer have resistances of  $20\Omega$  and  $0.04\Omega$  respectively. The total leakage reactance is  $70\Omega$  as referred to the primary winding. Find full load regulation at a power factor of  $0.8$  lagging. (5)

(c) Write short notes on following: (5x2=10)

- (i) Construction of a single phase transformer.  
(ii) Phasor diagram of a transformer for an inductive load.

Roll No. ....

**Lingaya's University, Faridabad**  
**B.Tech. 1<sup>st</sup> Year (Term – I)**  
**Examination – October, 2010**  
**Electrical Engineering (EL-101)**

**Time: 3 Hours**

**Max. Marks: 100**

Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard will be entertained after the examination.

**Note:** All questions carry equal marks. Attempt five questions. Question 1 is compulsory. Select two questions from Section B & two from Section C.

**SECTION – A**

**Q-1. Part-A**

Select the correct answer of the following multiple choice questions.

(1x10=10)

(i) KVL states that in a closed circuit of an electric network:

- (a)  $\sum E=0$  (b)  $\sum I=0$  (c)  $\sum v=0$  (d)  $\sum E+ \sum V=0$

(ii) A network which does not have either voltage source or current source is called:

- (a) active network (b) passive network  
(c) resistive network (d) dummy network

(iii) If the effective value of the sinusoidal voltage is  $111\text{ volts}$ . Its average value will be:

- (a)  $100\text{ V}$  (b)  $123.21\text{ V}$  (c)  $156.51\text{ V}$  (d) none of the above

(iv) Peak factor of an alternating current is given by relation

- (a)  $I_{\text{rms}} / I_{\text{avg}}$  (b)  $I_m / I_{\text{rms}}$  (c)  $I_{\text{avg}} / I_{\text{rms}}$  (d)  $I_{\text{rms}} / I_m$

(v) In a balanced three phase, star connected system, the relation between phase voltage  $V_{\text{ph}}$  and line  $V_L$  is :

- (a)  $V_{\text{ph}} = \sqrt{3} V_L$  (b)  $V_{\text{ph}} = 0.577 V_L$  (c)  $V_{\text{ph}} = \frac{V_L}{\sqrt{2}}$  (d) none of these

(vi) A 3 phase load is said to be a balanced load, if all the three phases have the same:

(a) impedance (b) power factor (c) both a and b (d) none of above

(vii) MMF is analogous to:

(a) electric current in electric circuit (b) current density in conductor  
(c) electromotive force (d) voltage

(viii) If the supply frequency to the transformer is increased the iron loss:

(a) increased not change (b) will be zero (c) will increase (d) will decrease

(ix) Synchronous speed of a synchronous machine is given as:

(a)  $N_s = 120 f / p$  (b)  $N_s = 120 p / f$  (c)  $N_s = 120 / fp$  (d)  $N_s = 1200 / fp$

(x) Which of following electrical machine has the highest efficiency:

(a) d.c. generator (b) a. c. generator (c) Transformer (d) induction motor.

### Part-B

(a) State Kirchhoff's current and voltage laws. Explain with suitable examples. (5)

(b) What do you mean by series or voltage resonance? Explain it with the graphical representation in an R-L-C series circuit (5)

### Section – B

Q-2. (a) What are the similarities and dissimilarities in magnetic and electric circuit? (6)

(b) Define the following terms: (1+5=6)

(i) Reluctance (ii) permeance (iii) MMF  
(iv) permeability (v) magnetic flux density (vi) magnetic circuit

(c) What is hysteresis loss? Explain B-H curve and how magnetic calculations from B-H curve are done. State the importance of hysteresis loop. Draw the hysteresis loop for hard steel, silicon steel and wrought iron. (8)

Q-3. (a) What is the significance of back emf in d.c. machines. Derive the expression for it? (2+4=6)

(b) What is function of commutator in a d.c. motor? How d.c. motors are classified? Draw the diagram with required equations of induced emf for every case. (1+5=6)

(c) Write short notes on:

(i) Constructional features of a d.c. machine

(ii) principle of operation of a 3 phase induction motor. (4x2=8)


Q-4. (a) Differentiate between recording and integrating type of instruments. Give two examples of each of these instruments. (4)

(b) Explain principle & working of single phase induction type energy meter. (8)


(c) Explain in brief the working principle of permanent magnet moving coil instrument. Why is the scale linear? (8)
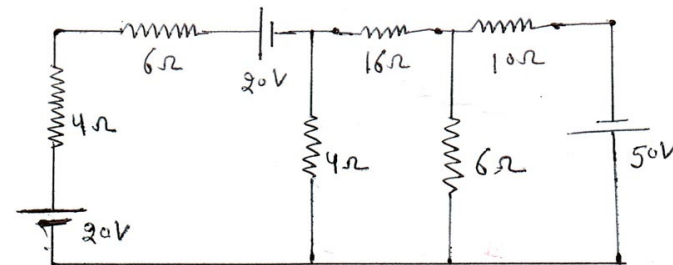
### Section- C

Q-5. (a) Define conductance and conductivity of the conductor material. Using nodal analysis method find the current through  $16 \Omega$  resistor in the circuit given below: (2+8=10)



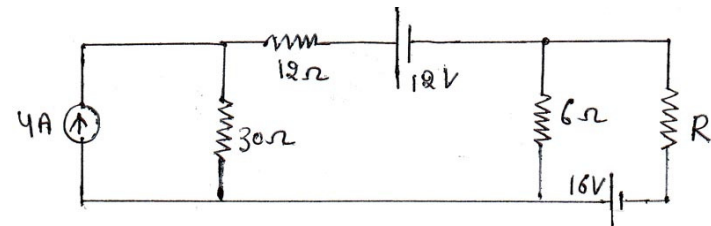(b) What is maximum power transfer theorem? Where this theorem is used? Find the value of resistance R to have maximum power transfer in the circuit given below. Also obtain the amount of maximum power. (4+6=10)



Q-6. (a) What do you understand by phase lag and phase lead? Explain with the help of example.