

- Q-7. (a) A balanced delta connected load of $8 + j6$ ohm per phase is connected to a 3-phase 230 V, 50 Hz supply. Find line current, power factor, reactive power and total volt-amperes. [7]
- (b) The input to a 3-phase induction motor running on no-load was measured by two wattmeter method. The readings of wattmeter were 1.2 KW and 6 KW, the first reading having been obtained by reversing the current coil connection. Find power input to the motor & power factor. [7]
- (c) Explain methods of power factor improvement. [6]
- Q-8. (a) A 2 ohm resistance, 0.125 F capacitance and 3 H inductance are connected in series across a voltage $v(t) = 12 \sin(2t + 30^\circ)$. Find impedance, current, power factor and active power. [10]
- (b) When voltage $v = 10 \sin(500t - 60^\circ)$ is applied to a series A.C. circuit, the current is $i = 6 \sin(500t - 10^\circ)$. Find: (i) power factor (ii) apparent power (iii) active power (iv) reactive power. [10]

Roll No.

Lingaya's University
B.Tech. 1st Year (Term – II)
Examination – Feb 2011
Electrical Engineering (EL - 101)

[Time: 3 Hours]

[Max. Marks: 100]

Before answering the question, candidate should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note: – Attempt five questions in all. All questions carry equal marks. Question no. 1 is compulsory. Select two questions from Section B and two questions from Section C.

Section – A

Q-1. Part – A

Select the correct answer of the following multiple choice questions. [10x1=10]

- (i) To determine the polarity of voltage drop across a resistor, it is necessary to know the
 (a) Value of resistance
 (b) Direction of current in the resistance
 (c) Value of current in the resistance
 (d) Value of resistance & direction of current
- (ii) The peak value of sine wave is 100. The *rms* value is
 (a) 70.7 (b) 50 (c) 35.35 (d) 100
- (iii) The internal resistance of a circuit is 16 ohm. For maximum power transfer, the load resistance should be
 (a) 4 ohm (b) 6 ohm (c) 16 ohm (d) 20 ohm
- (iv) Open circuit test of a transformer provides
 (a) Copper loss (b) Core loss
 (c) Copper & core loss (d) None of these
- (v) Value of slip in an induction motor is
 (a) $N - N_s$ (b) $N_s - N$ (c) N_s (d) N

- (vi) Reluctance in a magnetic circuit is analogous to
 - (a) Conductance
 - (b) Inductance
 - (c) Capacitance
 - (d) Resistance
- (vii) A moving coil ammeter is used to measure
 - (a) A.C. & D.C. current
 - (b) Only A.C. current
 - (c) Only D.C. current
 - (d) None of these
- (viii) The maximum value of power factor in A.C. circuit is
 - (a) 0
 - (b) 1
 - (c) Between 0 & 1
 - (d) -1
- (ix) A material for permanent magnet should have
 - (a) High retentivity
 - (b) High permeability
 - (c) Low hysteresis loss
 - (d) High hysteresis loss
- (x) Core of a transformer is laminated to reduce
 - (a) Hysteresis loss
 - (b) Eddy current loss
 - (c) Hysteresis & eddy current loss
 - (d) Copper loss

Part – B

- (a) State & explain Norton's theorem. [5]
- (b) Derive *emf* equation of a transformer. [5]

Section – B

- Q-2. (a) Draw and explain equivalent circuit of a transformer. [6]
- (b) Explain principle, construction & working of a transformer. [7]
- (c) Explain efficiency of a transformer. Derive the condition for maximum efficiency. [7]
- Q-3. (a) Explain the principle of operation of three phase induction motor.
- (b) Explain various methods of speed control of D.C. motor. [2x10=20]
- Q-4. (a) Explain principle, construction & working of energy meter.
- (b) Explain principle, construction & working of moving coil ammeter. [2x10=20]

Section – C

- Q-5. (a) A 4700 Ω resistor and 2 micro-farad capacitor are connected in parallel across a 240V, 60 Hertz source. Determine circuit impedance and line current. [10]
- (b) Determine Thevenin's equivalent circuit which may be used to represent the given network at the terminal AB (figure – 1) and find the current in branch AB. [10]

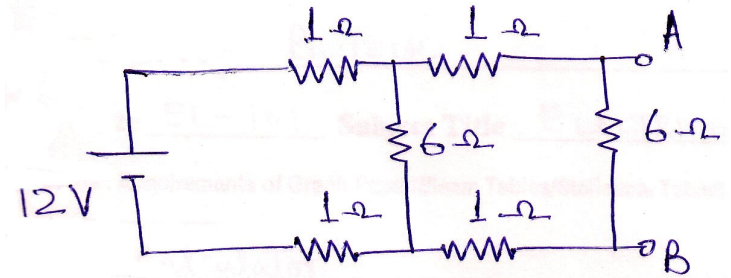


Fig- 1

- Q-6. (a) Define following:-
 - (i) Permeance
 - (ii) Reluctance
 - (iii) Permeability
 - (iii) Reluctivity
 - (v) Magnetic field intensity
 [5]
- (b) Explain hysteresis phenomenon. [6]
- (c) An iron ring is composed of three sections. The cross-sectional area is 0.001 sq. m. for each section. The mean arc length are $L_a = 0.3$ m, $L_b = 0.2$, $L_c = 0.1$ m. An air gap of 0.1 mm is cut in the ring. Relative permeability for section a, b and c are 5000, 1000 and 10000 respectively. Given $\mu_0 = 4\pi \times 10^{-7}$. Find reluctances of sections including air-gap. [9]