

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 02

B.Tech. (Sem. - 4th)

ANALOG ELECTRONICS

SUBJECT CODE : EC - 202

Paper ID : [A0306]

[Note : Please fill subject code and paper ID on OMR]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 × 2 = 20)

- a) What is PIV of a diode in a rectifier circuits?
- b) What is a Zener diode? Draw its V-I characteristics?
- c) Why are two transistors used in a Wein Bridge Oscillator?
- d) What is meant by 'Cross-over Distortion'?
- e) State Barkhausen's Criteria for Oscillation.
- f) Explain the effect of coupling capacitor on low frequency response of BJT amplifiers.
- g) What are multi-stage amplifiers?
- h) Discuss the effect of Emitter bypass capacitor on low frequency response of BJT amplifiers.
- i) Define : Gain Margin.
- j) Why do we need three RC networks for a phase - shift oscillator?

Section - B

(4 × 5 = 20)

- Q2)** An amplifier has voltage gain with feedback of 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2% , determine the values of open loop gain A and feedback ratio β .

