

[Total Marks : 100]

S.E / EXTC - Sem - IV

(3 Hours)

N.B. (1) Question No. 1 is **compulsory**.(2) Solve any **four** questions from the remaining.(3) Assume suitable data if **necessary** and mention the **same** in answer-sheet.Electronic Devices & Circuit - II

20

1. Solve any **four** :—


- Explain how to improve CMRR in differential amplifier.
- Explain principle of operation of oscillator.
- State the importance of frequency response in amplifier circuits. Why at low and at high frequencies gain of CE amplifier is low.
- What are the advantages of negative feedback ?
- Differentiate between Small signal and Large signal amplifiers.

2. Design a two stage RC coupled BJT amplifier to meet the following 20 specifications :—

$$A_v \geq 5000, S_{IO} \leq 10, f_L \leq 20 \text{ Hz}, V_o = 2.5 \text{ V} \text{ and } V_{CC} = 12 \text{ V}.$$

For designed circuit calculate A_v , R_i and R_o .

3. For the circuit shown in figure.

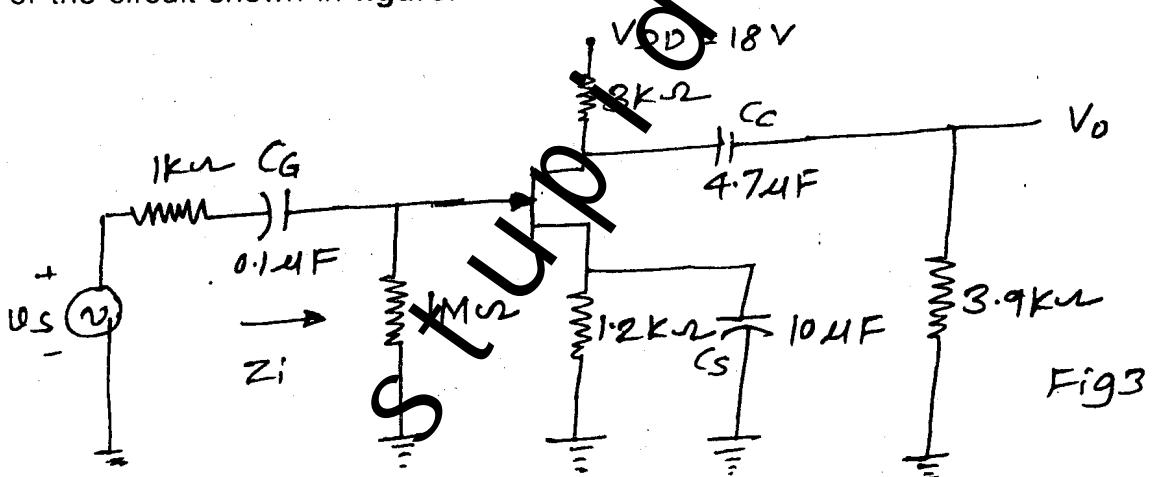

For JFET $I_{DSS} = 6 \text{ mA}$, $V_p = -6 \text{ V}$, $r_d = \infty$, $C_{gd} = 4 \text{ pF}$, $C_{gs} = 6 \text{ pF}$, $C_{ds} = 1 \text{ pF}$ and $C_{wi} = 3 \text{ pF}$, $C_{wo} = 5 \text{ pF}$.

- Determine V_{GSQ} and I_{DSQ} .
- Determine g_{m_o} and gm .

- Calculate midband gain $A_v = \frac{V_o}{V_i}$

- Determine Z_i

- Calculate $A_{vs} = \frac{V_o}{V_s}$

- Calculate lower cutoff frequency due to C_G , C_S and C_C as shown in figure. Also find effective lower cutoff frequency.


- Calculate higher cutoff frequency due to input time constant (fH_i) and due to output time constant (fH_o).

[TURN OVER]

Con. 6200-GT-6510-10.

2

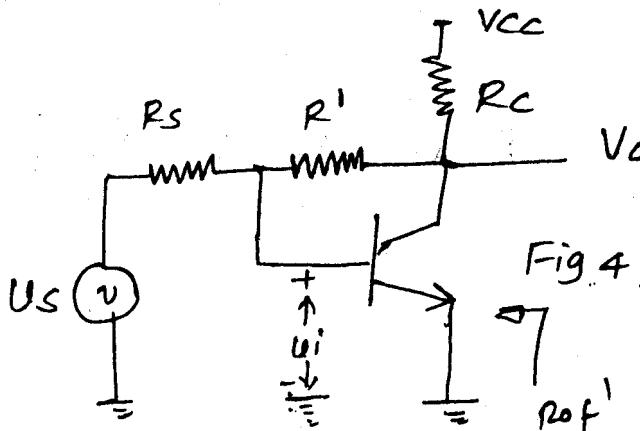4. (a) For the circuit shown in **figure**, identify type of feedback and determine (i) Avf, 10
(ii) Rif, (iii) R'of using feedback approach. (Note Vcc is not required.)




$$\begin{aligned}R_C &= 4K \\R'_1 &= 40K \\R_E &= 10K \\h_{ie} &= 1.1 \\h_{fe} &= 50 \\&\text{neglect } h_{re}, h_{oe}\end{aligned}$$

- (b) Explain various types of negative feedback amplifiers with the help of neat block diagrams. For each type give stability ratio, feedback factor (β), Input resistance Rif, output resistance Rof. 10

5. (a) For the differential amplifier shown in **figure** determine —

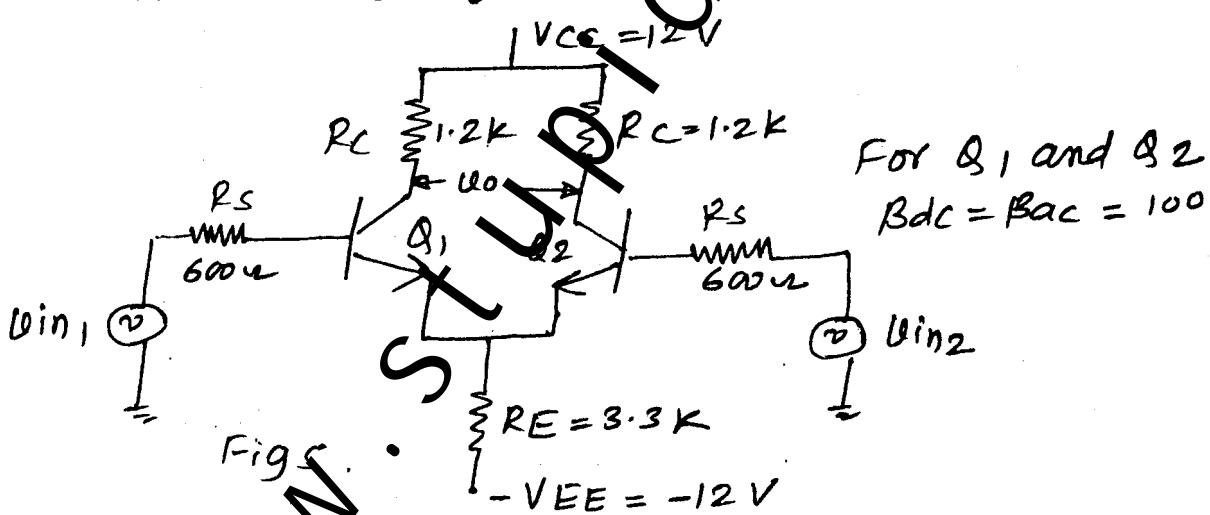- (i) I_{CQ} , V_{CEQ} (ii) Differential gain A_d (iii) Common Mode gain A_c and (iv) CMRR



- (b) Draw transistorized Astable Multivibrator and explain its working with waveforms at important nodes. 10

6. (a) Draw circuit diagram of RC phase shift BJT oscillator and derive expression for frequency of oscillation. 10
(b) Design a large signal transformer coupled class 'A' power amplifier to provide 10 W output to the 4Ω load. 10

7. Write short notes on any four :—

- (a) Cascode Amplifier (d) Class AB push-pull power amplifier
(b) High input impedance circuits (e) Schmitt trigger.
(c) High frequency LC oscillator

20

DBEC DATA SHEET

Transistor type	P_{dmax} @ 25°C Watts	I_{cmax} @ 25°C Amp	$V_{ce(\text{sat})}$ volts	V_{ceo} (Sus)	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$V_{ce(sus)}$ volts d.c.	$T_j \text{ max}$ °C	D.C. current min	gain typ.	Small signal max.	h_f	V_{be} max.	θ_{je} above 25°C	θ_{je} W/°C		
ECN 055	115.5	15.0	1.0	60	60	60	70	200	20	50	70	15	50	1.8	1.5	0.7	
ECN 149	50.0	5.0	1.0	50	50	55	60	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 100	30.0	4.0	1.0	50	50	—	—	150	30	50	110	33	60	115	1.2	4.0	0.3
BC147A	5.0	0.7	0.6	70	60	—	—	200	50	90	280	50	90	280	0.9	3.5	0.05
2N 525(PNP)	0.225	0.5	0.25	85	45	6	125	115	180	220	125	220	260	0.9	—	—	—
BC147B	0.25	0.1	0.25	50	45	6	100	35	—	65	—	45	—	—	—	—	—

Transistor type	hie	hoe	hre	θ_{ja}	BF 11-JFET MUTUAL CHARACTERISTICS														
BC 147A	2.7 KΩ	18μ A	1.5 × 10 ⁻⁴	0.4°C/mw	—	—	—	—	—	—	—	—	—	—					
2N 525 (PNP)	1.4 KΩ	25μ A	3.2 × 10 ⁻⁴	—	—V _{gs} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
BC 147B	4.5 KΩ	30μ A	2 × 10 ⁻⁴	0.4°C/mw	I _{ds} max. mA	10	9.0	8.3	7.7	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
ECN 100	500 Ω	—	—	—	I _{ds} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
ECN 149	250 Ω	—	—	—	I _{ds} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
ECN 055	100 Ω	—	—	—															
2N 3055	25 Ω	—	—	—															

N-Channel JFET

Type	$V_{ds \text{ max.}}$ Volts	$V_{dg \text{ max.}}$ Volts	$V_{gs \text{ max.}}$ Volts	$P_d \text{ max.}$ @25°C	$T_i \text{ max.}$	I_{dss}	g_m (typical)	$-V_p$ Volts	i_d Derate above 25°C	θ_{ia}	
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ A	6	50 kΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ A	2.5	50 kΩ	—	0.59°C/mW