

**DECEMBER 2008**

Code: AE09

Subject: ANALOG & DIGITAL ELECTRONICS

Time: 3 Hours


Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following:  
(2x10)

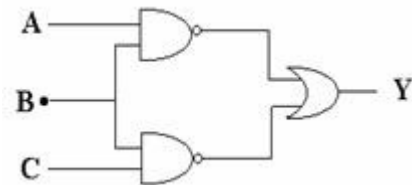- a. A PLA can be used  
(A) as a microprocessor logic. (B) a combinational logic.  
(C) a sequential logic. (D) None of above.
- b. For the logic circuit shown the O/P Y is equal to



- (A)  $\overline{ABC}$   
(B)  $\overline{A} + \overline{B} + C$   
(C)  $\overline{A} + \overline{B} + \overline{C}$   
(D)  $\overline{AB} + \overline{BC}$
- c. Which one is the fastest logic family  
(A) ECL. (B) TTL.  
(C) NMOS. (D)  $T^2L$
- d. If each input voltage is amplified by a different factor at the output then the opamp circuit is called as

- (A) Averaging amplifier.                      (B) Summing amplifier.  
 (C) Scaling amplifier.                        (D) Differential amplifier.
- e. The input resistance of 741 op-amp is
- (A) 10  $M\Omega$ .                                      (B) 1  $M\Omega$ .  
 (C) 100  $\Omega$ .                                        (D) 1  $K\Omega$ .
- f. The ratio of change in input offset voltage when variation in supply voltage is made, is called \_\_\_\_\_
- (A) SVRR    (B) Slew rate  
 (C) CMRR    (D) Voltage gain
- g. A 1:16 demultiplexer has following features
- (A) 1 I/P, 16 O/P's, 4 control signals.  
 (B) 2 I/P, 8 O/P's, 2 control signals.  
 (C) 2 I/P, 8 O/P's, 2 strobe signals.  
 (D) 16 O/P's.
- h. Unity gain bandwidth Product of 741 op-amp is
- (A) 4 MHz    (B) 6 MHz  
 (C) 1 MHz    (D) 100 Hz
- i. A notch filter is a
- (A) Wide band pass filter                      (B) Narrow band pass filter  
 (C) Wide band reject filter                      (D) Narrow band reject filter
- j. The number of flip flop required to construct MOD-7 counter that counts from 0 to 6 is
- (A) 4.    (B) 3.  
 (C) 2.    (D) 1.

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. Explain the factors that determines the operating speed of Logic gate. Discuss, how the speed performance can be improved in Schottky TTL transistors. (8)

- b. Write the various features of ECL family and draw the basic ECL logic NOR gate and explain it. (8)
- Q.3** a. Explain the architecture of 741 op-amp? Discuss the operation of each block? (8)
- b. Draw the circuit of a MOS operational amplifier & explain its operation. (8)
- Q.4** a. Compare and contrast a programmable logic array with a programmable array logic (PAL). (6)
- b. Write the acronyms EPROM & E<sup>2</sup>PROM. (2)
- c. What do you mean by priority encoder and explain the priority encoder for 10 line decimal to 4 line BCD with its truth table? (8)
- Q.5** a. What is race around condition in JK flip flop? How this condition will be overcome? (8)
- b. Explain how shift register can be used as  
(i) serial to parallel data converter, and (ii) parallel to serial data converter. (8)
- Q.6** a. What are the different types of A/D converter? Explain the converter, which is designed to convert analog wave form into binary code. (8)
- b. Explain Dual slope converter. Discuss the advantages & disadvantages of Dual slope converter. (8)
- Q.7** a. What types of MOSFET is used in CMOS logic family? Mention its advantages & disadvantages with a neat sketch. Also describe the CMOS NOR gate. (12)
- b. Draw the circuit symbol for transmission gate? Explain the operation of transmission gate in short. (4)
- Q.8** a. Explain how switched capacitor filter behaves as a resistance with a circuit diagram. (8)
- b. Determine the order of 1-dB ripple Chebyshev filter that gives a 40 dB attenuation at  $\omega/\omega_c = 2$ . Determine the 3-dB bandwidth of the filter. (8)
- Q.9** Write short notes on any **TWO** of the following:
- (i) N-MOS logic circuits.
- (ii) log and antilog amplifiers.

- (iii) Digital comparator.
- (iv) Seven segment display system.

**(8+8)**