

Code: AE-27

Subject: DIGITAL HARDWARE DESIGN

<b>JUNE 2007</b>
------------------

Time: 3 Hours

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
  - Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
  - Any required data not explicitly given, may be suitably assumed and stated.
- 

**Q.1 Choose the correct or best alternative in the following: (2x10)**

- a. VHDL, stands for
- (A) Verilog Hardware Description Language  
(B) Very High Speed Device Language  
(C) Versatile Hardware Description Language  
(D) Very High Speed Integrated Circuit Hardware Description Language
- b. "The main module is described as the interconnection of simpler modules (hierarchical description)". This statement discuss
- (A) Behavioural Architecture                      (B) Data flow Architecture  
(C) Structural Architecture                      (D) None of the above
- c. Two numbers with digits X and Y and radix 5 and 4 have following relationship:  $(XY)_5 = (YX)_4$  then
- (A) X=4, Y=3                                      (B) X=4, Y=3  
(C) X=6, Y=3                                      (D) X=3, Y=4
- d. Arrange the microinstruction execution cycle
1. Fetch    2. Execute    3. Decode    4. calculate the address of next
- (A) 1-2-3-4                                      (B) 1-3-2-4  
(C) 2-1-3-4                                      (D) 2-3-1-4
- e. Typical elements of a SRAM-controlled FPGA are:
- (A) Programmable switches and multiplexers  
(B) Look-up tables  
(C) Flip-Flops  
(D) All of the above

f. Hamming code for the decimal digit 4 coded in BCD is

- (A) 1001100                      (B) 1000100  
(C) 0010100                      (D) 1101100

g. The circuit shown in Fig.1 detects the following sequence

- (A) 0111                              (B) 0000  
(C) 0101                              (D) 1111

 


Fig. 1

h. The correct answer of the simplified form of the Boolean equation

$$T(x,y,z) = (x+y) [x'(y'+z')] + x'y' + x'z'$$

- (A) 0                                      (B) 1  
(C)  $x+y'$                               (D)  $y'+z'$

i. Compare to Vertical control field format, Horizontal control field format:

- (A) is faster in generation of the control signal  
(B) is inefficient in memory space usage  
(C) requires no decoding  
(D) All of the above

j. A multiplier multiplies N bit binary number by M bit binary number, the bit size of the result is

- (A)  $N \times M$                               (B)  $N^2$   
(C)  $M^2$                                       (D)  $N+M$

---

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

---

**Q.2** a. Briefly explain the following:

(i) Races

(ii) Package declaration in VHDL

(iii) Unate function

(iv) Explicit sequencing

**(2+2+2+2=8)**

b. Find the prime implicants of the function

$$f(x_3, x_2, x_1, x_0) = \text{zero-set}(7, 13, 15). \quad (4)$$

c. Design a minimal gate network for a combinational system specified as follows:

Input:  $x \in \{0, 1, 2, \dots, 9\}$  coded in BCD as

$$\underline{x} = (x_3, x_2, x_1, x_0), x_i \in \{0, 1\}$$

Output:  $z \in \{0, 1\}$

$$\text{Function: } z = \begin{cases} 1 & \text{if } x \in \{0, 2, 3, 5, 8\} \\ 0 & \text{otherwise} \end{cases} \quad (4)$$

**Q.3** a. What do you mean by functional decomposition? Explain serial and parallel decomposition. **(8)**

b. Define symmetric function and find whether the function

$F(w, x, y, z) = \sum (0, 1, 3, 5, 8, 10, 11, 12, 13, 15)$  is symmetric. If it is so express the function in symmetric notation.

**(8)**

**Q.4** a. Discuss relationship between system specification and implementation of digital system. **(3)**

b. Briefly explain the following:

(i) FPGA

(ii) Modulo K counter

**(6)**

c. Determine whether the function

$f(x_1, x_2, x_3, x_4) = \sum (0, 1, 3, 4, 5, 6, 7, 12, 13)$  is a threshold function, and if it is, find a weight-threshold vector. **(7)**

**Q.5** a. Discuss importance and classification of data paths. **(6)**

b. Design a synchronous sequential circuit, which is required to produce an output pulse  $z=1$ ,

whenever the sequence 1111 occurs. Overlapping sequences are accepted. For example, if the input is 01011111....., the required output is 00000011.

(i) Draw a state diagram.

(ii) Select an assignment and show the excitation and output tables

(iii) Write down the excitation functions for SR flip-flops, and draw the corresponding logic diagram. **(10)**

**Q.6** a. Implement a four bit adder using a 512 X 5 ROM module. **(4)**

b. Draw an ASM chart to detect the sequence 0101. **(6)**

c. Implement six input decoder using co-incident and tree decoder networks. **(6)**

**Q.7** Write the VHDL code for the following:

(i) Write a VHDL code for D flip-flop with asynchronous clear and preset using behavioural approach.

(ii) Write a VHDL code for one bit full adder using data flow architecture. Extend it to 4 bit adder using structural approach.

(iii) Write a VHDL code for 4-bit shifter with following features:

(a) parallel Load (b) left right shift control **(4+6+6)**

**Q.8** a. Discuss Ring counter in detail. Modify Ring counter to make it Twisted-tail ring counter. **(6)**

b. For the following machine shown in Table 1, find the equivalence partition and a corresponding reduce machine in standard form. Also solve same problem with merger graph method. **(10)**

PS	NS, Z	
	X=0	X=1
A	F, 0	B, 0
B	F, 0	A, 0
C	E, 0	B, 1
D	E, 0	A, 1
E	C, 0	F, 1
F	B, 0	C, 0

**Table 1**

**Q.9** Write explanatory notes on (Any **FOUR**)

- (i) Hazard free asynchronous circuits
- (ii) Structural style of Modeling in VHDL
- (iii) Incompletely specified machine
- (iv) Compare Moore Model and Melay model with example
- (v) Merits and Demerits of Programmable modules. **(4 × 4)**