

Code: A-09/C-03/T-03

Subject: ANALOG & DIGITAL ELECTRONICS

Time: 3 Hours


Max. Marks: 100

NOTE: There are 11 Questions in all.

- Question 1 is compulsory and carries 16 marks. Answer to Q. 1. must be written in the space provided for it in the answer book supplied and nowhere else.
- Answer any THREE Questions each from Part I and Part II. Each of these questions carries 14 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or best alternative in the following:  
(2x8)

 - a. For the circuit shown in Fig.1, the input resistance  $R_{id}$  will be
- (A)  $2R_1$ . (B)  $2R_1 + R_2$ .  
(C)  $2(R_1 + R_2)$ . (D) Infinity.




- b. A second order filter has its poles at  $s = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$ . The transmission is zero at  $\omega = 2 \text{ rad/s}$  and is unity at  $\omega = 0$ . The transfer function of the filter is
- (A)  $\frac{1}{4} \frac{(s^2 + s)}{(s^2 - s + 1)}$ . (B)  $\frac{1}{4} \frac{(s^2 + s)}{(s^2 + s + 1)}$ .  
(C)  $\frac{1}{4} \frac{(s^2)}{(s^2 + s + 0.25)}$ . (D)  $\frac{1}{4} \frac{(s^2 - s)}{(s^2 - s - 1)}$ .

$$T(s) = \frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

c. Transfer function of a filter is given by \_\_\_\_\_ filter. . It represents a


- (A) Low pass. (B) High pass.  
(C) Band pass. (D) Band stop.

d. The circuit shown below in Fig.2

 

represents \_\_\_\_\_ filter.

 - (A) Low pass. (B) High pass.  
(C) Band pass. (D) All pass.



- e. The circuit shown in Fig.3 below represents \_\_\_\_\_ gate
- (A) AND.  
 (B) NAND.  
 (C) OR.  
 (D) NOR.
- f. Active loaded MOS differential circuit has a
- (A) high CMRR. (B) low CMRR.  
 (C) high delay. (D) high differential gain.
- g. NPN transistor is not suitable for good analog switch because
- (A)  $I_C - V_{CE}$  characteristic curve pass directly through origin.  
 (B) the device has very high input impedance.  
 (C) the device is asymmetrical with an offset voltage  $V_{CE\ off}$ .  
 (D) it has well defined transition frequency  $f_T$ .
- h. CMOS logic has the property of
- (A) increased capacitance and delay. (B) decreased area.  
 (C) high noise margin. (D) low static power dissipation.

### PART I

Answer any THREE Questions. Each question carries 14 marks.

- Q.2** a. Explain Miller Integrator. What are the effects of the OP-AMP input offset voltage, input bias and offset currents on the performance of Miller Integrator. (7)
- b. Consider a symmetrical square wave of 20V peak to peak, zero average and 2ms period applied to a Miller integrator. Find the value of the time constant (CR) such that the triangular waveforms at the output has 20V peak to peak amplitude. (7)
- Q.3** a. Draw the circuit diagram of two stage CMOS op-amp configuration. What do you understand by systematic output dc offset voltage? How can it be eliminated? (8)
- b. Draw the circuit diagram of a CMOS inverter and explain its operation. (6)
- Q.4** The transfer function of a two port network is given by  $T(s) = \frac{z_2}{z_1 + z_2}$  where  $z_1$  and  $z_2$  represent any impedances. Explain how the following passive filters can be realized from this network.
- (i) Bandpass filter. (4)
- (ii) Notch filter. (5)
- (iii) All pass filter. (5)
- Q.5** a. With proper diagram explain the operation of dual slope A/D converter and charge redistribution A/D converter. Compare their advantages and disadvantages. (10)
- b. Explain the operation of sample & hold circuit. Discuss its applications. (4)
- Q.6** a. What types of doping should be used in a switching diode. What is reverse recovery time? (4)
- b. Explain the operation of a MOSFET analog switch with suitable circuit diagram. (6)
- c. What property of Schottky diode make it suitable for fast switching? Explain. (4)

## PART II

**Answer any THREE Questions. Each question carries 14 marks.**

- Q.7** Implement the following Boolean expressions by synthesizing Pull up and Pull down networks:

(i)  $Y = \overline{AB}$ . (4)

(ii)  $Y = \overline{A(B + CD)}$ . (5)

(iii)  $Y = A\overline{B} + \overline{A}B$ . (5)

**Q.8** a. Explain the following logic families and compare their performances. (9)

(i) ECL. (ii) TTL

b. How ECL and TTL logic families are interfaced with each other. (5)

**Q.9** a. With a suitable circuit diagram explain how a four bit binary full adder works. How this 4-bit adder can be used as subtracter. (8)

b. Explain the operation of a BCD to decimal decoder. (6)

**Q.10** Explain the following with timing diagram.

(i) JK flip-flop. (7)

(ii) Clocked SR flip-flop. (7)

**Q.11** Write short notes on any **TWO** of the following:

(i) Programmable logic Array.

(ii) RAM & PROM.

(iii) Seven segment display system.

(iv) Shift register. (7+7)