

Con. 1717-06.

(REVISED COURSE)  
(3 Hours)TV-7956  
[Total Marks : 100]

- N. B. : (1) Question No. 1 is compulsory.  
(2) Solve any four out of remaining six questions.

1. (a) Find Hexadecimal Equivalent of - 6
- 1)  $(2338.122)_{10}$
  - 2)  $(326)_7$
  - 3)  $(761.514)_8$
- (b) Perform the following operations - 6
- 1)  $(F88)_{16} + (D89)_{16}$
  - 2)  $(762)_{BCD} + (348)_{BCD}$
  - 3)  $(246)_{10} - (435)_{10}$  using 2's complement method.
- (c) What are self complementing codes ? Explain with 2 examples. 4
- (d) Perform the following operations - 4
- 1)  $(1101.11)_2 \times (101.1001)_2$
  - 2)  $(10000111)_2 \div (1101)_2$
2. (a) Simplify using Boolean Theorems and implement using AOI gates only -
- 1)  $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$ . 3
  - 2)  $[(C + \bar{C}D)(C + \bar{C}\bar{D})][(AB + \bar{A}\bar{B}) + (A \oplus B)]$  5
- (b) Given logic expression.
- $$F = A\bar{B} + AC + \bar{C} + A\bar{B}C + ABC.$$
- 1) Express in Standard SOP form and simplify using boolean theorems. 6
  - 2) Draw K map and simplify 3
  - 3) Draw a logic diagram using NAND gates only. 3
3. (a) Implement BCD Adder using 7483, 4 bit binary adder IC. Explain its operation. 10
- (b) What is SR Flip Flop ? Explain its operation. Write truth table, characteristic equation and excitation table for the same. 10
4. (a) There are four adjacent parking slots in a company. Each slot is equipped with a special sensor whose output is asserted low when a car is occupying a slot, otherwise the sensor's output is high. Design and draw a schematic for a system, which will generate a low output if and only if there are two or more than two adjacent slots vacant. 10
- (b) Explain the working of IC 7485, 4 bit comparator and hence implement a 5 bit comparator using the same IC. 10
5. (a) Using Quine McClusky method of minimization 12
- solve,
- $$F = \sum m(8,9,10,11,13,15,16,18,21,24,25,26,27,30,31)$$
- (b) Write a VHDL program for decoder like 74LS138 (3:8 decoder) 8
6. (a) Explain what is tristate gate. Draw the symbol, truth table and circuit diagram of the same. 8
- (b) Draw a neat circuit diagram of 2 inputs TTL NAND gate and explain its operation. Draw transfer Characteristics and give specifications of the same. 12

7. (a) What is a multiplexer ? Implement,  
 $F = \pi M (0,1,4,5,7)$  using 4:1 multiplexer.

8

(b) Write short notes on (any two) :—

12

- 1) Master slave JK flip flop
- 2) Static hazards
- 3) 74180 Parity generator and Checker .