

Total number of printed pages – 8

B. Tech

BENG 1105

First Semester Examination – 2007

BASIC ELECTRONICS

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory
and any *five* from the rest.

The figures in the right-hand margin
indicate marks.

1. Answer the following questions : 2×10
- (a) Distinguish metals from semiconductors
with reference to position of Fermi level.
- (b) What is Zener Breakdown ? Give two
reasons.

P.T.O.

(c) Derive the expression of I_C versus I_B for a CE transistor configuration.

(d) Convert $(0.275)_{10}$ into binary equivalent and $(100101)_2$ into decimal equivalent.

(e) Derive the expression for amplification factor μ of FET.

(f) Draw the circuit of an OPAMP integrator.

(g) Write two disadvantages of positive feedback.

(h) Give two reasons of using modulation.

(i) Draw frequency response of a practical operational amplifier.

(j) Define modulus of an n-bit counter. What is the modulus of a decade counter ?

2. (a) Name a p-n diode that is used in tuned circuits. Explain its operation. 2

(b) Draw the circuit of a double ended clipper using ideal p-n diodes which limits the outputs from +3 Volt to -3 Volt for sinusoidal input of amplitude 5 Volt. 3

(c) Draw output waveform V_o for the biased clamping circuit shown in Fig. 1. Assume $V_i = 5V$ square wave. What happens to the output waveform when the diode is reversed ? 5

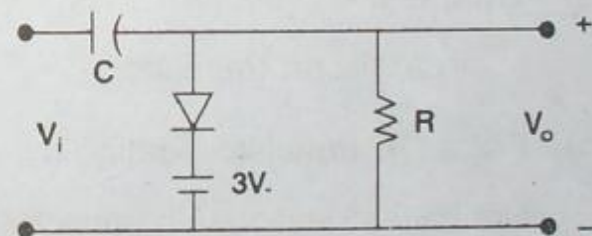


Fig. 1

3. (a) In the circuit shown in Fig. 2, find the minimum value of R_x for which the transistor remains in saturation. Assume that a silicon transistor with $V_{BE, sat} = 0.8$ volt, $\beta = h_{FE} = 100$ and $V_{CE, sat} = 0.2$ V is used in the circuit.

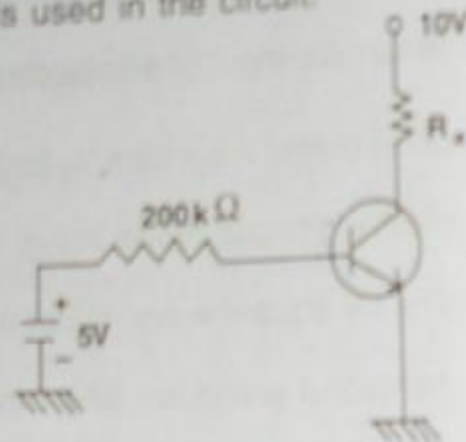


Fig. 2

- (b) What is the collector current relative to I_{CO} in a silicon transistor?
- (c) For a CE transistor, define h_{FE} and h_{FE} . Derive the relationship between h_{FE} and h_{FE} .

4. (a) For the circuit shown in Fig. 3, find the collector current I_C . Assume that a silicon transistor with $h_{FE} = 98$ is used.

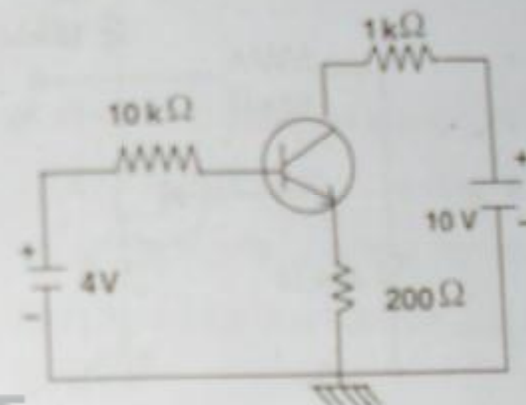


Fig. 3

- (b) Describe the principle of operation of enhancement type MOSFET with suitable diagrams. Sketch its transfer characteristics.
5. (a) Calculate the voltage gain of the circuit shown in Fig. 4, if the input is given

between gate and ground. The FET parameters are $\mu = 30$ and $r_d = 5 \text{ K ohms}$.

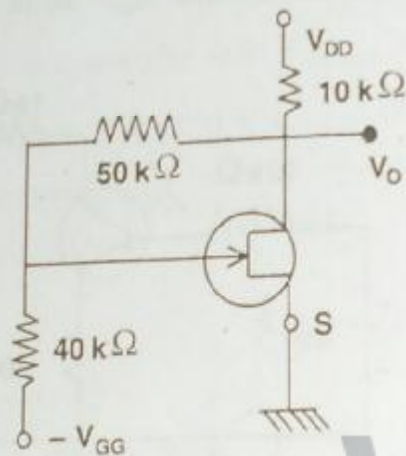


Fig. 4

- (b) The gain of an amplifier changes from a value of -800 by 10% . Calculate the gain change of the amplifier used in a feedback circuit with $\beta = -\frac{1}{20}$.

6. (a) Sketch the circuit diagram of a modulo 10 counter. Explain the operation.

- (b) Using Boolean algebra, verify

$$\overline{AB + BC + CA} = \overline{A} \overline{B} + \overline{B} \overline{C} + \overline{C} \overline{A} \quad 2$$

- (c) Implement EXOR logic using NOR gates only.


7. (a) Draw the schematic block diagram of the basic OPAMP with inverting and non inverting inputs. Indicate its equivalent circuit. List six characteristics of an ideal OPAMP.

- (b) Sketch the output of a differentiator circuit using an OPAMP, if the input is a square wave of 10 MHz . Assume the time constant of the circuit to be 1 milli seconds .

8. (a) Derive the relationship between the output power of an AM transmitter and the depth of modulation, and plot this as

a graph for values of the modulation index from zero to maximum. A suppressed zero graph is misleading in this instance, and must not be used. 5

- (b) A certain transmitter radiates 9 kW with the carrier unmodulated, and 10.125 kW when the carrier is sinusoidally modulated. Calculate the modulation index. If another sine wave, corresponding to 40% modulation is transmitted simultaneously, determine the total radiated power. 5

 **VGYAN**.COM
POWER OF KNOWLEDGE