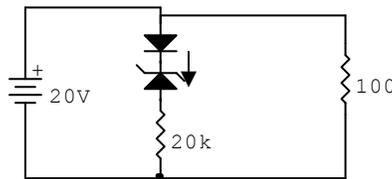



**FOURTH SEMESTER EXAMINATION -2005
BASIC ELECTRONICS**

Answer question no. 1 which is compulsory and any five from rest

1. Answer the following. 2x10
- a. If the depletion width of a p-n junction with doping levels of $N_A = 10^{16} /\text{cm}^3$ and $N_D = 10^{18} /\text{cm}^3$ is x_d , what distance does the depletion region penetrate into n-side of the junction?
- b. What is the value of the current I in the following circuit assuming $V_z = 5.6\text{V}$ and $V_D = 0.7\text{V}$.




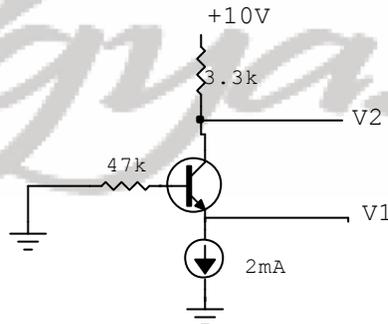- c. If $292_{10} = 1204_b$, determine the value of b .
- d. Convert the decimal number 359 to its octal equivalent .
- e. Find the node voltage V_2 and I_c for the following circuit . Take β to be very high.




- f. An enhancement type NMOs transistor with $V_1 = 2\text{V}$ has its source terminal grounded and its gate is given given 3V . In what region of operation the device operates for $V_D = 5\text{V}$ and $V_D = 1\text{V}$?

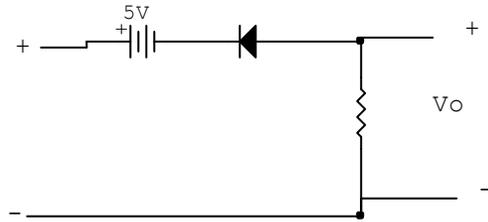- g. Draw and scale the output waveform of the following circuit if a sinewave of 10V p-p is applied to the following circuit.



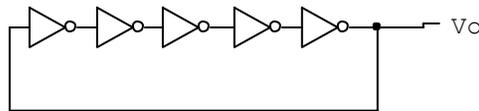- h. A 10V forward voltage is applied to a silicon diode in series with a load of $10K\Omega$. Draw the dc load line and find its slope.
- i. If each inverter in the following figure has a propagation delay of 10ns, determine the waveshape of the output waveform V_o . What is its frequency?




- j. Apply DeMorgan's law to the following expression :


$$\overline{A\overline{B}(C + \overline{D})}$$

- A germanium diode displays a forward voltage of 0.25V at 10mA current at room temperature ($300^\circ K$). Estimate the reverse saturation current (I_s) assuming unity ideality factor. Calculate the bias voltage needed for diode currents of 1mA and 100mA. Also estimate the values of I_s and diode forward current at 0.25V at $30^\circ C$ above room temperature. 10
- A bridge rectifier uses a diode with forward resistance of 5Ω and secondary voltage is 30V(rms). Determine the dc output voltage for $I_{dc} = 200mA$ and the rms value of the output ripple voltage. 10
- For both the circuit shown below calculate I_B , I_C and V_{CE} . Take $V_{CC} = 22V$, $V_{BE} = 0.7V$, $R_B = 86K$, $R_C = 1K$, $R_E = 1K$, $R_F = 80K$, $V_{BE} = 0.7V$ and $\beta = 120$. 5+5


a.

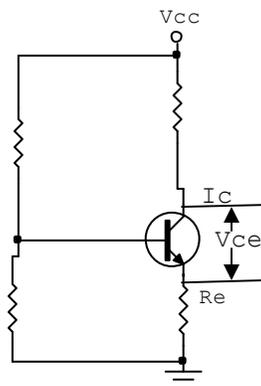

b.

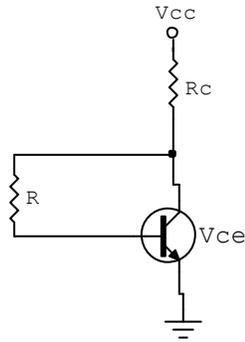

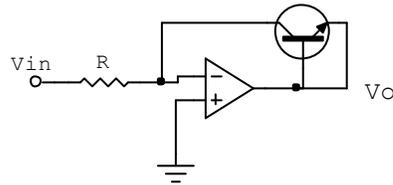6. Derive the transfer characteristics in terms of R , I_s (I_s being the reverse saturation current of the transistor) and V_T . Assume $n=1$. 10



7. a. Bring out the essential difference between an analog communication system and a digital communication system. 5
 b. What type of time base is used in a CRO? Explain with a neat sketch.. 5

Vgyan.com

--X--