

Roll No.

Total No. of Questions : 09]

*Library -
May 2008*

[Total No. of Pages : 02

Paper ID [EC204]

(Please fill this Paper ID in OMR Sheet)

B.Tech. (Sem. - 4th)

DIGITAL ELECTRONICS (EC-204)

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 × 2 = 20)

- a) Convert decimal 225.225 to binary, octal and hexadecimal bases.
- b) Give the truth-table for each flip-flop type: (a) J-K; (b) D; and (c) T.
- c) Find two's complement of the numbers (i) 01001110; (ii) 01100100.
- d) List applications of a direct coupled amplifier.
- e) Explain why there may be a race condition in a shift register?
- f) In a function of six variables the total maximum number of terms which the expression can have will be
- g) Comment on the parameters which serve to describe the quality of performance of a D/A converter.
- h) What is a ripple counter?
- i) Differentiate between static and dynamic shift registers.
- j) Determine the resolution of the output from a DAC that has a 12-bit input.

Section - B

(4 × 5 = 20)

- Q2)** A four-variable function is given as $f(A,B,C,D) = \prod M(0,3,4,5,6,7,11,13,14,15)$. Use a K-map to minimize the function.
- Q3)** Define a demultiplexer. Show how to convert a decoder into a demultiplexer. Indicate how to add a strobe to this system.

- Q4)** Draw the logic symbols for T and RST flip-flops. Explain the function of each type of flip-flop.
- Q5)** Give an order of magnitude which is applicable to various logic families for (a) fan-out; (b) power dissipation per gate; (c) propagation delay per gate; (d) clock rate.
- Q6)** Represent the decimal numbers (a) 27, (b) 396 and (c) 4096 in binary form in (i) ASCII code, (ii) Gray code, and (iii) Excess 3 code.

Section - C

(2 × 10 = 20)

- Q7)** Draw and explain the basic block diagram of (i) voltage of frequency conversion and (ii) voltage of time conversion
- Q8)** (a) Draw the basic block diagram of a voltage of frequency conversion. Sketch the system waveforms and explain its operation.
- (b) An A/D converter has the following characteristics: resolution = 12 bits; relative accuracy = 0.03 per cent full scale; and full scale output = +5V.
- (i) What is the quantization error in volts?
- (ii) What is the possible error in volts?
- Q9)** Write short notes on the following:
- (a) Counter design with state equation and state diagrams.
- (b) Classification and characteristics of memories.