

**B.TECH. DEGREE III SEMESTER (SUPPLEMENTARY) EXAMINATION IN
INFORMATION TECHNOLOGY/COMPUTER SCIENCE AND ENGINEERING
JUNE 2002**

**IT/CS 304 DIGITAL CIRCUITS AND
LOGIC DESIGN
(1995 Admissions)**

Time: 3 Hours

Maximum Marks: 100

- I. (a) Convert the following decimal numbers to binary:
(i) 12.0625 (ii) 673.23 (2 x 5 = 10)
(b) Convert the following binary numbers to decimal:
(i) 1110101.110
(ii) 1101101.111 (2 x 5 = 10)
- OR**
- II. (a) Convert the following numbers to decimal, octal and binary.
(i) $(2AC5.D)_{16}$ (ii) $(F329)_{16}$ (12)
(b) Explain various error detecting and error correcting codes. (8)
- III. (a) Simplify the Boolean function using k-map.
 $f(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ (10)
(b) Design a 3 to 8 line decoder and show its truth table. (10)
- OR**
- IV. Implement a full adder circuit with a decoder and two OR gates. (20)
- V. (a) Explain tristate logic and its application. (10)
(b) Draw the circuit diagram of a basic 2 inputs NAND gate in TTL and explain its operation. (10)
- OR**
- VI. (a) Explain the techniques for interfacing TTL to CMOS and CMOS to TTL. (10)
(b) List out the specification(s) of the TTL logic family. (10)
- VII. (a) Using a suitable diagram, explain the working of a master slave J - K Flip-Flop. Explain how race around condition is eliminated. (10)
(b) With a circuit diagram explain the working of a modulo-8 counter. (10)
- OR**
- VIII. (a) Draw the circuit of a Johnson counter. Explain its operation. (10)
(b) What are the difference(s) between synchronous and asynchronous digital logic circuits? (10)
- IX. (a) Explain the application(s) of ROMs and RAMs. (10)
(b) Explain how write operation takes place in a magnetic core memory. (10)
- OR**
- X. (a) Explain the principle and use of PLA. (10)
(b) With a logic diagram, explain 74157 two input data selector/multiplexer. (10)

