

B.Tech. Degree III Semester Examination
January 2002

- X. (a) Realise a 32 - to - 1 line multiplexer using four 8 : 1 muxes and one 4 : 1 mux. (12)
 (b) Write short note on 'EPROM'. (4)
 (c) (i) How many address lines are there in the decoder of a 512 x 1 bit ROM?
 (ii) How many number of NAND gates are needed in the decoder for a 1024 x 2 bit ROM? (4)

IT 304 ELECTRONIC CIRCUITS AND LOGIC DESIGN

Time: 3 Hours


Maximum Marks: 100

- I. (a) Draw and explain the frequency response of an RC coupled amplifier. What is the role played various inter-electrode and wiring capacitors? (10)
 (b) Explain the construction of a crystal oscillator. Give the expression for resonant frequency. (8)
 (c) Why JFET is preferred in the design of front end of Radio Receivers? (2)


OR

- II. (a) Explain the drain curves for n-channel JFET. Show the different operating regions. What is I_{DSS} , $V_{GS(off)}$, V_P ? (12)
 (b) Explain with necessary diagram the working of Weinbridge oscillator. (6)
 (c) Specify the use of transformer coupling. (2)

 - III. (a) In the figure given below, the 1000Hz square wave is applied to the RC circuit. Compare the pulse width of the square wave to the time constant of the circuit. Sketch $V_C(t)$. (10)



(Turn over)

 

- III. (b) Describe the working of positive voltage clamper with sinusoidal input. (6)
 (c) Bringout the difference between differential gain and common-mode gain. What is CMRR? (4)

OR

- IV. (a) Explain the working of SCR using two transistor theory. Derive the condition required for turning ON the SCR. (8)
 (b) Explain the function of a 2-level diode clipper with necessary input, output waveforms. (6)
 (c) Determine the output voltage of a differential amplifier for input voltages of $V_{i1} = 150\mu V$ and $V_{i2} = 100\mu V$. The amplifier has a differential mode gain of $A_d = 1000$ and the value of CMRR is 40dB. Why high CMRR is desirable for op-amp? (6)

- V. (a) Realise a 4 bit Gray to 8421 code converter using basic gates.

Input gray code is $G_3 \ G_2 \ G_1 \ G_0$

Output 8421 code is $W \ X \ Y \ Z$

Use the K-map for simplification. (10)

- (b) Give the NOR-NOR implementation of $F = AB + \bar{B}C$. (6)
 (c) Why NAND gate is called a universal building block? Illustrate. (4)

OR

- VI. (a) Realise a Full adder using only NAND gates. Give the truth table for full adder. Realise the full adder using half adder and basic gates. (10)
 (b) Show that AND gate in a positive logic is the same as the OR gate in a negative logic. (6)
 (c) Find the canonical expansion of $X\bar{Y} + YZ + \bar{X}Z$. Distinguish between canonical and non-canonical form. (4)

Contd.....3.

- VII. (a) Explain the following terms with respect to digital ICs.
 (i) Noise margin (ii) Fan out
 (iii) Logic flexibility (iv) Operating speed
 (v) Power dissipation (10)

- (b) Specify at least two application areas where the following digital IC families are used.
 (i) TTL (ii) CMOS
 (iii) ECL (6)

- (c) Realise a 3-bit Ring counter using JK flipflops. Give the count sequence. (4)

OR

- VIII. (a) Summarise the advantages, limitations and typical application areas of CMOS digital ICs. (8)
 (b) An 8-bit ring counter uses a clock frequency of 2MHz.
 (i) How long is each timing bit high?
 (ii) How long does it take to cycle through all the counts? (4)
 (c) Design a mod 5 synchronous counter using JK flipflops. (8)

- IX. (a) Differentiate between PLA and PAL devices. (6)
 (b) Design an encoder using diode matrix for the following truth table. (6)

Inputs				Outputs			
X_3	X_2	X_1	X_0	Y_3	Y_2	Y_1	Y_0
0	0	0	1	0	1	1	1
0	0	1	0	1	1	0	0
0	1	0	0	1	1	0	1
1	0	0	0	0	0	1	0

- (c) Realise a 4 line-to-10 line decoder using basic gates. Give the required truth table. (8)

OR

Contd.....4.