

S.E. (COMPUTER INFORMATION TECHNOLOGY) SEM III
(REV) EXAMINATION MAY 2007

Con. 2856-07.

Digital Logic Design and Application

ND-432

(REVISED COURSE)

(3 Hours)

[Total Marks : 100

N.B (1) Question No. 1 is compulsory.

(2) Attempt any four questions out of remaining six questions.

(3) Assume suitable additional data if necessary.

1. (a) Convert $(1762.46)_{10}$ to Octal, Binary and Hexadecimal. 6
(b) Perform the following operations without converting to any other base. 8
- (i) $(BC5)_4 - (A2B)_H$
(ii) $(63)_8 * (14)_8$
(iii) $(102.3)_4 + (212.3)_4$
(iv) $(11010)_2 \div (101)_2$
- (c) (i) Write the truth table and excitation of J-K Flip Flop. 2
(ii) What is a Gray Code ? Give any application. 2
(iii) Write the Hamming Code for 1010. 2
2. (a) (i) Subtract using 1's and 2's complement method $(64)_{10} - (31)_{10}$. 2
(ii) Addition of 275 and 496 to be performed using BCD addition rules. 2
(iii) Implement EX-OR gate using four, two input NAND gates only. 2
(iv) State De-Morgans Theorems. 2
(b) Simplify using Boolean Theorems and draw Logic Diagram for the following : 12
- (i) $\bar{X}YZ + X\bar{Y}Z + XY\bar{Z} + XYZ$
(ii) $P [Q + R] (\overline{PQ + PR})$
(iii) $\bar{W}Y + \bar{W}XZ + \bar{W}X\bar{Y}\bar{Z} + W\bar{X}Y$
(iv) $A + \bar{A}B + (\bar{A} \cdot \bar{B}) C + ABCD$
3. (a) Given the logic expression— 12
- $AB + A\bar{C} + C + AD + \bar{A}\bar{B}C + ABC$
- (i) Express in standard SOP form
(ii) Draw the k-map for the equation
(iii) Minimize and realise using NAND gates only.
- (b) Realise the following using 16:1 MUX and 4:16 line decoder 8
 $f(A, B, C, D) = \sum m (1, 2, 4, 7, 11, 13)$
4. (a) Obtain minimal expression using Quine McClusky 10
 $f(A, B, C, D) = \sum m (0, 1, 3, 5, 7, 10, 11, 13, 14, 15)$
(b) Design a 4-bit BCD Adder using IC 7483. 10

[TURN OVER

5. (a) A panel light in the control room at the launching of a satellite is to go ON if and only if the pressure in both fuel and oxidiser tanks is equal to or above a required minimum and there are 10 minutes or less to lift off or if the pressure in the oxidiser tank is equal to or above a required minimum and pressure in fuel tank is below a required minimum but there are more than 10 minutes to lift off, or if the pressure in the oxidiser tank is below a required minimum but there are more than 10 minutes to lift off. 12
- Design a two level combinational circuit to control panel light.
- (b) Simplify $f(P, Q, R, S) = \pi M(0, 2, 5, 7, 8, 13, 15)$ using K-map and realise using NOR gates only. 8
6. (a) Design a 3 bit Up-Down Asynchronous Counter with direction control M using J-K Flip Flops. 10
- (b) Design a Decade Synchronous Counter using J-K Flip Flops. 10
7. (a) Draw neat diagram of two-input TTL NAND gate and explain its operation. Also draw transfer characteristics. 10
- (b) Write short notes on any two :— 10
- (i) PAL and PLA
 - (ii) ALU
 - (iii) Priority Encoder.