

Electronic Devices & Circuits - II 3 p.m. to 6 p.m.

Con. 2580-09.

VR-3825

(REVISED COURSE)

(3 Hours)

[Total Marks : 100

- N.B.: (1) Question Nos. 1 and 2 are **compulsory**.
 (2) Attempt **three** questions from the remaining **five** questions.
 (3) Assume suitable data if **necessary**.


1. (a) Draw the low frequency model of a JFET and obtain expressions for the voltage gain, input impedance, output impedance in CS Amplifier. 10
 (b) Show the effect of low frequency and high frequency on coupling and bypass capacitors. 10

2. (a) For a cascaded amplifier, show that the overall lower 3 dB frequency, 10

$$f_{LT} = \frac{f_L}{\sqrt{2^{1/n} - 1}} \text{ and } f_{HT} = f_H \sqrt{2^{1/n} - 1} \text{ with } n \text{ stages.}$$

- (b) A differential amplifier has a differential gain 50 dBs, CMRR = 75 dBs. 10
 $V_{s1} = 15 \text{ mv}$, $V_{s2} = 10 \text{ mv}$. Find error voltage and % error in the output voltage.

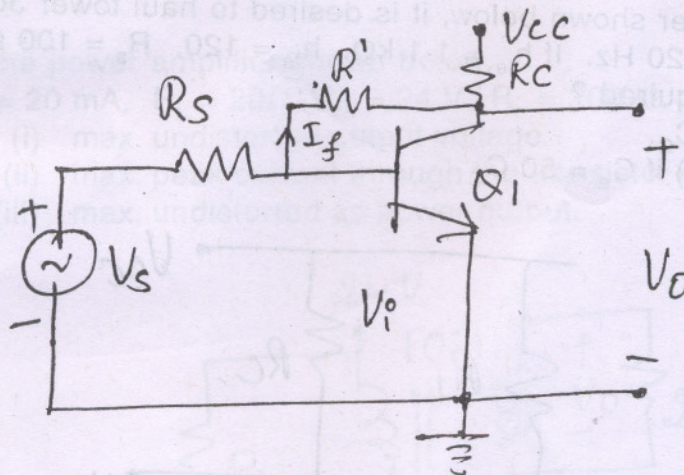3. (a) The following circuit has the parameters. $R_c = 4 \text{ k}\Omega$, $R' = 40 \text{ k}\Omega$, $R_s = 10 \text{ k}\Omega$, 12
 $h_{ie} = 1.1 \text{ k}\Omega$, $h_{ie} = 50$, $h_{re} = h_{oe} = 0$.
 Find A_{vf} , R_{if} , R_{of} , R_{if}' , R_{of}'



- (b) Explain the various feedback topologies. 8

4. (a) Derive an expression for the frequency of oscillation of a transistorized RC phase-shift oscillator. 12

- (b) A class A transformer coupled circuit is to deliver a maximum power of 6W to 4 Ω load. $V_{CC} = 25 \text{ V}$, $V_{min} = 0$. Find, 8


- (i) Transformer turn ratio (n) = $\frac{N_1}{N_2}$
 (ii) Peak collector current I_m .
 (iii) Q (I_C , V_{CE})
 (iv) Conversion efficiency.

5. (a) Explain the operation of a Schmitt Trigger with a neat sketch. **10**
- (b) Design a phase shift oscillator using FET having a $g_m = 5000 \text{ k}\Omega$, $r_d = 40 \text{ k}\Omega$, and a FB circuit of $R = 10 \text{ k}\Omega$. Frequency of oscillation is 1 KHz. **10**

[TURN OVER

6. (a) For the following circuit, $V_{cc} = 12\text{ V}$, $R_L = 4.7\text{ k}\Omega$, $R_E = 1\text{ k}\Omega$, $R_1 = 15\text{ k}\Omega$, $R_2 = 2.2\text{ k}\Omega$, $R_s = 600\ \Omega$. $h_{fe} = 100$, $h_{ie} = 1\text{ k}\Omega$. Find,

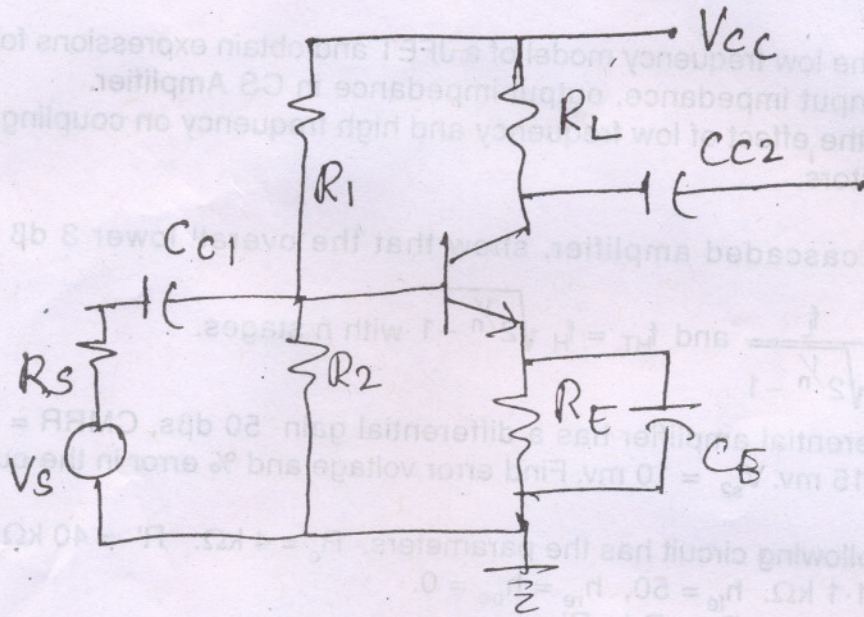
- (i) Calculate mid frequency voltage gain $\frac{V_o}{V_s}$ and $\frac{V_o}{V_i}$
- (ii) Calculate the size of bypass capacitor if $f_L = 50\text{ Hz}$.
- (iii) Calculate the size of coupling capacitor if $f_L = 50\text{ Hz}$.



(b) For the amplifier shown below, it is desired to haul tower 3dB frequency of not more than 20 Hz. If $h_{ie} = 1.1\text{ k}\Omega$. $h_{fe} = 120$, $R_s = 100\ \Omega$. What is the value of C_C required ?

Assume $C_e = C_C$.

(b) Repeat part (a) if $C_e = 50 C_C$

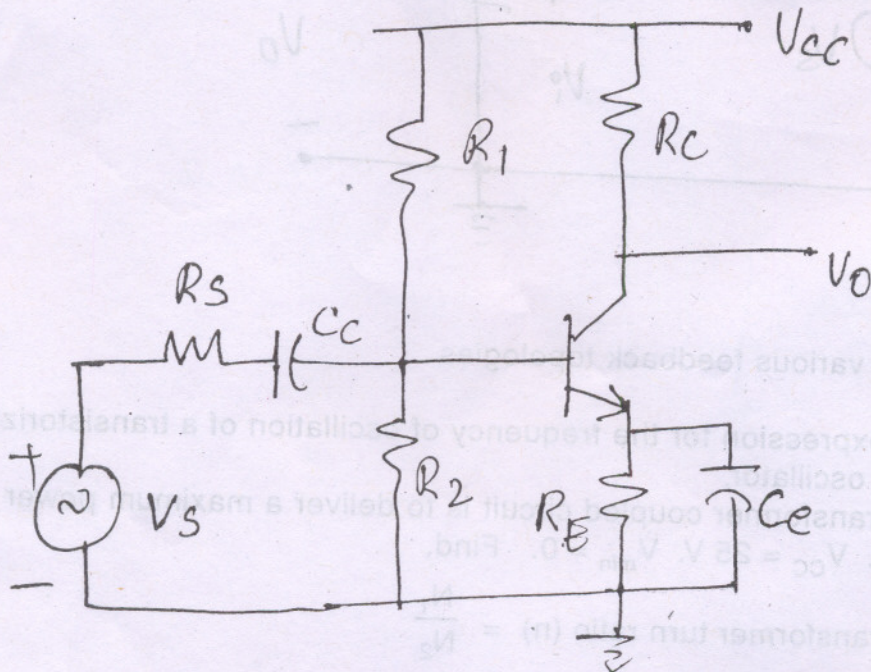


7. (a) The following circuit has the parameters—

$h_{ib} = 50 \Omega$, $h_{fb} = -0.99$, $h_{rb} = h_{ob} = 0$
 $h_{ie} = 500 \Omega$, $h_{fe} = -100$, $h_{re} = 1$ and $h_{oc} = 0$.

(i) Find the overall voltage gain $= \frac{V_o}{V_s}$

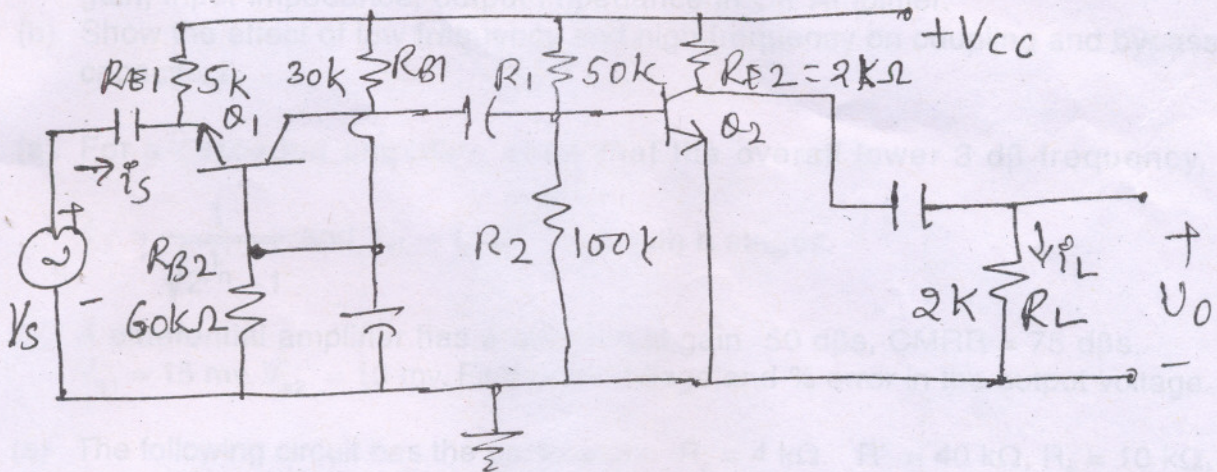(ii) Find the overall current gain $= \frac{i_L}{i_s}$



(b) For the power amplifier shown below,

$I_{CQ} = 20 \text{ mA}$, $R_L = 20 \Omega$, $V_{CC} = 24 \text{ V}$, $R_e = 200 \Omega$. Find

- (i) max. undistorted output voltage.
- (ii) max. peak current through the transistor collector.
- (iii) max. undistorted ac power output.

